

CIRCUIT CELLAR

I N K[®]

THE COMPUTER APPLICATIONS JOURNAL

**MEASUREMENT
& CONTROL**

*SPECIAL SECTION:
Embedded
Graphics & Video*

Time Domain Reflectometer

Overlay Text on Video

X-10 Interfacing

October/November, 1992 — Issue #29



\$3.95 U.S.
\$4.95 Canada

EDITOR'S INK

A Look at Next Year



We're approaching the end of another editorial year, and many of you are anxious to find out what we have in store for the next year. Before I list the upcoming themes, let me take a moment to encourage you to look at the list with an eye toward writing an article. Does one of the themes come close to what you do in your everyday job? Perhaps you just finished a project that relates to one of the topics. If so, chances are you've learned a few tricks that would surely benefit your fellow readers.

Don't assume that just because you're comfortable with a "basic" concept, everyone else is just as comfortable. Write an article to show off what you know and everyone will benefit from your knowledge. For example, if you work with analog circuits all day long, your expertise can go a long way in helping someone whose job doesn't extend much past bits and bytes.

What's that? You've never written an article and wouldn't know where to begin? Nonsense. Bounce your ideas off us and we'll be happy to work with you to structure a well-written article in no time. What's important is that you know your stuff and you take that first step by contacting us with your ideas. You may call me at (203) 875-2199, leave me a message on the Circuit Cellar BBS ((203) 871-1988), send me a fax ((203) 872-2204), or put your ideas on paper and send them by mail (4 Park St., Vernon, CT 06066).

Now for next year's themes. I'll have some specific dates for you in the next issue, but I didn't want to put off telling you about the topics.

Home & Building Automation
Real-Time Programming
Communication
Graphics & Vi
Power Control & Conversion
Data Acquisition

Embedded Interfacing
Signal Conditioning
Signal Processing
Measurement & Control
Programmable Devices
Embedded Control

Nothing catches your eye, but you have some other ideas? That's OK, too. There is often room in each issue for an article that doesn't strictly fit that issue's theme, so we still want to hear about those ideas.

BACK TO THE PRESENT

We're hard at work judging this year's Circuit Cellar Design Contest entries and we'll have the results in the next issue. In the meantime, we have two articles in this issue written by past Design Contest winners. The MC68HC11-based two-dimensional sensor used with a geranium-planting robot won first place in the General Category last year and the Time Domain Reflectometer won first place in the Cost-Effective Category the year before.

Be sure to keep an eye out in future issues for our new "Design Contest Winner" logo that now marks an author as one of the best.

CIRCUIT CELLAR **INK**

THE COMPUTER APPLICATIONS JOURNAL

FOUNDER/EDITORIAL DIRECTOR
Steve Ciarcia

MANAGING EDITOR
Ken Davidson

ASSOCIATE EDITOR
Lisa Nadile

ENGINEERING STAFF
Jeff Bachiochi & Ed Nisley

WEST COAST EDITOR
Tom Cantrell

CONTRIBUTING EDITOR
John Dybowski

NEW PRODUCTS EDITOR
Havt Weiner

ART DIRECTOR
Lisa Ferry

STAFF RESEARCHERS:

Northeast
John Dybowski
Midwest
Jon Elson & Tim McDonough
West Coast
Frank Kuechmann

PUBLISHER
Daniel Rodrigues

PUBLISHER'S ASSISTANT
Susan McGill

CIRCULATION COORDINATOR
Rose Mansella

CIRCULATION ASSISTANT
Barbara Maleski

CIRCULATION CONSULTANT
Gregory Spitzfaden

BUSINESS MANAGER
Jeannette Walters

ADVERTISING COORDINATOR
Dan Gorsky

CIRCUIT CELLAR INK (ISSN 0896-8985) is published bimonthly by Circuit Cellar Incorporated, 4 Park Street, Suite 20, Vernon, CT 06066 (203) 875-2751. Second-class postage paid at Vernon, CT and additional offices. One-year (6 issues) subscription rates: USA and possessions \$17.95, Canada/Mexico \$21.95, all other countries \$32.95. All subscription orders payable in U.S. funds only, via international postal money order or check drawn on U.S. bank. Direct subscription orders to Circuit Cellar INK, Subscriptions, P.O. Box 3050-C, Southeastern, PA 19398 or call (215) 630-1914.

POSTMASTER: Please send address changes to Circuit Cellar INK, Circulation Dept., P.O. Box 3050-C, Southeastern, PA 19398.

Cover illustration by Robert Tinney

HAJAR ASSOCIATES NATIONAL ADVERTISING REPRESENTATIVES

NORTHEAST
Debra Andersen
(617) 769-8950
Fax: (617) 769-8982

SOUTHEAST
Christa Collins
(305) 966-3939
Fax: (305) 985-8457

WEST COAST
Barbara Jones
& Shelley Rainey
(714) 540-3554
Fax: (714) 540-7103

MID-ATLANTIC
Barbara Best
(908) 741-7744
Fax: (908) 741-6623

MIDWEST
Nanette Traetow
(706) 789-3080
Fax: (706) 789-3082

Circuit Cellar BBS—24 Hrs. 300/1200/2400 bps, 8 bits, no parity, 1 stop bit, (203) 871-1988; 9600 bps Courier HST, (203) 871-0549

All programs and schematics in Circuit Cellar INK have been carefully reviewed to ensure their performance is in accordance with the specifications described, and programs are posted on the Circuit Cellar BBS for electronic transfer by subscribers.

Circuit Cellar INK makes no warranties and assumes no responsibility or liability of any kind for errors in these programs or schematics or for the consequences of any such errors. Furthermore, because of possible variation in the quality and condition of materials and workmanship of reader-assembled projects, Circuit Cellar INK disclaims any responsibility for the safe and proper function of reader-assembled projects based upon or from plans, descriptions, or information published in Circuit Cellar INK.

Entire contents copyright © 1992 by Circuit Cellar Incorporated. All rights reserved. Reproduction of this publication in whole or in part without written consent from Circuit Cellar Inc. is prohibited.

INSIDE ISSUE 29

- 12 Planting Geraniums by Robot/Build an MC68HC11-based 2-D Sensor
by Brian Farmer
- 22 The Design of a Time Domain Reflectometer
by Brian Kenner and John Wettroth
- 34 Serial I/O on the IBM PC
by Jim Schimpf

SPECIAL SECTION Embedded Graphics & Video



Add Text Overlay to Any Video Display
by Bill Houghton



The Virtues of the Hue, Lightness, Saturation Color Model
by James R. Furlong

61

Driving Multiple VGA Monitors
by Michael Swartzendruber

2 Editor's **INK**/Ken Davidson
A Look at Next Year

6 New Product News
edited by Harv Weiner

64 Firmware Furnace/Ed Nisley
Extending Your Control: The HCS II **MCIR-Link**

74 From the Bench/Jeff Bachiochi
X-10 Interfacing with **PLIX**

80 **Silicon** Update/Tom Cantrell
I'm **18.432**—and I Like It

88 Practical Algorithms/John Dybowski
The Middle Ground/Negotiating a Keyboard Interface

95 **ConnectTime**—Excerpts from the Circuit Cellar BBS
conducted by Ken Davidson

112 Steve's Own **INK**/Steve Ciarcia
Let Me Tell You About Yourself

97 Advertiser's Index

NEW PRODUCT NEWS

Edited by Harv Weiner


UNIVERSAL DEVICE PROGRAMMER

The first device programmer in production offering a single universal PLCC socket has been announced by B&C Microsystems Inc. The new socket technology of the Proteus104 accommodates any PLCC device from 20 to 84 pins, reducing PC board traces and capacitance on the programmer header. A 48-pin ZIF socket is mounted alongside for programming 300- and 600-mil DIP devices.

The **Protéus104** features fully overvoltage- and overcurrent-protected pin drivers, full digital and analog capabilities for all pin drivers, true system self-calibration of all voltage sources and full diagnostics of all pin drivers, a built-in controller and timer with 250-ns resolution, and state machine testing with rise and skew time of less than 10 ns.

The **Protéus104** also features expandable pin driver boards, allowing upgrades to any level within its 24- to 104-pin range. An entry-level version with 24-pin drivers and a 40-pin ZIF socket is the base configuration. For production environments when programming MOS devices, gang (parallel) modules replace the universal module and provide higher throughput to meet manufacturing needs by providing eight or sixteen ZIF sockets. Also available is a memory card gang module (supporting PCMCIA 2.0 Standard) with sixteen sockets.

The programming and algorithm development environment is based on a single executable file with a built-in editor and compiler for fast software development and ease of use. Semiconductor manufacturers use a powerful Algorithm Development Language (ADEL) in the creation of new device algorithms. ADEL can also make changes to existing algorithms, when revisions are required, and can drastically reduce turn-around time for the user of the devices. An extension of ADEL allows the creation of special test algorithms independent of those officially published ones embedded in the Proteus104 system.

 

Communication with any PC, XT, or AT is via a parallel printer port, which has been optimized for the fastest and most reliable performance. The speed limitations exhibited by PC bus-based programmers are absent. The parallel port is searched by the programmer and the connection made automatically. All device library software is available through a Bulletin Board System or by floppy diskettes.

The **Protéus104** is priced from \$745 to \$4995.

B&C Microsystems, Inc.
750 N. Pastoria Ave.
Sunnyvale, CA 94086
(408) 730-5511
Fax: (408) 730-5521

#500

NEW PRODUCT NEWS

LOW-COST NETWORKED MICROCONTROLLER


The GCB11, an 8-bit networked microcontroller hardware and software package, has been announced by Coactive Aesthetics Inc. The 3" x 4" board, based on the popular Motorola MC68HC 11 F 1 chip, includes 32K of static RAM, 32K of ROM and requires only a +5-volt supply.

The GCB11 includes 20 digital I/O lines and eight channels of 8-bit A/D conversion. Communication is provided by a standard RS-232 port and an RS-485 port for a multidrop network with up to 32 nodes. Additional 485 drivers are on board for connecting a PC using the RS-232 to the RS-485 network, without the need for additional circuitry or boards. The boards can be jumper configured as either a

master or a slave on the network, and code can be downloaded and debugged across the network.

The GCB11 Package comes with a complete set of development tools and network and application libraries. The GNU C cross-compiler operates under PC-DOS and includes support for C++ and Objective C. The GNU Linker is also included. The ROM Monitor-Debugger allows program downloads in S-record format. Break points can be set and single step/step over execution is provided. Read and modify features are provided for memory, CPU registers, I/O registers, EEPROMS, and ports. An assembler and disassembler are also included.

 Master-slave packet communications software



provides rapid development of distributed control applications at various baud rates up to 115.2 kbps. Application utilities include a PWM motor driver library for transparent support of up to four DC motors, encoder feedback for speed and position control of up to three motors, input signal debounce library, and support for ADC sampling at regular intervals as a

background task Source code for all software is provided (C and assembler)

The complete GCB11 package sells for \$179.

Coactive Aesthetics, Inc.
P.O. Box #425967
San Francisco, CA 94142
(415) 626-5152
Fax: (415) 626-6320

#501

LOW-COST 8051 C PACKAGE

Franklin Software's new Engineer's Evaluation Kit, Release I, is a complete C programming package for 8051 development at the price of a standard 8051 assembler. The kit targets engineers and students who have tried earlier C products and found them either too weak and slow or too expensive. The kit allows you to experience the power and efficiency of an advanced C for 8051 software development and maintenance.

Based on technology developed for Franklin's Professional Developer's Kit, the Evaluation Kit includes a C compiler, a macro assembler, a linker, a powerful symbolic debugger-simulator, C libraries, and utilities. The kit features fast compilation and highly optimized object code. Execution speed is comparable to the best in the industry, and performance is equal to a tightly coded assembler.

The Engineer's Evaluation Kit is an entry-level companion to, and fully upgradable to, Franklin's Professional Development Kit for the 8051. Priced during introduction at \$299 plus an optional support contract, the C kit is an affordable way for engineers to discover the advantages of a complete C environment for 8051 development.

Franklin Software, Inc.
888 Saratoga Ave., #2
San Jose, CA 95129
(800) 283-4080 Ext. 896
Fax: (468) 296-8061

#502

NEW PRODUCT NEWS

PROGRAMMABLE RELAY CONTROLLER PROVIDES ANALOG AND DIGITAL SUPPORT

A family of programmable relay controllers with both analog and digital I/O capabilities for low-end control and sensor interface applications has been introduced by DIP Inc. The Pico PLC units provide digital, analog, PWM, RS-232 I/O, and an auxiliary sensor power supply. Integrated programming and debugging support allow the PPLC to be programmed using a standard data terminal or PC. No specialized programming software is required.


Extending the control language typically found in low-end PLC units with a full set of arithmetic and comparison operators, the PPLC products allow the user to intermix analog and digital operations using ladder-logic-formatted command strings. The unit may be put into a single step or display mode for interactive debugging. File transfers are supported to and from a PC programming unit using standard PC-based communications packages. EEPROM program storage provides for 256 program elements with an average execution time of 50 μ s per element.

The PPLC will replace combinations of discrete relays, counters, timers, and comparators in applications such as production monitoring, intelligent sensor interfaces, front-end preprocessing for larger programmable controllers, sequence control, and low-end motion control systems requiring peripheral interfaces. A comprehensive programming guide cuts the learning time to less than two hours.

The base unit (PPLC) provides four inputs (120 VAC), four outputs (120 VAC, 2 amps), two analog channels (0-10 VDC), a PWM output (open collector), an RS-232 serial channel, and a sensor supply voltage of 12 VDC at 200 mA. The entire unit is packaged in a 2.75" x 3" DIN-rail-compatible case with captive screw terminals. A board-level version (PPLC-BRD) extends the I/O to eight inputs, eight outputs, and four analog inputs. Both units sell for \$239 in single quantities.

DIP Industrial Products
P.O. Box #9550
Moreno Valley, CA 92552
(714) 924.1730
Fax: (714) 924-3359

#503

 

PC-BASED MOTION CONTROLLER

MicroKinetics Corporation has introduced Quickstep, a new stepper motor controller containing on-board translators and power drivers for up to three axes all on one card. It is designed for cost-sensitive applications that do not require very high stepping speeds and where the convenience of having the indexers and drivers on one card is important. The Quickstep plugs directly into any 8- or 16-bit ISA bus IBM PC or compatible, eliminating the need for an external enclosure.

Features include programmable acceleration and deceleration, automatic overtemperature protection, end-of-travel detection on all axes, two auxiliary outputs per card, and a shield-open interrupt. The Quickstep operates interactively; no uploading or downloading of programs is required. It provides keyboard control of such functions as Jog, Pause, Abort, and so forth, and drives motors requiring up to 0.9 amps at 12 VDC. A built-in timer assures motor speed consistency regardless of computer speed. The Quickstep requires only one 8-bit slot and features

programmable address selection to allow coexistence with other cards that may otherwise cause address conflicts.

The software is very easy to incorporate into any application. The included subroutine libraries support C and QuickBasic, and feature linear and circular interpolation, ramping, keyboard interactive jog, and electronic gearing.

The QuickStep motor controller sells for \$389 for a three-axes system. One-axis and two-axes systems are available for less.

MicroKinetics Corp.
1220 Kennestone Cir., Ste. J
Marietta, GA 30066
(404) 422-7845
Fax: (404) 422-7854

#504

NEW PRODUCT NEWS

HARD DRIVE ENCYCLOPEDIA


The "Micro House Encyclopedia of Hard Drives" is now available from Jensen Tools. This unique, three-volume support tool provides comprehensive technical help for the installation and upgrade or maintenance of multivendor hard drives. It contains information on hundreds of drives from Alps to Zebec, including many discontinued makes and models. The information is loose-leaf bound in three-ring binders to make page replacement and update easy, and comes with a fast, easy software version on DOS 5.25" diskettes.

Included are separate volumes on setup, controller cards, and drive settings. The information includes everything service professionals need to know about switch settings, cable locations, configuration parameters, power specifications, error codes, and interface basics for ST506/412, SCSI, ESDI, IDE, floppy, and more. Clear drawings detail switch settings and cable connections for both drives and controller cards. Also included are BIOS tables and a complete index of manufacturers with contact information.

The "Micro House Encyclopedia of Hard Drives" (Part #764B880) is featured in Jensen's Catalog Supplement D and costs \$150.

Jensen Tools, Inc.
7815 S. 46th St. Phoenix, AZ 86044 . (602) 968-6241

#505

 

The \$595 Solution to 8051 System Development

PDK51



The PDK51 is a fully integrated hardware, firmware, and software system designed to help you develop your products quickly and cost effectively.

All you need to use the PDK51 is an IBM-PC/XT/AT or compatible. We supply the rest.

PDK51 PLUS includes everything in the PDK51 plus Vers. 3 of our popular BXC518051/8052 BASIC compiler-\$800.

Call Now! 508-369-9556 or FAX 508-369-9549



Binary Technology, Inc.

P.O. Box 541 • Carlisle, MA 01741



#103

PRODUCT DEVELOPMENT

* MADE EASY! *

With **EMAC's** feature packed **Single Board Computers** and **easy to use BASIC compiler** your product/application can become a reality in no time. **EMAC's** BASIC compiler allows you to develop the software right on the **Single Board Computer**. **No more time lost linking**, downloading, or burning EPROMs. immediately see the results of a program change. Make modifications or dump memory **right** on the board. Since this BASIC is compiled and written entirely in assembly language, your programs will fly. **Full floating point, trig. functions, windowing, and networking**, all at your fingertips. But you say you need **multitasking**; how about up to **32 tasks with priority scheduling** built in. No adding libraries. And this **multitasker** is as easy to use as the BASIC language. If BASIC is not your language of choice, **EMAC** offers **Assembler, ANSI C, and Forth** - you choose. But enough about the software, **software** is nothing without a good hardware foundation with the features you need to make the job easy. Need to drive relays? Take advantage of **8 high drive digital output lines**. Have some digital input lines that are kind of noisy? **Utilize 8 optically coupled inputs**. You can also take advantage of **16 programmable I/O lines, 6 timer/counters, and 4 serial 485 ports**. But wait there's more, **a fast, 16 channel, 13 bit A/D, opt. 2 channel, 12 bit D/A, and opt. real time clock**. Add up to **512K memory, EEPROM, single supply operation** and the **EPAC 3000 G2** can handle just about anything. **The EPAC 3000 G2 is just \$389.00 Qty. 1.**

EMAC, inc.

618-529-4525

FAX: 61 8-457-0110

P.O. BOX 2042 CARBONDALE, IL 62902

#104

NEW PRODUCT NEWS


SOLID-STATE DISK SYSTEM FEATURES REMOVABLE MEMORY CARD

The MNC 1150 high-speed solid-state "disk" system features a removable PCMCIA 2.0 memory card slot for ISA and EISA computers. The MS-LXX-compatible system stores files in fast semiconductor memory rather than mechanical disks to achieve the high speed without wear. The on-board BIOS ROM allows instant-on and instant-reset capability.

The MNC 1150 offers complete PCMCIA 2.0 compatibility, which can support memory cards up to 64 megabytes

with a 16-bit data path. In addition, eight 32-pin JEDEC sockets for SRAM, EPROM, EEPROM, and flash memory chips are provided (for a total storage capacity of 72 megabytes). It has been designed with CMOS technology using a versatile register-based interface with error sensing and selectable interrupts to ensure data integrity in critical environments.

 The PCMCIA 2.0 card socket is accessible through the card bracket, so memory cards can be loaded and




unloaded while the computer system is operating. Dual-battery backup is provided for the JEDEC sockets when SRAM is used. On-board flash memory programmer and support software is provided. Power requirements are less than 1 amp at 5 volts and up to 250 mA at 12 volts (when programming flash memory).

Evaluation units are available for \$295 with zero memory.

MNC International, Inc.
2817 Anthony La. South
Minneapolis, MN 55418
(612) 788-1099
Fax: (612) 766-9365

#506

2" x 4" EMBEDDED PC

 

Microcontroller.

Microcomputer.

"Megatel Wildcards provide PC functionality in a flexible, small format."

Wildcard 88™

- CPU clock to 10 MHz
- Replaces full PC motherboard
- Co-processor and BIOS socket
- DMA, Bus, DRAM, Keyboard controllers

Multi/10

- On-board SCSI Host Adapter (supports up to 7 devices)
- Floppy Controller (1.44M, 1.2M)
- 2 RS-232. 1 Parallel. 1 RS-485 multi-protocol serial port

Vid/Mem:

- 640Kb User memory
- Video/Colour LCD controls CGA, Hercules®, IBM® Mono; (runs LCD Panels)

All Wildcards are low power single +5 volt operation.

125 Wendell Ave., Weston, Ont. M9N3K9 Fax: (416) 245-6505

For information on our representatives please contact our head office at the number below.

(416) 245-3324

Wildcard 88 and Megatel are trademark of Megatel Computer Corp. Hercules is a trademark of Hercules Corp IBM is a trademark of IBM Corp

megatel®

#105

FEATURES

12

Planting Geraniums
by Robot

22

The Design of a Time
Domain Reflectometer

34

Serial I/O on the
IBM PC



FEATURE ARTICLE

Brian Farmer

Planting Geraniums by Robot

Build an MC68HC11- based 2-D Sensor

What do you do when you need a sensor for an application nobody has thought of? Build your own. This unique sensor helps a robot prevent damage to delicate plant cuttings when handling them.



“Opposites attract,” so the saying goes. Maybe it’s true with people, but definitely not with robots and flowers. Even though the latter are about as opposite as can be, they don’t attract. Matter of fact, they are about as incompatible as you can get. Robots are inclined towards uniformity, and flowers are inherently diverse. That’s where my sensor comes in, providing a necessary ingredient for a marriage that would otherwise never work, or technically speaking, assisting a robotic system to accommodate nonuniformity.

Robotic systems aren’t anything new. They’ve been around industry for years, improving productivity and quality and doing many hazardous or uncomfortable tasks for workers. For example, the automotive and electronics industries use robots to perform repetitive and precise tasks. This form of automation is implemented in predictable and structured environments [1] with defined spatial configurations.

Agricultural robotics ventures beyond the predictable to the unpredictable environment. No formal methodology exists for designing automation systems that work with biological products that are of variable

 


Figure 1—The robot's job is to pick plant cuttings off a conveyor belt, trim leaves and the stem, and insert the cutting into a plug of peat. The sensor helps the robot compensate for the natural bend in the plant's stem.

for propagation to be used as a case study. A conveyor brings geranium cuttings into a robot work envelope. Using machine vision, the supervisory computer locates a cutting and classifies all primary plant parts. Knowledge of plant structure is used to grade and determine an appropriate processing strategy.

Control is passed to the robot and end effector controllers. The robot grasps a single cutting from the conveyor with a gripper, moves it to a pneumatic device for leaf removal (if necessary), takes it to a pneumatic cutter for stem trimming, and inserts it into a plug of propagation medium (in this case, peat). Fixtures and sensors mounted within the workspace assist the processing (Figure 1).

THE CHALLENGE

The problem the robot had early on was it damaged a significant number of cuttings. Its strictly vertical insertion motion into the plug did not regard the bend in the geranium stem. It could neither recognize different relative angles of stem growth frequently found on cuttings nor the change in stem orientation during workcell preparation.

For the reliable insertion of cuttings into plugs, the direction and degree of bend at the base of the stem had to be determined. Then, the robot arm had to make the appropriate moves to align the end of the stem with the hole in the peat plug accurately.

size, shape, color, orientation, and stress or strain relationships [2].

This scenario presents quite an inviting challenge, and who can resist one of those? Not many. Fundamental research is widely underway to establish methods for the design of cognitive machines (robots) that can autonomously or semiautonomously operate with contingencies.

handling and processing living plant materials. This accommodation of variability is contrary to a typical industrial application where an attempt is made to eliminate any inconsistencies.

Dr. Ward Simonton developed a robotic workcell for the labor-intensive preparation of geranium cuttings

THE ROBOT

Most robots are capable of repeating a preprogrammed sequence of operations; however, for robots to operate effectively in a changing or uncertain environment, the machine must be equipped with sensors. Therefore, a key activity in robotics research is examining methods for coordinating information from various sensors to control robotic actions [3].

At the Georgia Station Mechatronics Laboratory, research is investigating pragmatic techniques that allow robotic systems to accommodate the significant variability present when

Company/item	Model Name/No.	Range	Resolution
Type: LVDT			
Schlumberger Ind.	ACR/15	0.030 m	∞
Type: Ultrasonic			
Polaroid Corp.	Design Kit	0.27 m-10.7 m	0.003 m-3 m
Contaq Tech.	UDM-RMU	0.15 m-9.14m	0.0002 m
Ultrasonic Arrays	DMS-100	0.005 m-6.61 m	0.0002 m
Cosense	ML-101	0.02 m-2.74 m	0.00005 m
Type: Optoelectronic			
Banner Engineering	MP-6	3.05 m	0.013 m
Banner Engineering	SBF5 w/IR2.53S	0.025 m	∞
Frost Controls	Edge Sensing Sensor	0.025 m	0.0025 m
Keyence	2-D, LS-3033 & LS-3100	0.03 m	0.000002 m

∞ : Analog output; resolution primarily limited by measuring device.

Table 1—Numerous sensors are available that might have helped in this project, but none fit the project criteria.

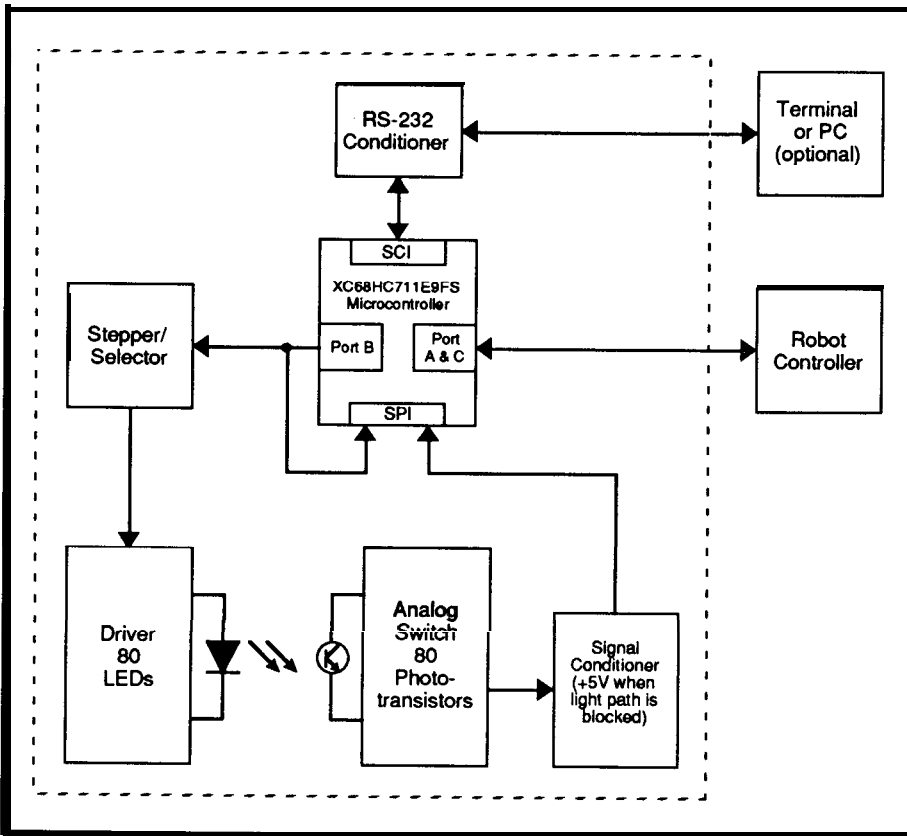



Figure 2—The external robot controller starts the whole measurement process. Results may be optionally displayed on a terminal screen.

I considered several commercially available sensors for the stem bend measurement, including LVDTs, ultrasonic transducers, and optoelectronics (refer to Table 1). With the LVDT, physical contact between its armature and the object sensed requires force, resulting in deflections and *incorrect* measurements due to the elasticity of the geranium stem.

Ultrasonics (Contaq Technology) can make noncontact measurements; however, it needs relatively precise insonification of the ultrasonic beam on a specific area of a small object. Standard collimating tubes do not normally ensure a measurement focused on a 1- to 2-mm object section. In addition, precision ultrasonic sensors are costly (Ultrasonic Arrays & Cosense).

I then turned to commercial optoelectronic sensors. Discrete measurements from an arrayed "curtain of light" would be possible with an emitter-receiver pair for binary blocked/unblocked detection. I considered an b-channel Sensor

ProControl!

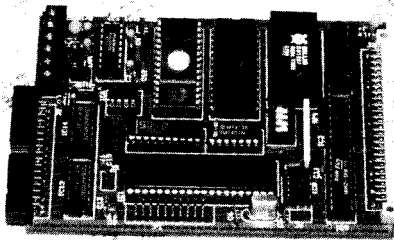

Introducing the Most Expandable 3 1/2 Board Available

MCU-31/2 from \$149.95

On Board Options Include:

- * 16 Channels 10 bit A/D - 14µs w/S/H
- * Dallas 1287 RTC
- * Flexible mem config's: RAM - 8/32KB
ROM - 8/16/32/64 KB
- * RS-232 or 485 - jumper selectable
- * Watchdog timer w/ jumper sel. reset source
- * Pre decoded external bus for very easy user interface - directly compatible with other ADS boards (see back issues of Circuit Cellar INK)

More I/O modules are available.
Call for our FREE catalogue today!

(404) 352-4788


Advanced Design Solutions

1920 Moores Mill Road
Atlanta, GA 303 18

UNIVERSAL PROGRAMMER

PAL
GAL
EPROM
EEPROM
FLASH
MICRO

87C51
87C751
87C752
PIC

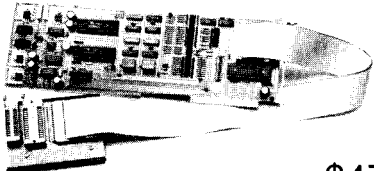

\$475.00

5ns PALs
4 MEG EPROM (8 & 16 bit)
22V10 & 26CV12 GALS


Parts added at your request

Free software updates on BBS
Powerful menu driven software

	16V8
	22V10
	26CV12
	27C040
	93C46
	XC1 736

400 MHz LOGIC ANALYZER

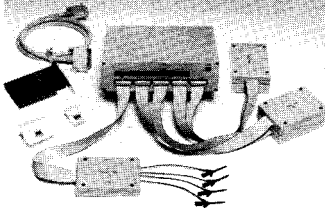up to 128 channels
up to 400 MHz
16K samples/channel
Variable threshold levels
8 External clocks
16 level triggering



\$799 - LA12100 (100 MHz,24 Ch)	Price is Complete
\$1299 - LA32200 (200 MHz,32 Ch)	Pods and Software included
\$1899 - LA32400 (400 MHz,32 Ch)	

Call (201) 808-8990

Link Computer Graphics, Inc.

369 Passaic Ave, Suite 100, Fairfield, NJ 07004 fax.: 808-8781

Multiplexer Module (Banner), but it has fairly poor resolution (5-12 mm). Other light curtain devices offered by Banner and Sick Optoelectronics simply provide presence detection or the edge measurement of a surface.

A 1-D C-shape sensor is available from Frost Controls that measures an object's size using an analog signal proportional to the area blocked, and it also can be constructed to detect position. However, this unit is 12.5 mm thick, which is the minimum displacement between measured dimensions. Due primarily to cost and complexity, I did not consider the various types of laser-based position measurement systems (Keyence, \$14,400) for this application [4].

Evidently, no commercially available position measurement device fit the needs of this application, so I developed a sensor and coupled it to an MC68HC11 microcontroller [5,6,7]. The pairing of the measuring element and the inexpensive microcontroller yielded an externally controlled programmable sensor that reported

 


Photo 1-The sensor uses pairs of LEDs and phototransistors to sense the position of a plant cutting inserted in the hole in the middle.

measurement results through a parallel/serial interface.

DESIGN CRITERIA

The primary design goal for my sensor was that it detect the direction

and magnitude of bend on a geranium cutting stem's base relative to the robot's grasp. To make this determination, the robot is directed to position geranium cuttings in a fixed location in the workcell, then to measure

FREE CALL FOR HELP

800-537-5043

PARADIGM LOCATE • PARADIGM TDREM
• PARADIGM DEBUG •

Comprehensive software development tools for all Intel 80C186 and NEC V-Series microprocessors.

- Borland C++ and Microsoft C/C++ support
- Choice of stand-alone or in-circuit emulator debugging
- Unlimited toll-free technical support
- 30day money-back guarantee

Help IS Available Call today for complete product information and embedded system application solutions. You won't be disappointed!

PARADIGM

*Proven Solutions for Embedded
C/C++ Developers*

Paradigm Systems, 3301 Country Club Road,
Suite 2214, Endwell, NV 13760

TEL: (607) 748-5966 FAX: (607) 748-5968

Trademarks are property of respective holders.

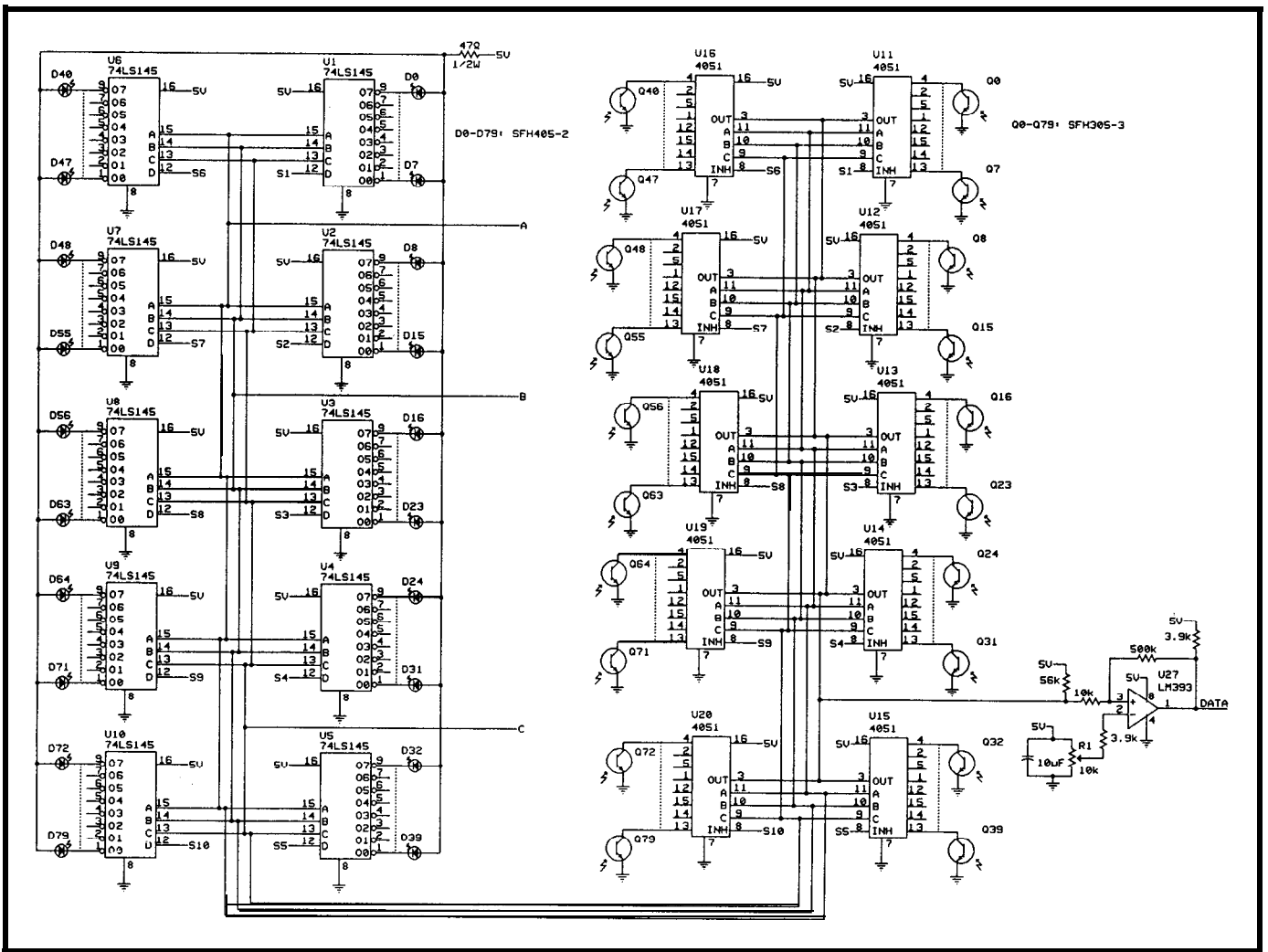


Figure 3a—The bulk of the sensor is made up of the LED/phototransistor pairs. One at a time, each LED is lit and its companion phototransistor is checked to find out if the light path is being blocked.

quickly the stem's position with a sensor. The bend of the stem is referenced from the robot's grasp point to the bottom of the stem, and the information is used when inserting the cutting into the plug. Geranium cutting stems are frequently 5-10 mm in diameter with bends of 0-0.6 radians. Before a stem has been inserted into the plug, it generally extends below the robot's fingers 15-20 mm.

Thus, the design criteria for the sensor included a 1- to 2-mm resolution, a 25-mm range in two dimensions, a 1-mm maximum displacement between measured dimensions, and a 100-ms maximum response time. Object size was assumed to be within the range of 4-12 mm. Also, I needed to keep component cost under \$500. I pursued a small, noncontact sensing method because of the infrequent need

for cleaning and the absence of any force applied to the plant stem, which could affect the measurement or disturb the cutting within the gripper.

THE SENSOR


In 1989, I developed the first sensor for this application [4]. It was based on two 10-element infrared LED emitter and phototransistor receiver pairs (Siemens LD260/BPX80)[8] physically aligned as a 25-mm x 25-mm square. Emitter-receiver pairs were not multiplexed. The entire first dimension was activated and latched, and the same was repeated for the second dimension. Both dimensions were read by a 6809 microprocessor through a parallel PLA interface.

The minimum object size measured was 5 mm in diameter or width, and average position measurement errors in the x and y dimensions were

2.4 mm and 2.0 mm, respectively (these values are within the range of expected accuracy due to the 2.5-mm resolution). Response time was 115 ms, repeatability was excellent, and the unit insertion operation increased in performance from 80% to 98% for 204 cuttings. The sensor was connected to a single-board computer, the Wintek 6809 Control Module.

While the position sensor performed well, I needed to improve resolution and range to achieve the design goal for a minimum object size measurement of 4 mm and to overcome the occasional shortcomings of the 25-mm range. The resulting project won first place in the General Category of the third annual Circuit Cellar Design Contest (see Photo 1). It uses multiplexed emitter-receiver pairs (Siemens SFH405-2/SFH305-3) with a smaller component width, a smaller

Figure 3b—An MC68HC11 processor oversees the entire measurement process. The processor's on-board memory and peripherals keep external support circuitry to an absolute minimum.

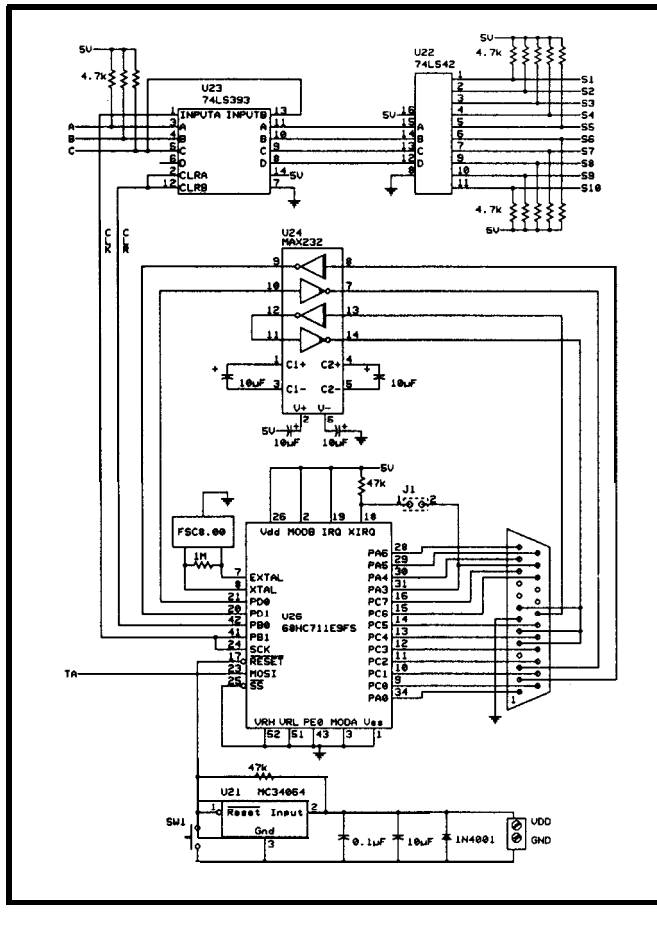

emission-acceptance angle, a larger 50-mm x 50-mm sensing area, and an MC68HC11 microcontroller unit (MCU).

The entire measurement process [refer to Figure 2) is requested by an external robot controller to the smart sensor. Once initiated, the MCU controls and reads the sensor through a three-line interface: *CLR*, *CLK*, and *DATA*. The MCU then calculates the center of the object inserted into the square based on absence of light at individual receiver elements in two dimensions. The object position is coded using 6 bits for each dimension.

Once a GO request is received, the computer sequence is as follows [refer to Figure 3 for the schematic): The MCU resets U21/U22, turning on the pair D7 and Q7 and latching their condition into the synchronous serial peripheral interface (SPI) port. It then sequences down the line along the horizontal (x) axis to D32 and Q32, storing each pair's condition in on-board RAM in single-byte groups. The scan continues in the y direction without interruption to D72 and Q72.

Notice the reverse sequencing process: 7, 6, 5, 4, 3, 2, 1, 0, 15, 14, ..., 39, 38, 37, 36, 35, 34, 33, 32, 47, 46, ..., 73, 72. This feature allows the highest to the lowest pair to match with the MSB to the LSB in on-board RAM and also follows the high-to-low order SPI format. Only one pair is energized at any one time.

If any of the beams within these 80 pairs is obstructed, the output of U26 will go high for the respective pair according to the threshold set by R1. A high or low will be loaded into the SPI port for all pairs blocked or unblocked, respectively [9]. When the MCU provides the stepping-clocking sequence for the final pair, one extra count is clocked in order to deactivate all pairs to lessen power drain during idle time. Both sets of serialized signals are read from on-board RAM, and object position is calculated and sent to the parallel/serial output.

THE SOFTWARE

My MC68HC 11 configured with pin *PE0* to ground and jumper J1 allows RS-232 sensor-to-PC software

Only \$851 for iceMASTER-PE

The world's most innovative 8051 emulator is incredibly affordable. Metalink's unique Advanced Emulation Technology (AET, patent pending) delivers the best possible emulator value for engineers, consultants and students.

AET is a revolutionary design architecture that provides more features with 75% fewer components, smaller board space and lower cost. Emulator and probe electronics are integrated in a single package only 3" by 4".

Metotink also delivers leading-edge customer service, including a 30 day money back guarantee, 10 day trial for qualified customers, rental plans and free technical support.

- ✔ Up to 40 MHz Operation
- ✔ 64K Emulation Code Memory
- ✔ 64K External Data Memory
- ✔ 128K Hardware Breakpoints
- ✔ 16K Trace Memory
- ✔ Transparent Trace (View Trace While Executing)
- ✔ Real Time & Nonintrusive
- ✔ Symbolic & Source-Level Debug
- ✔ Built-In Self-Test
- ✔ Windowed User Interface
- ✔ Serial link to Any PC
- ✔ Performance Analyzer
- ✔ Macro Cross Assembler
- ✔ Supports 8031/8032's
- ✔ Supports 8XC751/8XC752's



Call today for FREE DEMO DISK!
(800) METAICE (800) 638-2423
 MetaLink Corporation P.O. Box 1329 Chandler, Az 85244-1329
 Phone: (602) 9260797 FAX: (602)926-1198



Listing 1—A demonstration program shows what's involved in dealing with the position sensor.

* 68HC11 Register Equates

```

PORTC EQU    $1003
PORTB EQU    $1004
DDRC  EQU    $1007
DDRD  EQU    $1009
SPCR  EQU    $1028
SPSR  EQU    $1029
SPDR  EQU    $102A
    
```

* Buffalo 3.2 Eauates and Jump Table adr

```

USTACK EQU    547          (0033-0047)
WARMST EQU    $FF7C       Warm start
    
```

* RAM VARIABLES

```

                ORG    so001          Lower half of RAM

DA10 RMB    1          U10 & U20 pairs
DA9  RMB    1          U9 & U19 pairs
DA8  RMB    1          U8 & U18 pairs
DA7  RMB    1          U7 & U17 pairs
DA6  RMB    1          U6 & U16 pairs
DA5  RMB    1          U5 & U15 pairs
DA4  RMB    1          U4 & U14 pairs
DA3  RMB    1          U3 & U13 pairs
DA2  RMB    1          U2 & U12 pairs
DA1  RMB    1          U1 & U11 pairs
    
```

```

                ORG    so100          Upper half of RAM
    
```

* START

* Register Initialization

```

LDS    #USTACK    Init stack pointer
LDAB   #0         Zero B for counter
LDX    #0000A    Set X as counter
    
```

* SPI initialization

```

LDAA   #02        Prepare CLK/SCK hi
                    and CLR lo
STAA   PORTB
LDAA   #00000010
STAA   DDRD       SS*, SCK, MOSI, MISO, RxD-In, TxD-Out
LDAA   #01001100 SPI on as slave,
                    CPHA=1, CPOL=1
STAA   SPCR       Clear any
LDAA   SPSR
LDAA   SPDR       possible SPIF
    
```

• PBO is 74LS393's CLR. PB1 is 74LS393's

* CLK and SCK for SPI.

• Initiate scan

```

LDAA   #01        First falling edge
STAA   PORTB      of SCK indicates
                    start of xfer
*
CLR    PORTB      Scan initiated with
                    D7/Q7 pair activation
*
    
```


```

JSR    WAIT1      Wait a while
LDAA   #02        D7/Q7's condition
STAA   PORTB      xfered thru MOSI
    
```

(continued)

RELAY INTERFACE

PROVIDES SOFTWARE CONTROL OF RELAYS

 


CONNECTS TO RS-232

AR-16 RELAY INTERFACE\$ 69.95
 Two 8 channel relay output ports are provided for control of up to 16 relays (expandable to 126 relays using EX-16 expansion cards). Each relay output port connects to a relay card or terminal block. A variety of relay cards and relays are stocked. Call for more info. RS-422 available (distances to 4,000 feet). PS-4 port selector may be used to control satellite AR-16 interfaces. (up to 16,384 relays)
 RD-8 REED RELAY CARD (8 relays, 10 VA.) \$ 49.95
 RH-8 RELAY CARD (10 amp SPDT 277 VAC) \$ 69.95
 EX-16 RELAY EXPANSION CARD (16 channel)...\$ 59.91

ANALOG TO DIGITAL

8, 10 & 12 BIT RESOLUTION

 

CONNECTS TO RS-232

ADC-16 A/D CONVERTER (16 channel, 6 bit)...\$ 99.95
 Input temperature, voltage, amperage, pressure, energy usage, energy demand, light levels, joystick movement and a wide variety of other types of analog signals. Inputs may be expanded to 32 analog or 126 status inputs using the AD-16 or ST-32 expansion cards. 112 relays may be controlled using EX-16 expansion cards. Analog inputs may be configured for temperature input using the TE-6 temperature input conversion. RS-422 available. PS-4 port selector may be used to connect satellite ADC-16 interfaces (up to 4,096 analog inputs/16,384 status inputs and 14,336 relays). Call for info on 10 8 12 bit converters. *terminal block and cable sold separately)
 ST-32 STATUS EXPANSION CARD \$ 79.95
 *put on/off status of relays, switches, HVAC equipment, thermostats, security devices, smoke detectors and other devices including keypads and binary coded outputs.
 *Provides 32 status inputs (opto isolators sold separately).
 TE-6 TEMPERATURE INPUT CONVERSION \$ 49.95
 *includes 8 temperature sensors & terminal block.
 *Temperature range is minus 40 to 145 degrees F.
 PS-4 PORT SELECTOR (4 channels RS-422)...\$ 79.95
 *Converts an RS-232 port into 4 selectable RS-422 ports.
 TOUCH TONE DECODER and other serial interfacing products available Call for free information packet.

- FULL TECHNICAL SUPPORT...Provided over the telephone by our staff. EACH ORDER INCLUDES A FREE DISK WITH PROGRAMMING EXAMPLES IN BASIC, C AND ASSEMBLY LANGUAGE. A detailed technical reference manual is also included.
- HIGH RELIABILITY...engineered for continuous 24 hour industrial applications. All ICs socketed.
- Use with IBM and compatibles, Tandy, Apple, Mac and most other computers with RS-232 or RS-422 ports. All standard baud rates and protocols may be used (50 to 19,200 baud).

Use our 800 number to order FREE INFORMATION PACKET. Technical Information (614) 464-4470.

24 HOUR ORDER LINE (800) 842-7714
 Visa-Mastercard-American Express-COD

International & Domestic FAX (614) 464-9656
 Use for information, technical support & orders
ELECTRONIC ENERGY CONTROL, INC.
 360 South Fifth Street, Suite 604
 Columbus, Ohio 43215

w112

Listing 1-continued

```

        INCB          Record data count
* Loop through scan
LP1  CLR   PORTB     Next pair activated
     JSR   WAIT1     Wait a while
LP2  LDAA  #$02      Next pair's condition xfered
     STAA PORTB
        INCB          Record data count
     CMPB #8         One byte yet?
     BNE  LP1        No, go back for more
     CLR  PORTB     Yes, activate next pair
LP3  LDAA  SPSR      SPDR full with 1 byte?
     BPL  LP3       Keep looking for flag
     LDAA SPDR      Load into on-board RAM
     STAA 0.X
     JSR  WAIT1     Wait a while
     LDAB #$00      Reset data counter
     DEX
     CPX  #$0000    Count down
     BNE  LP2      All data in?
     LDAA #$0C      No, go back for more
     STAA SPCR     Yes, SPI off. Resets/ends
     JMP  WARMST   transfer. And...
*                               go back to Buffalo prompt ">"
* Subroutine
*
WAIT1 LDAA  #$30     Counter
WAIT1A SUBA #1      Count down
      BNE  WAIT1A   Finished?
      RTS
    
```

debugging and development with Motorola's BUFFALO program. Listing 1 provides a demonstration program used to acquire and store data.

The code is implemented in the MCU's on-board RAM as a subroutine while under control of the BUFFALO program, with a warm start back into BUFFALO after program execution occurs. Again, acquired emitter-receiver pair data is displayed on a PC's screen from on-board RAM with a BUFFALO command. The most important software detail involves the *SCK* and *DATA* timing. *SCK*(*CLK*) speed is dependent on the phototransistors' rise and fall time.

Although SPI rates as high as 2.1 megabits per second are possible, Siemens specifies the receiver with a 6 μ s maximum rise and fall time. Still yet, testing yielded 129 μ s due to the effect of coupling with the multiplexer, resulting in an optimum period of 135 μ s (7.41 kHz, which isn't one of the four selections in master mode). SPI polarity and phase were initialized for stepping on the falling edge of the clock, and data latching on the rising edge.

Calculating position requires determining the nature of the data from the arrays. Data is classified as reliable or unreliable. Unreliable data refers to noise (any pattern other than one consecutive group of blocked elements) or signal absence (all elements unblocked or all elements blocked), with appropriate codes transmitted for each type of condition. Reliable data is processed by a simple algorithm to locate the object center.

As I noted earlier, the microcontroller uses six parallel bits per dimension to code the calculated object position within the array of the sensor. In addition, raw position, position codes, and error codes are sent to the optional terminal for user verification if desired. The 26-pin dual-row header on the circuit board provides RS-232 interfacing when a 25-to-9-pin adapter is used. Nine of the 25 pins are used to avoid circuit contention with the parallel output on the same header.

Eventually I will want robustness: the ability to handle unreliable data. I

NBS-10 Interface Card provides gateway to network

PC Master

Embedded controllers on a multidrop network

slave controller 1: 8051

slave controller 2: 68HC11

slave controller 3: Z180

Distributed Control and Data Acquisition

Connectivity is implemented at low cost with a network designed by **CIMETRICS TECHNOLOGY**.

Our hardware/software solution includes:
 Microcontroller code, PC/XT/AT interface card, NSP protocol, and application development software toolkit.

CIMETRICS TECHNOLOGY
the network solution for embedded controllers

120 West State Street, Ithaca, New York, 14850
 Phone: 607-273-5715 FAX: 607-273-5712

x113

hope to implement a form of fuzzy logic in the future to deal with the tendency of the data rather than rigid rules of traditional logic [10].

PERFORMANCE OF THE SENSOR

I conducted several tests to determine operational limits of accuracy, repeatability, and speed. Tests showed a minimum of 0.22 mm for object size measurements. Average position measurement errors in the x and y dimensions were 0.07 mm and 0 mm, respectively. Measurement time was 11 ms (demonstration program). Finally, the sensor had excellent repeatability and a greatly reduced power drain (including a single +5-volt supply) compared to the first circuit.

The component cost was \$476.76. An insertion performance of over 98% of cuttings is projected. The sensor has added some other benefits as well. It can detect the proper grasp of a cutting by the robot before attempting insertion into the plug. Also, it has the capability to abort a particular cutting cycle if no object is detected. ☐

REFERENCES

1. W. L. Whittaker, G. Turkiyya, M. Herbert, "An architecture and two cases in range-based modeling and planning," IEEE, 1987.
2. W. Simonton, "Automatic plant handling and processing in a robotic workcell," *Transactions of the ASAE*, 1990.
3. W. Simonton, "Issues in robotic system design for transplant production systems," *International Symposium on Transplant production Systems*, Yokohama, Japan, 1992.
4. W. Simonton, B. Farmer, "Sensor for two-dimensional position measurement of small objects," *Transactions of the ASAE*, 1992.
5. S. Ciarcia, "Why microcontrollers?," *BYTE*, August 1988.
6. S. Ciarcia, B. Brown, "Using the Motorola MC68HC11," *Circuit Cellar INK*, Issue 18, December/January 1991.
7. *M68HC11 Reference Manual*, Motorola Inc., 1989.
8. *Optoelectronics Data Book*, Siemens Components, Optoelectronics Division, 1990.
9. S. Ciarcia, "Let your fingers do the talking," August 1978, *BYTE*.
10. M. AbdelRahman, "Artificial Intelligence expands sensor applications," *Electrical Construction & Maintenance*, December 1991.

Brian Farmer was formerly an Electronics Engineer with the University of Georgia Experiment Station and occasionally does consulting through Power Tech Inc. He is now a full-time student in the University of Arkansas's Electrical Engineering Graduate program with a teaching assistantship.

My thanks to the clear thinking and wise supervision of Dr. Ward Simonton.


IRS

- 401 Very Useful
- 402 Moderately Useful
- 403 Not Useful

TW523 Power Line Interface


Developers Kit

 Interface Your Computer To Transmit And Receive X-10 Codes Over Your AC Power Line. Two-Way Communication. Real Time Environment Control.



Kit Includes TW523, Cable, Interface Connector (S/P) Documentation. Source Code Supplied in "C", Pascal, BASIC or Run Time. Disks 5.25in & 3.5in Format.


\$75.00

 

Baran-Harper Group Inc.

Voice (416) 294-6473 BBS (416) 471-6776
Fax (416) 471-3730

 The Quick Way into Embedded Software Development



Integrated
Development
Environment
For (Almost)
Any
Language

IDEAL brings together all of the tools used to develop software for Single Board Computers (SBC) and blends them into a menu-driven windowed environment that speeds your development process.

- Automates the Compile-Assemble-Link-Download Cycle
- Works with any Compiler, Assembler, Linker, etc.
- Use the built-in Editor or link to your own Editor, it's easy
- Great for BASIC and FORTH interpreters too
- Interrupt driven serial communications to the SBC
- Swaps memory to make room for the largest tools
- Resizable, Zoomable Windows for Editing, Browsing and Target Communications
- Fully integrated mouse and keyboard control
- In use for 2 years at Major Universities and Corporations

Requires PC/XT/AT w/512K 30 day Money-Back Guarantee
Demo Available on BBS



creative applications engineering, inc.
Phone (415) 494-2363
CompuServe: 74 156,1207
BIX: ecaryer

F.O. Box 9524, Stanford, CA 94309 BBS (415) 494-8463



FEATURE ARTICLE

Brian Kenner
& John Wettroth

The Design of a Time Domain Reflectometer

As anyone who's tried to track down an elusive network cabling problem knows, improper termination and bad cables are common culprits. Let this time domain reflectometer make your life a little bit easier.



A few years ago, a friend of mine needed a portable network cable tester. He does LAN management and found that cable problems were the cause of a very large number of network instabilities. I wasn't surprised, having also managed several large networks at one point in my life. I had grown weary of having a system fail whenever someone decided to rearrange the office and inadvertently disconnected the network while moving a computer.

Certainly, no replacement exists for building networks with some level of *fault tolerance*, but doing so is not always physically possible or economically viable. The type of cable tester my friend suggested was not going to solve network errors originating from the "designer office worker" anyway.

Nevertheless, my friend reasoned that if a truly fault-tolerant network wasn't possible, providing the means to quickly locate the cable fault was the next best thing. He proposed I build a network cable tester: a Time Domain Reflectometer (TDR).

Our portable TDR is based on the Intel 87C51 microcontroller. We designed it primarily to measure the

length and termination impedance of coaxial cables commonly used in computer networks, such as Ethernet, Arcnet, and so forth.

The TDR uses time domain reflectometry techniques to measure length and calculates the actual termination impedance based on the amplitude of the reflected waveform. It has a measurement range of approximately 1800 feet and handles 50- and 75-ohm characteristic impedance cables (primarily RG-58 and RG-59 used in *thin-wire* networks).

The hardware combines an 87C51 microcontroller with a 4-line 20-character LCD display, an infrared three-key touch-screen interface, a low-power PAL, a dual 8-bit DAC, a very high-speed comparator, and a handful of digital and analog "jelly-beans" to bring it all together.

The software consists of approximately 3K of 8051 assembly language, which includes a flexible menu system, a custom integer math package, and the actual measurement code. A 9-volt battery powers the unit, which features automatic shutoff, and it is packaged in a 2" x 4" x 6" plastic enclosure. We also kept the bill of materials below \$200.

THEORY OF TDRS

The TDR capitalizes on the traveling waveform's characteristic of reflecting some portion of its power as it passes through the interface of two dissimilar materials. A detailed understanding of why these reflections occur requires more space than I have. However, I will cover the theory necessary to build the TDR, which centers on how electromagnetic waves propagate down a transmission line.

 


Figure 1—Some vectors and differential calculus help show how the time domain reflectometer works.

Transmission lines result from the interaction of wire sections that make up any circuit. In most cases, the interaction between the wire in the signal and return paths is insignificant relative to the effect of the physical components that form the system. However, in the case of network cabling, the distributed reactance (both inductive and capacitive) is substantial with respect to the data rates involved. Figure 1 and some differential calculus help show how these reactive elements sum.

In an infinitesimally small element of the transmission line, dz , voltage and current are defined by

$$V - (V + dV) = -dV = (Ldz) \left(\frac{\partial I}{\partial t} \right)$$

and

$$-dI = (Cdz) \left(\frac{\partial V}{\partial t} \right)$$

where L is the series inductance and C is the parallel capacitance of the cable conductors measured in inductance and capacitance per unit foot. If I assume a **lossless** transmission line, I can combine the above equations to form a pair of linear differential equations representing the variation of voltage and current in the conductors at position z . These equations are

$$-\left(\frac{\partial V}{\partial z} \right) - L \left(\frac{\partial I}{\partial t} \right)$$

$$-\left(\frac{\partial I}{\partial z} \right) - C \left(\frac{\partial V}{\partial t} \right)$$

$$\frac{\partial^2 V}{\partial z^2} - \frac{\partial}{\partial z} \left(L \frac{\partial I}{\partial t} \right) - \frac{\partial}{\partial t} \left(L \frac{\partial I}{\partial z} \right) - LC \frac{\partial^2 V}{\partial t^2}$$

They have a solution of

$$V = F_1(z_0 - vt) + F_2(z_0 + vt)$$

where v and z_0 must be

$$v = \frac{1}{\sqrt{LC}}$$

$$z_0 = \sqrt{\frac{L}{C}}$$

z_0 and v play very important roles in the TDR's capability to make its measurements. z_0 is the characteristic impedance of the cable and is used to determine the magnitude of the waveform (and possibly phase) reflected at the interface of the two conductors. The parameter v , defined as

 


Photo 1-The time domain reflectometer uses a 4-line by 20-character display for all operator input and output. Soft keys and touch screen circuitry make for a very flexible interface.

$$v = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{\epsilon\mu}}$$

is the velocity of the electromagnetic wave in the cable and is used to compute the physical distance to the discontinuity.

In a vacuum, the dielectric constant (ϵ) and permeability (μ) are equal to 8.854×10^{-12} F/m and $4\pi \times 10^{-7}$ H/m, respectively, so the speed of propagation becomes c , or the speed of light.

Defining the equations for capacitance and inductance per unit length of the two most commonly used types of cable is also helpful. For coaxial conductors

$$C = \frac{2\pi\epsilon}{\ln\left(\frac{b}{a}\right)}, \quad L = \frac{\mu \ln\left(\frac{b}{a}\right)}{2\pi}$$

For parallel conductors

$$C = \frac{\pi\epsilon}{\ln\left(\frac{2d}{a}\right)}, \quad L = \frac{\mu \ln\left(\frac{b}{a}\right)}{2\pi}$$

Using these equations, I can define Z_0 in terms of the physical and electrical properties of the cable: parameter a , the diameter of the inner conductor; b , the diameter of the outer conductor in coaxial cables; and d , the distance between conductors in parallel wire cables. The equation for a coaxial conductor is

$$Z_0 = \frac{1}{2\pi} \left(\frac{\mu}{\epsilon} \right)^{1/2} \ln\left(\frac{b}{a}\right)$$

and for a parallel conductor is

$$Z_0 = \frac{1}{\pi} \left(\frac{\mu}{\epsilon} \right)^{1/2} \ln\left(\frac{2d}{a}\right)$$

The TDR makes its basic measurement by injecting a pulse into the cable and subsequently measuring the amplitude and phase of any reflected pulse. The reflected pulse's amplitude and phase indicate the impedance of the new material. The time elapsed between pulse injection and the detection of the return pulse is then used to compute the round-trip distance to the cable discontinuity.

What may be obvious at this point is if the pulse is not reflected, no discontinuity exists in the cable. The mystery is why any portion of the wave reflects at all, and upon being reflected, why the electromagnetic wave may undergo a phase change.

Though the TDR's injected pulse is by no means sinusoidal, Fourier analysis shows it is composed of sinusoids. For the following discussion, it is easier to assume the traveling wave is purely sinusoidal and of some particular frequency. If the transmission line is terminated and assumed to be lossless, then the load,

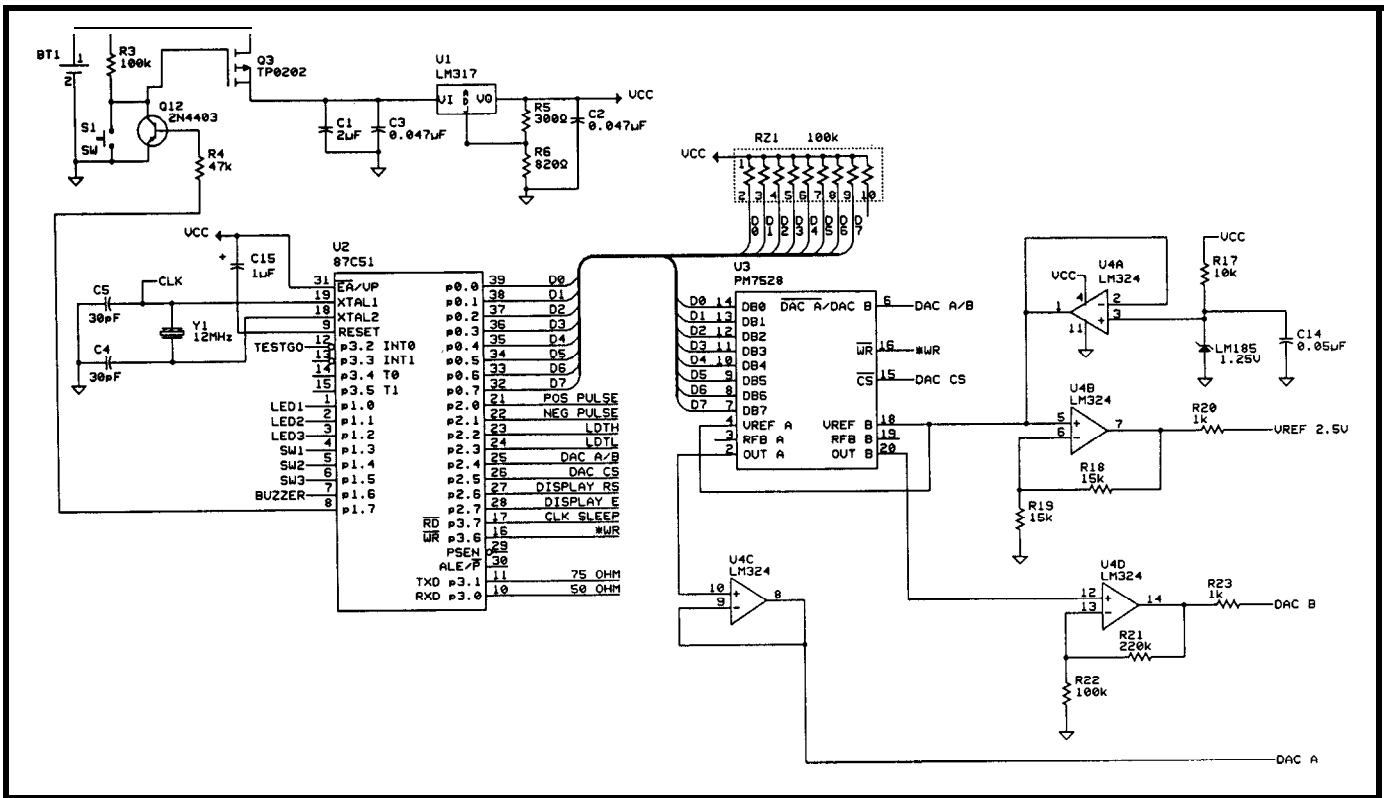


Figure 2-An 87C51 nms the TDR. A 2-channel DAC is used b control the LCD display contrast and to create a variable offset for the measurement circuits. The power control circuitry automatically powers the system up at the press of a button and powers if down after a fixed period of inactivity.

Z_L must also equal V/I of the incident waveform. Thus, using the equation developed for V and I , the following relationships can be established:

$$V = Ae^{j\omega t - z/v} + A'e^{j\omega t - z/v}$$

$$Z_L I = Ae^{j\omega t - z/v} - A'e^{j\omega t - z/v}$$

Don't let the complex exponentials distract you. They are, in conjunction with the parameter A , part of the characterization of the general sinusoid and will be divided out. What remains is an equation relating the complex amplitude of the incident waveform to the load impedance, Z_L , and the characteristic impedance, Z_0 .

$$\left(\frac{V}{Z_0}\right)_{z=0} = \frac{Z_L}{Z_0} = \frac{Ae^{j\omega t - z/v} + A'e^{j\omega t - z/v}}{Ae^{j\omega t - z/v} - A'e^{j\omega t - z/v}}$$

$$= \frac{(A + A')}{(A - A')}$$

$$\frac{A'}{A} = \frac{(Z_L - Z_0)}{(Z_L + Z_0)}$$

This equation is the definitive relationship for TDR. With it, you can anticipate the reflection of any

waveform with predictable results. In the limit, with Z_0 equal to zero, A' equals $-A$ and shows that the incident waveform will be entirely reflected with a 180° phase change. When the load impedance is infinite, A' equals A , and the entire waveform reflects, but this time without a phase change.

As long as the load impedance is purely resistive and does not equal the characteristic impedance exactly, the reflected wave will have at least some portion of its power reflected, with either a 0° or a 180° phase change. Not surprisingly, you will observe a phase change other than 0° or 180° when the load is reactive.

An understanding of how power dissipates in the transmission line explains why a portion of the wave reflects at all.

$$\text{Power} = IV = \frac{V^2}{Z_0} = v \left(\frac{1}{2} LI^2 + \frac{1}{2} CV^2 \right)$$

Because the equations developed in the preceding paragraphs are based upon a lossless transmission line, power dissipation only occurs by transmitting power from one section of the cable to the following section. It

does not occur by the conversion of electrical energy to heat energy as you might expect in resistive circuits.

In fact, as I have shown, although Z_0 is real, P represents the magnitude of power passing any point on the transmission line during a given instant. As long as each subsequent section of the transmission line has the impedance Z_0 , the waveform continues to travel down the transmission line undisturbed; each section passes energy to subsequent sections.

The specific V^2/Z_0 changes upon reaching a section of cable or termination resistance that does not have the equivalent characteristic impedance. Some portion of the power must be either returned or reflected because a diminished or increased magnitude of power is transmitted to the new load. The 0° or 180° phase is a consequence of the increase or decrease in power transmitted at that point.

Real-life transmission lines do not behave strictly this way. At some point, the cable length becomes significant because the assumption that cables are lossless is not valid. In real cables, both the conductor and the

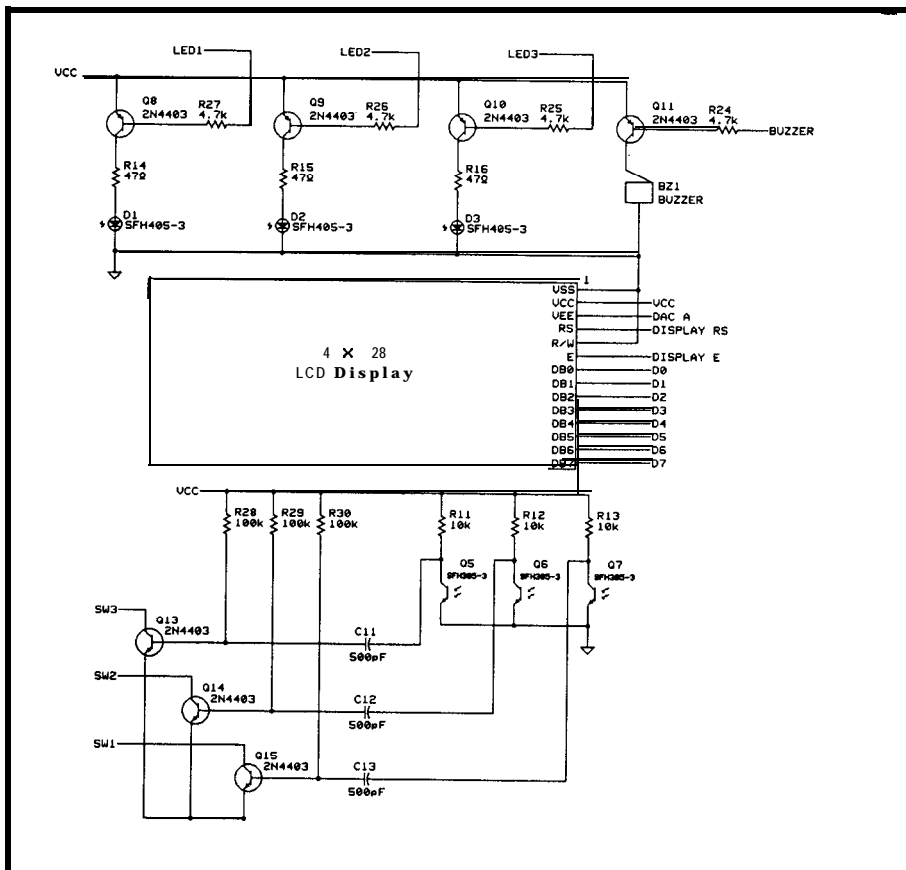


Figure 3—User input to the TDR is through a touch screen interface. Three pairs of LEDs and phototransistors detect a finger pointing at one of three choices displayed on the LCD display.

dielectrics have resistance. This resistance not only affects the transmitted wave amplitude, but also influences the phase relationships of the frequency components in the transmitted waveform. The TDR is forced to consider this fact when computing termination resistance. Ultimately, this real-life effect limits the length of cable the TDR can test.

HUMAN INTERFACE

We imagined how the TDR would be used and attempted to build the instrument around those purposes. The TDR had to have a simple interface and a small package. Simply stated, the number of basic actions required to operate any instrument or appliance should be as few as possible. Because nearly anyone can memorize three or four operations to perform some function, we restricted the number of keys on the TDR to three and let the software handle the rest.

With the above goals in mind, we decided to make a touch screen interface. That would allow us to

present three "buttons" on the display and let the operator select one with the point of a finger. It also allows us to add features later by simply changing the firmware.

For our design, the best combination of keys was two for moving through menus and one for selecting an option. We ensured that any function or operation in the TDR would be compatible with the three-key interface, which unfortunately meant we would have to anticipate any parameter that eventual users may wish to enter and incorporate into the menu.

CABLE TYPES

Computer networks can and do use a variety of cable types. Most of them fall into two categories: coaxial and twisted pair. Each category has its own characteristic impedance. The problem is TDR has its own intrinsic characteristic impedance, which may or may not match the cable under test, so there may be reflections generated at the interface of the TDR and the cable under test.

Rejecting this reflection with software is possible, but the noise margin will be affected. Unfortunately, some portion of the waveform's power also will return before it reaches the cable fault, further reducing the instrument's usable range. Initially, we thought this problem meant a reduction in supported cable types because some form of internal termination was required to perform the measurement. In the end, we decided to cover the two most common types of coaxial cables with a very small relay, which toggles the TDR's internal termination resistance between 50 and 75 ohms.

HARDWARE DESIGN

The electronics for the system consist of two major parts: microcontroller and measurement. The microcontroller electronics include the LCD display, DAC, and IR touch-screen circuits. The measurement electronics consist of a high-speed comparator, a low-power latching relay, and a discrete cable interface circuit.

The microcontroller is an 87C51 operating at 12 MHz (see Figure 2). The microcontroller's oscillator also clocks the measurement PAL, U9. The clock to the PAL is enabled and disabled to save power when actual measurements are not in progress.

The three data inputs for the PAL, the LCD display, and dual DAC data inputs populate the microprocessor's port 0. The DAC is the only device actually addressed as a memory device (i.e., using the MOVX instruction).

A single 9-volt battery powers the TDR. Automatic power down is accomplished with the aid of PMOS FET Q3 and NPN transistor Q12.

When the operator presses the "on" switch S1, the gate of Q3 is pulled low, applying power to the LM317 and subsequently the microcontroller. At power-up, all processor port pins go high including P1.7, which keeps Q3 and Q12 turned on. To power down, the processor simply drops P1.7. The sum of the leakages of Q3 and Q12, which are extremely low and comparable to the self-discharge rate of the 9-volt battery, equals the amount of standby current when the system is off.

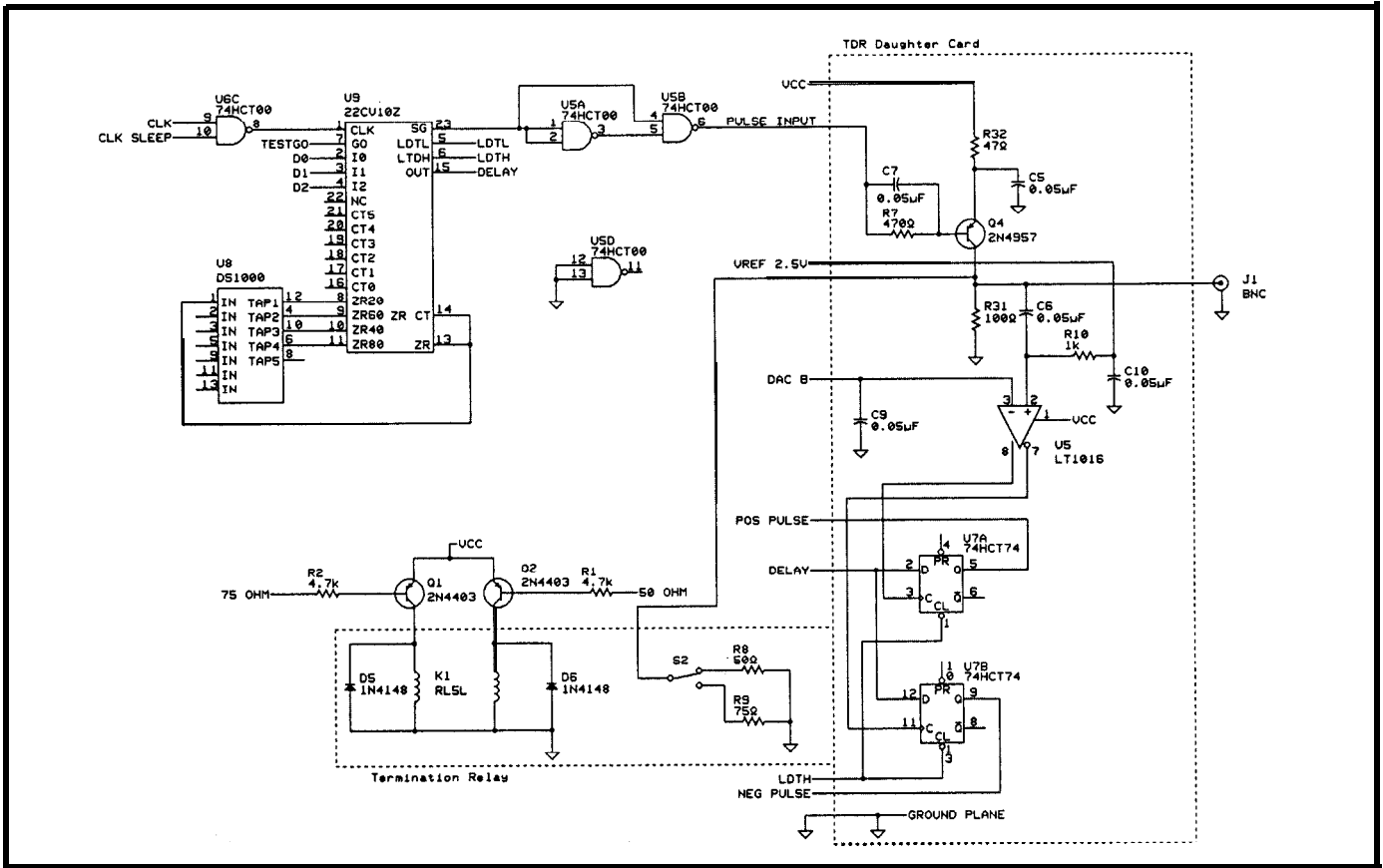


Figure 4—All the noise-critical circuitry is wired on a daughterboard with a ground plane. The 22CV10Z PAL chip eliminates a handful of circuitry.

BDT™ BASIC Developers Tool

ATTENTION: BASIC-52, BASIC-180 and BASIC-11 DEVELOPERS

Finally, an advanced development environment for BASIC single-board computers. **BDT** combines all the tools you need—including **Editor, Compiler, Debugger** and **Terminal** emulator in a powerful, fast, easy-to-use, and totally integrated package.

```

Line 130 Col 1 Insert indent * SIMULING BDT
'If not BDT on 65 deg. line, use the Bresenham algorithm
First, determine the lines major and minor axis
and assign the appropriate values ex: dmj/dmx or dmj/dmy'

IF abs(dx) <= abs(dy) THEN BEGIN 'x is major axis'
  dmj=dz 'major axis distance'
  dmx=j:dmj:dmj 'major/minor axis dx address'
  abs(dx) <= abs(dy) 'the values of major/minor axis distance'
  dir=j:dmj:dmj:dmj 'major/minor axis direction flags'
  DM
ELSE BEGIN 'y is major axis'
  dmj=dz
  dmy=j:dmj:dmj
  abs(dx) <= abs(dy)
  dir=j:dmj:dmj:dmj
  DM
'Finally, the Bresenham algorithm draws the line'

c1=c1+abs(dx) 'initialize error accumulator'
FOR i=0 TO dmj STEP dir:mj
  IF abs(c1) <= abs(dx) THEN BEGIN 'if x is major axis'

```

Editor

- Configurable keystrokes and colors. Memory resident text (FASTI)
- Block move/copy/delete/read/write. Find & replace • Auto-indent
- Compiler
- Structured programs: DO/UNTIL, WHILE/WEND, BEGIN/END. No line numbers
- Up to 20-character variable and label names. Subroutine LOCAL variables
- Five types of comments (including multiline) stripped during download

Debugger

- UP to 1000 BREAK/PASS points. Execution PROFILE. Up to 40 WATCH variables
- Integer variables WATCHable as DEC/HEX/BIN. A,,, or partial, array WATCH

Terminal

- Editor, file, and compile buffer download to SBC • File capture from SBC
- Host PC Requirements
- 5.12K. One disk drive. One serial port. Mono, C/E/V/GA. DOS 3.x-5.0

Individual versions are available for BASIC-52 (BDT52), BASIC-180 (BDT180) and BASIC-11 (BDT11) SBCs @ \$199. **SPECIAL OFFER—“BDT-PAK”** combines all three versions @ \$489 for a savings of over \$100. Order today—offer expires soon...

MICRO FUTURE 40944 Coscodo Place . Fremont, California 94539
(510) 657-0264 . FAX (510) 657-5441 . BBS (510) 657-5442

4 Configurations Available

The Heart of the Matter...

RTXC™

Real-Time Multitasking Executive

• HITACHI 6303 . INTEL 80x88/x86, 80x96, 80x51
 • MOTOROLA 680x0, 683xx, 68HC11, 68HC16
 • INMOS T400, T800 . ZILOG Z80/Z180

- Preemptive Scheduling
- Fixed or Dynamic Priorities
- Timeout on some services
- Configurable and ROMable
- Intertask Communications
 - Messages
 - Queues
 - Semaphores
- Memory Management
- Resource Manager
- Over 50 Executive Services Available
- System Level Debugging Utility
- System Generation Utility
- 450 Page User Manual

- Written in C
- Source Code Included
- No Royalties
- Technical Support
- Broad C Compiler Support
- Sensible License Agreement
- Most Popular C Compilers supported

Ask about ASSIST™
Our new PC Development Package Combination

One Time License Fee From \$995
 Discounts for Multiple Licenses/Ports
The only real-time kernel you'll ever need™

A.T. BARRETT & ASSOCIATES, INC.
 11501 Chimney Rock, Houston, TX 77035
 FAX 713/728-1049
 Phone 800/525-4302 or 713/728-9688

FREE DEMO AVAILABLE

THE LCD

The LCD display is a standard 4-line by 20-character module [Figure 3]. The menu program uses the top two lines to display measurement data and menu information, and it uses the last two lines to display soft-key data for the touch-screen keyboard.

DAC A of U3 provides LCD contrast control VEE through op-amp follower U4c. The DAC voltage reference is provided by D4, a micropower 1.25volt bandgap reference. The reference is buffered by op-amp follower U4a and also provides a 2.5volt reference to the measurement circuit through amplifier U4b.

TOUCH-SCREEN LED CIRCUITRY

An infrared light across the face of the display, in a configuration where the operator's fingers interrupt it, implements the touch-screen display.

D1, D2, and D3 provide the IR light to phototransistors Q3, Q4, and Q5, respectively. Transistors Q8 through Q10 drive the LEDs at 70 mA for brief periods of time. P1.0, P1.1, and P1.2 provide the control signals through resistors R25, R26, and R27.

The phototransistors operate at low gains using small collector loads of 1 k to minimize ambient light swamping further. The transistors are AC coupled to transistor switches Q14 through Q15 by a differentiating network consisting of C13 and R28 through C11 and R30, respectively. These transistors provide microcontroller input P1.3, P1.4, and P1.5.

When an LED is turned on, its respective phototransistor conducts about 2 mA with a fast falling edge. Differentiating capacitors pass this fast edge with a time constant of 50 μ s. The pulse turns off the NPN transistor, producing a 50- μ s high on the processor's input for each falling edge on its LED. The software samples the phototransistor outputs briefly after it turns on an LED. If it sees a high input, then the light from the LED must be reaching the phototransistor, so a "key" must not be pressed.

MEASUREMENT ELECTRONICS

The maximum resolution in termination resistance is limited by

Listing 1 -- The TDR PAL is defined using a high-level description to let the compiler make better use of the part and to reduce the number of outputs.

```

/*****
/*
/* TIME DOMAIN REFLECTOMETER PAL
/*
/* It does the following:
/* 6 bit programmable down ctr. ldt in two 1/2's, ldth,ldtl
/* zr_ct goes high at zero
/* synchronizes go output falling edge of go in and clock
/* multiplexes dallas delay generator on inputs
/*
*****/

TDR (in clk,i2..0,ldtl,ldth,go,zr,zr20,zr40,zr60,zr80; /* inputs */
    out dlout;
    reg ct5..0 sg,zr_ct) /* registered outs */

/* define relationships- begin */
* _____ */

/* define groups */
/* ----- */
group i[i2..0];
group ct[ct5..0];
group mux[i2..0];
group d[zr80,zr60,zr40,zr20,zr];

/* clocks */
/* _____ */
sg.ck = clk;
zr_ct.ck = clk;
ct[].ck = clk;

/* do output enables */
/* ----- */
sg.oe = 1;
zr_ct.oe = 1;
dlout.oe = 1;
ct5.oe = 1;
ct4.oe = 1;
ct3.oe = 1;
ct2.oe = 1;
ct1.oe = 1;
ct0.oe = 1;

/* have to do this to get feedback */
/* do aclr and spre */
/* ----- */
sg.aclr = 0;
zr_ct.aclr = 0;
sg.pre = 0;
zr_ct.pre = 0;
ct[].aclr = 0;
ct[].pre = 0;

/* define mux action, load low and high and count */
/* ----- */
dlout = d[mux[]]; /* mux high level construct */
if (go==1){ /* if go high wait for load or hang */
    if (ldtl==1 && ldth==1){ /* if both loads high just stay here */
        sg = 0; /* sync go = 0. no pulse */
        zr_ct = 0; /* zr_ct=0, input to delay line */
        ct[] = ct[]; /* don't decrement counter- hang */
    }
    else { /* if one or more loads are low then */
        if (ldtl==0){ /* if load low. load in to low ct */

```

(continued)

the minimum signal-to-noise ratio, so critical portions of the measurement circuits are located on a small, very tightly hand-wired daughter board (see Figure 4) with a ground plane. These key circuits include the termination relay, the comparator, and the D flip-flop. The logic board contains the less-critical portions of the measurement circuit.

The heart of the measurement circuit is U9, a low-power, high-speed PAL device (ICT **22CV10Z**). It reduces the chip count by as much as four MSI logic devices and makes fitting all the electronics into a small package possible. This device orchestrates all the high-speed operations and timing done by the system. Listing 1 presents the PAL's defining code.

Outputting a time delay to the PAL begins a measurement. The PAL includes a 6-bit presetable down counter, an B-to-1 digital multiplexer, and a synchronizer circuit. Only five of the eight multiplexer inputs are used, and they are connected to the delay line chip U8.

The input to the delay line is the zero output of the 6-bit counter (**ZR_CT**). The counter is clocked at 12 MHz (83.3-ns period) and followed by a selectable multiplexer delay of 0, 20, 40, 60, or 80 ns to produce the delay output. The PAL operates through three data inputs that have multiple uses, depending on the state of three other inputs: load high (**LDTH**), load low (**LDTL**), and Go (**GO**).

When **LDTH** goes low, the PAL preloads the three high bits of the counter. **LDTL** performs a similar function for the three low bits of the counter. The static value left on the three inputs selects the multiplexer routing. Note that the zero delay output (**ZR_CT**) comes out of the PAL and back into the PAL multiplexer zero delay input (**ZR**). Logically, the PAL could do this routing internally, but having it do so would skew the propagation delay for the zero delay output.

The microprocessor brings the PAL **GO** input low to begin a measurement. This signal is synchronized in the PAL with the next clock edge to output a synchronous **GO** output (**SG**).

Listing 1—continued

```

ct5 = ct5;          /* leave high bits alone */
ct4 = ct4;
ct3 = ct3;
ct2 = i2;
ct1 = i1;
ct0 = i0;
}
if (ldth==0) {     /* if load high. load in to high ct */
ct5 = i2;          /* leave high bits alone */
ct4 = i1;
ct3 = i0;
ct2 = ct2;
ct1 = ct1;
ct0 = ct0;
}
}
else {             /* go is low- let's jam */
if (ct[>0]) {     /* if still count loop decrementing */
sg = 1;           /* put out sync go on first clock */
ct[ ]--;          /* decrement counter */
if (ct[ ]==1)    /* on last count bring zr_ct high */
zr_ct = 1;
else
zr_ct = 0;       /* else zr_ct is low- to delay line */
}
else {
if (go==0){      /* if at zero then keep zr_ct 1 */
zr_ct = 1;       /* leave count and sg at 1 */
ct[ ] = ct[ ];
sg = 1;
}
}
}
/* put part definition */
/* ----- */
putpart("P22CV10Z","tdr",
/*      1 2 3 4 5 6 7 8 9 10 11 12 */
clk,i0,i1,i2,ldtl,ldth,go,zr20,zr60,zr40,zr80,GND,
/*      13 14 15 16 17 18 19 20 21 22 23 24 */
zr,zr_ct,d1out.ct0.ct1.ct2.ct3.ct4.ct5, _, sg,VCC)

/* end of definitions */
/* end of module */
}

```

The rising edge of **SG** is applied to the glitch monostable circuit formed by NAND gates **U6a** and **U6b**. The output of this circuit goes low for about 8 ns on the rising edge of **SG**. This pulse drives the base of **Q4**.

When **Q4's** base is pulled low, it generates the very fast pulse at the BNC test cable output. **C6** fixes the high-level output impedance of the TDR at a very low value. Once **Q4** is turned off, the setting of latching relay **K1** and the parallel combination of **R8**, **R9**, and **R3** determine the impedance

the line sees. This impedance is either 50 ohms or 75 ohms depending on the setting of **K1**.

Note that **K1** is a permanent-magnet latching relay briefly pulsed by the microprocessor to change state through **Q1** and **Q2**, although it draws no quiescent power.

The output connector is also capacitively coupled to **U5**, an **LT1016** [a very high-speed comparator]. This device has a propagation delay of 7 ns and specifically operates on a single supply. The comparator does have a

limited common mode range of 1.25–3.5 volts when run on 5 volts.

To push the signal into this range, the positive input is biased to 2.5 volts by doubling the voltage reference, which brings it to the approximate center of the common mode range. DAC B and amplifier U4d provide the negative input to the comparator. The range of this input is 0–3.95 volts. The DAC resolution is about 16 mV for measuring the height of the returned waveform.

The comparator has complementary outputs connected to the clock inputs of U7a and U7b. Two flip-flops eliminate the pulse-width uncertainty associated with measuring negative returning pulses. The microprocessor samples the flip-flops' outputs at the end of a trial measurement at P2.0 and P2.1.

The PAL's *LDTL* input clears the flip-flops at the beginning of a trial measurement. They are set after the return of a pulse if the D input provided by *DL_OUT* is present before the comparator senses the pulse.

The measurement circuit operates by injecting an extremely brief pulse [about 10 ns] onto the cable under test. This pulse travels down the cable and reflects from any discontinuities (changes in impedance) in the cable. These reflections return to the TDR and are captured by a very fast comparator, which clocks a D flip-flop.

A precisely delayed signal derived from the original output provides the D flip-flop's input. The PAL generates the delay, and a microprocessor can vary the delay line from 0 to 5.5 μ s in 20-ns steps. This time resolution leads to a distance resolution of 6 feet for typical cable types and a maximum cable length of 1700 feet.

TERMINATION RESISTANCE

Pulse amplitude measurements are made by adjusting the threshold of the comparator using a DAC until return pulses are no longer seen. The reflection coefficient is calculated by comparing the transmitted pulse height with the returned pulse height. If you assume the cable is lossless,

then calculate the termination resistance using the previously derived formula

$$Z_t = Z_o (1 - V_r/V_o) / (1 + V_r/V_o)$$


Assuming a cable is lossless does simplify matters, but it leads to large errors in the calculation of termination resistance for long cables. The actual attenuation coefficient per 100 feet depends on cable type and quality. Several standard nomographs are typically used by engineers for correcting reflection coefficient for line loss.

The TDR handles this problem by first determining the cable's length and the uncorrected reflection coefficient using the algorithm I've described. It then corrects the reflection coefficient for line loss based on the measured length before using the injected pulse amplitude in the previous equation.

The voltage attenuation constants for *RG-58* and *RG-59* are stored in firmware. They are approximately 3% per 100 feet of length for both *RG-58*

DOS Where You Want It

-Runs on Disk, ROM, FLASH

 

Already in widespread use on a variety of platforms, ROM-DOS has proven its dependability.

Develop your programs on a standard PC and run them in ROM with ROM-DOS, the flexible, affordable operating system that was designed for embedded applications. Compatible with MS-DOS 3.31, ROM-DOS boots and runs from ROM, disk, or FLASH memory. Features include: small size (low as 36K); runs executable files from ROM; FLASH disk support; remote disk and multimedia support; and a powerful utility suite. Confirmed compatible by VeriTest, an independent evaluator, ROM-DOS is already in widespread use on multiple system types. Developers Kit—which contains all the tools and utilities needed to configure ROM-DOS to your system, and includes license for 20 copies—costs only \$495. ROM-DOS royalty fees depend on quantity purchased, and range from \$3 to \$25 per copy.

Free Demo Disk! Call Today Toll-Free 1-800-221-6630

Datalight

17455 68th Ave NE, Suite 304, Bothell, WA 98011, USA • 206-486-8086 • fax 206-486-0253

and RG-59. Unfortunately, the attenuation is not linear. Though the TDR makes this simplification, it is able to compute termination resistances accurate to about $\pm 1\%$ for cables up to 100 feet. The accuracy of the termination resistance readout gets worse from here because the attenuation effect was empirically characterized out to 1700 feet. It is probably in the 10% range.

SOFTWARE DESIGN

The software for the TDR is very simple and straightforward with the exception of the menu system and the integer math package. We used the menu system to make the TDR easy to use and to permit some reasonable level of expansion and improvement. The integer math package affords some computational capability, but keeps code size within the constraints of the 4K maximum of 87C51.

The goal of the menu system is to provide a b-treelike structure through which menus and submenus can be called for and returned to in a straightforward fashion. We wanted to add, move, and remove menus and processes with ease. For the most part, we were successful.

Each menu item is defined within a menu structure. This structure may have an unlimited number of items and is terminated by a null. Each menu item consists of three words.

The first word is a pointer to the item's display menu string. The second word has the address to jump to if that menu item is selected. The last word is defined only when a submenu is to be loaded, in which case it holds the pointer to the submenu's data structure.

The menu system needed several routines to manipulate the data structure to operate. N X T M N U is a function created to load a submenu. It saves the calling menu's address in a parent menu stack, then it loads DPTR with a pointer to the new menu structure.

The function LASTMNU recovers the parent menu's table address and places that value into DPTR. UPDATE_MENU scrolls menu items through the display. PRINT_MENU updates the

Listing 2-The touch screen allows easy changes and additions to the menuing system.

```

; Main Menu Strings & Prompts
;-----
MAINMNU: DB      '***** MAIN MENU ****',OH
TESTCBL: DB      '1. Test Cable      ',OH
TESTTYP: DB      '2. Set Test Type   ',OH
CBLTYP:  DB      '3. Set Cable Type   ',OH
SHW_PAR: DB      '4. Show Setup      ',OH
ADJDSP:  DB      '5. Adjust Display  ',OH
;
;data structure for main menu
;
MMENU:  DW      MAINMNU      ; PTR to main menu string
;test cable
        DW      TESTCBL     ; PTR to function title
        DW      RUN         ; PTR to function routine
        DW      OH          ; No data this time
;test type
        DW      TESTTYP     ; PTR to submenu title
        DW      NXTMNU      ; PTR to Nextmenu program
        DW      TTMENU      ; PTR to submenu data structure
;cable type
        DW      CBLTYP      ; PTR to submenu title
        DW      NXTMNU      ; PTR to Nextmenu program
        DW      CMENU       ; PTR to submenu data structure
;show parameters
        DW      SHW_PAR     ; PTR to submenu title
        DW      SETUP       ; PTR to Nextmenu program
        OW      OH          ; PTR to submenu data structure
;adjust display
        DW      ADJDSP      ; PTR to submenu title
        DW      NXTMNU      ; PTR to Nextmenu program
        DW      ALMENU      ; PTR to submenu data structure
;end of main menu- zero
        OW      OH          ; nul establishes end of structure

; end of data structures for main menu
;-----
; NXTMNU: A task that saves the current value in DPTR
;         and reloads DPTR with a new menu structure.

Registers used

DPTR:    Loaded with new menu table address
ACC:     Scratch register
B(FO):   Scratch register
OH:      Scratch register
;-----
;
NXTMNU:  PUSH  ACC
        PUSH  OFOH      ; B register
        PUSH  OH        ; RO
        MOV   A,MENUPTR ; This section of code gets the
        RL   A          ; pointer to the menu stack,
        ADD  A,#MNUSTCK ; saves the current OPTR in
        MOV  RO,A       ; the menu stack, and
        MOV  @RO,DPH    ; the menu increments
        INC  RO         ; stack pointer
        MOV  @RO,DPL   ;
        INC  MENUPTR    ;
        MOV  A,OPPTR    ; This section of code uses the
        ADD  A,#MDATA   ; current menu table to obtain
        RL   A          ; the submenu table address.
        MOV  B,A        ; It then loads that address
        MOVC A,@A+DPTR ; into DPTR.
        PUSH ACC

```

(continued)

```

MOV   A,B
INC   A
MOV C A,@A+DPTR ;
MOV   DPL,A
POP   DPH

```

```

; Once a new table has been loaded, schedule the screen
; to be repainted.

```

```

SETB  DISPFLAG ; Set "print option" flag
SETB  TTLEFLAG ; Set "print title" flag
MOV   OPPTR,#0H ; Reset pointer to top of menu
INC   DPTR      Point to the first item
INC   DPTR      in the table.
POP   OH
POP   OFOH
POP   ACC
RET

```

display with the currently selected menu. Listing 2 is an excerpt from the TDR's code.

A small collection of functions that operate on 32-bit variables performs all math on the TDR. The TDR needed only an addition, subtraction, multiplication, and division function.

THE COMPLEAT TDR

The instrument we've described works in its most basic form, but we think there is plenty of room for improvement before any reasonable production could be considered. It would be fun to extend the number of cable types supported and maybe even add optical cable support. The biggest

leap in functionality would be to make the TDR, or something like it, a more integrated part of a network. It could be a device that resides semipassively on the network and is occasionally polled by a PC via an RS-232 connection. Use your imagination. □

Brian Kennez is a project engineer at Science Applications in San Diego, Calif. He has developed several fixed and hand-held microcontroller-based instruments used in vibration and radiation monitoring and analysis.

John Wettzoth is employed as the Chief Engineer of Science Applications' Military Products Division in San Diego, Calif. He also owns Tzavtech, a sole proprietorship involved in electronic instrumentation development and HP-48 calculator data acquisition.

IRS

404 Very Useful
405 Moderately Useful
406 Not Useful

ROM Borland or Microsoft C

Complete 80x86 ROM development kit!



Place your Microsoft or Borland C code in to ROM with the C_thru_ROM complete ROM development kit.

Whether you use Borland C or Microsoft C to develop for ROM, C_thru_ROM will help speed your projects to completion. This complete ROM development package is the only product that gives you all the tools you need for easy development of 80x86 ROM code on your PC. C_thru_ROM includes: ROMable startup code; floating point support; a ROMable library that includes *printf*, *malloc*, *free*, etc.; and a full 80x86 locator that outputs binary, Intel OMF, and hex formats. You can debug with your Turbo debugger or use Datalight's remote debugger. Either debugger will work through an available UART or ROM socket UARTs. This comprehensive ROM development package is available for only \$495. Call, write or fax today for your free demo disk and full details about C_thru_ROM.

Free Demo Disk! Call Today Toll-Free 1-800-221-6630


Datalight

1745.5 68th Ave NE, Suite 304, Bothell, WA 98011, USA • 206-486-8086 • fax 206-486-0253

Serial I/O on the IBM PC

FEATURE ARTICLE

Jim Schimpf

 

Connecting various devices to an IBM PC or compatible via the serial I/O is

very common, and done so with everything from a manufacturer's microprocessor development board to your latest widget. The serial interface is extremely convenient, requiring only a few wires and usually stretching far enough to make "remote control" mean something. The PC has the hardware to make this task easy, but the standard BIOS for IBM and clone PCs does not support anything but polling-type I/O, which means you are guaranteed to drop characters unless you use low data rates.

A large number of software I/O libraries are available that can make the PC serial I/O live up to its hardware. These libraries are all very good, but if you are like me and have more time than money, the simple full-duplex serial I/O package I describe here is all you need to make your project hum.

The code for SERCOM is written in Microsoft Quick C and can be easily added to your program. It can open multiple serial channels [your hardware limits the number] and each channel supports full duplex with ring buffers on both input and output. Various status checkers are present, so your program can monitor the arrival of each character or only be notified when a complete line is received. This way, even a program running on a slow 8088 can monitor two 9600-bps channels. Also included is a sample terminal emulator designed to talk to a popular microprocessor development board.

THE SERCOM SERIAL I/O PACKAGE

SERCOM has ring buffers on both input and output, which means the program using the serial input does not have to monitor the serial I/O line constantly. This arrangement is a major failing of the polling BIOS serial I/O. If your program is busy doing something else when a burst of characters arrives, you will get only a few characters and the rest will be dropped. The solution to this polling problem is to lower the data rate so the program will be able to check the line before another character can arrive.

Using SERCOM routines is like using the file operations of `stdio.h`. In this case, you include the header file `SERCOM.H` in all the modules of your program that you want to use the serial I/O routines. Listing 1 shows a skeleton for serial I/O.

Again like file operations, these routines let you have more than one open at a time. The supplied version of SERCOM limits you to two because standard PCs only support two ports. If you want to open more than two ports at a time, you will have to add their register and interrupt locations. You may open as many ports as you have hardware.

Table 1 shows the functions available when the port is opened. What each function does is obvious, but the comments in the `SERCOM.C` program source code provide descriptions of them.

Table 1 also shows a number of functions used a little less often. If you start your serial I/O program on the PC, then connect it to your remote system; plugging in the cables will probably generate a few garbage characters. In a case like this example, a call to `clean_ser()` ensures the input buffer is empty.

MTERM: A DEMONSTRATION PROGRAM

Included with the source code is a simple terminal emulator program called `MTERM`. I developed this program to talk to the Motorola EVM board and also included the capability to download S19 files to it.

As anyone who's tried to write serial support code for an IBM PC knows, the BIOS routines just don't cut it when trying to keep up with multiple high-speed ports. Jim's package replaces the BIOS with capable routines.

Listing 1-A *skeleton C program shows how a serial port is defined, opened, and closed.*

```
#include <stdio.h>
#include <bios.h>
#include "sercom.h"

main()
{
    COM *ser;

    /* Open the serial I/O port using COM1, 9600 bps, 8 data bits,
    no parity, a 1000-byte input buffer, and a 100-byte output
    buffer. */

    ser = ser_init(PORT_A,BAUD_9600,1000,100);
    if (ser == NULL) {
        exit(-1); /* Flag error, port not opened */
    }

    /* Insert main program here */

    /* Close the serial port. Failure to do this means the machine
    must be rebooted before the next program run. */

    ser_close(ser);
}
```

Writing a terminal emulator using the functions in SERCOM is simple. At the heart is a loop that monitors the PC keyboard [using `ks t a t ()`] and the serial I/O line [using `se r t s t ()`]. If a character is seen on the keyboard, it is read and sent to the serial port. If one is seen on the serial port, it is read and sent to the PC screen. When a key is typed on the PC keyboard, the remote serial device must echo it before it appears on the screen.

MTERM can both capture received data and transfer files. The program easily sends all the received data to and from a file just like it came from the keyboard.

SERCOM INTERNALS

Most of the code in SERCOM.C is very simple, but two areas deserve further explanation: initialization and ring buffers. The initialization (and shutdown) code manipulates a whole range of hardware registers in the serial I/O chip and interrupt controller of the PC. Ring buffers are a useful concept, and if you haven't used them in your code you should try them.

INITIALIZATION

At the start of the SERCOM code are a large number of `#define`s. Some

of these are the constants for the serial I/O channels. They give the address of the controller, the interrupt it is using, and the EOI command. This last command tells the 8259 interrupt controller in the system that the interrupt is handled. Other `#define`s give the names of the various registers in the serial I/O chip and the interrupt controller.

Where did all these values come from? Easiest are the serial device registers. In original IBM PCs, the the serial chip used was an Intel 8250. While most modern clone PCs use highly integrated chips that include the serial ports instead of individual

8250s, they are accessed in the same way.

To make the use of the device registers clearer, I added the simple macro

```
#define SREG(x) ((unsigned)
                ((unsigned)x + c->com_base))
```

that generates the address of the device registers. This way, because `c->com_base` is defined in the program context, the address of any device register is simply its offset (the `#defined` value) plus the base. So you will see things like

```
val = inp(SREG(LCR));
```

This code reads the LCR register using `SREG` to generate the address and the `inp` function to read this address.


With this step out of the way, you can look further into initialization. The first step is to set the data rate, parity, and number of bits per word. To do so, I used the Quick C function `_bios_serialcom()`. Using this function was simpler than actually setting the bits in the registers. If your C does not have it, writing an equivalent function is quite easy using the data sheet.

The ring buffers are allocated in the next step. Using the C memory allocation functions allows you to have variable-size buffers, and to have them created when you initialize the serial I/O port. This feature makes the SERCOM package more general. How these ring buffers work and are used is detailed in the next section.

<code>BOOLEAN putser(char ch, COM*c)</code>	Output a character
<code>int putsers(char*str, COM*c)</code>	Output a string
<code>int getser(COM*c)</code>	Get a character
<code>int getsers(COM*c, int len, char*str)</code>	Get a string
<code>BOOLEAN serhit(COM*c)</code>	Check for a character present in the input buffer
<code>BOOLEAN serline(COM*c)</code>	Test for NEWLINE-terminated string in the input buffer
<code>clean_ser(COM*c)</code>	Clear the input buffer
<code>ser_dtr(COM*c)</code>	Control DTR output
<code>ser_cts(COM*c)</code>	Control CTS output

Table 1 - The SERCOM package contains a very basic set of serial port access functions.

EPROM EMULATORS

 

\$99

AND UP

- Downloads through standard PC compatible printer port
- Includes RJ-11/12 adaptor and 6' modular cable
- Generates RESET and /RESET
- Accepts Binary, Intel HEX, Intel extended HEX and 'S' files
- Unique Vertical design minimizes mechanical interference and eliminates the possibility of noise, cross-talk or transmission-line effects from the use of a cable
- Multiple EE512s or EE1Ms can be daisy-chained for 16/24/32 bit target systems

EE256 (emulates 2764-27256) \$99
 EE512 (emulates 2764-27512) \$129
 EE1M (emulates 2764-27010) \$179

10 day MONEY-BACK GUARANTEE
 90 day repair/replace warranty

Technical Solutions

PO BOX 462101
 Garland, TX 75046-2101

Voice or FAX: (214) 272-9392

Call or FAX for ENGINEERING SPECS.

#122

Finally, you have to do the most complicated and delicate operation in the initialization: the setup of the interrupt vector and enabling serial **interrupts**. Carefully complete this step's actions in the proper order because you are changing values inside the operating system. The actions done here are

1. Save the old interrupt vectors.
2. Insert the new ones.
3. Notify the interrupt controller (8259) that interrupts are on.
4. Turn on the serial I/O **inter-**rupts.

All the code to do steps #1 through #4 is in the routine `ser_init()`. Separate sections in this routine handle the setup of COM1 and COM2. These sections set the unique constants in the COM data structure and set the different interrupt vectors. If you add another port, you will have to rewrite this routine, adding sections to support your hardware. Listing 2 shows the code to do all four steps. Note that you must turn the interrupts off before you do anything. This way, you won't be changing a vector while the system processor is trying to use it. The interrupts are turned off and the vectors are defined by Quick C; other

C compilers will have similar but different conventions. Steps #3 and #4 are then completed, and the interrupts are turned back on.

In the above section, notice that you turned on the interrupts for serial input but not for serial output. This omission was made simply because there isn't any data to output yet; thus, the 8250 transmit buffer is empty. The 8250 is set to generate a transmit interrupt on an empty transmit buffer, so that is *not* what you want now. The code to transmit data [`putser()`] turns on the interrupt whenever new data is to be sent and turns the interrupt off when there is no more.

Shutting down the serial I/O system is just the reverse of starting it. The most important functions are turning off the serial interrupt and removing and restoring the original interrupt vectors. If you don't complete these steps, then a random serial interrupt after your program finishes will use the wrong vectors and cause a system crash.

RING BUFFERS

Each serial port opened by SERCOM is assigned its own set of receive and transmit buffers (see Figure 1). Looking

Listing 2—Hooking the serial interrupts into the system and setting up the 8250 must be done properly to avoid a system crash.

```

/* Set the interrupt vector for COM1 */
_disable0;

/* Read old interrupt and set new one */
com1 = c;
c->old = _dos_getvect(c->int_number);
_dos_setvect(c->int_number, int_ser1);
break;

/* Enable IRQ4/COM1, IRQ3/COM2 on 8259 interrupt controller */
val = inp(INTC_MASK);
val &= c->irq_mask;
outp(INTC_MASK, val);

/* 8250 hardware setup */
val = inp(SREG(LSR));           /* Read and discard status */
val = inp(SREG(RBR));           /* Read and discard data */

val = inp(SREG(LCR));           /* Rst DLAB for IER access */
val &= 0x7F;                    /* 01111111B */
outp(SREG(LCR), val);
outp(SREG(IER), 1);             /* Enable Data Ready INT*/
outp(SREG(MCR), 0xB);           /* Enable OUT2, RTS, and DTR */

/* All done, restore interrupts to processor */
_enable0;
    
```

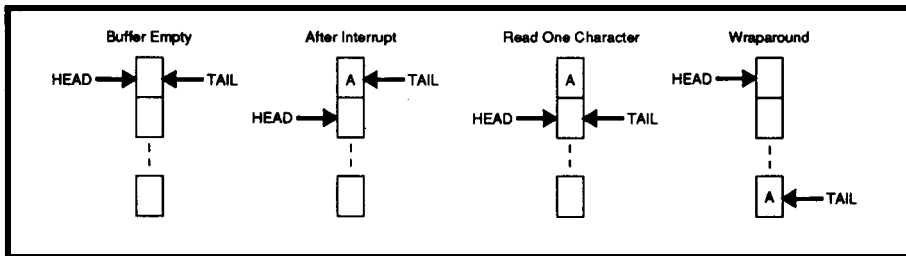


Figure 1-A ring buffer uses a pair of pointers to keep track of the beginning and the end of the buffer.

at the receive channel, you will see that the head pointer stores a character each time the hardware generates a received character interrupt. The character will be read from the hardware, inserted into the ring buffer at the head pointer location, and the pointer is advanced. The entire process happens in the background.

You can then get one character from the buffer by a SERCOM call. The character is taken from the tail pointer location, and the tail pointer is advanced. Each time a character is added to buffer, the head pointer is advanced. If the pointer hits the physical end of the buffer, it is reset to the start (which is where the *ring* in

the *ring buffer* comes from). When the head and tail pointers point to the same location in the buffer, it is either full or empty. The program keeps a count of the number of characters in the buffer at all times, so distinguishing between full and empty is easy. The ring output buffer is run the same way except the noninterrupt part of the program puts in characters at the head pointer and the interrupt driven output removes them at the tail pointer.

TIME UP FRONT

Serial support routines may seem like a small matter in the scope of a much larger program. However, done

incorrectly, they can bring a whole system down due to an unreliable serial port. Taking some time up front to ensure solid serial port operation will certainly pay off later. □

I want to thank C. J. Dunford for the original code to DUMBTERM, a simple terminal emulator.

Jim Schimpf works for an instrumentation firm designing hardware and software for highway measuring instruments.

SOFTWARE

Software for this article is available from the Circuit Cellar BBS and on Software On Disk for this issue. Please see the end of "ConnecTime" in this issue for downloading and ordering information.

IRS

- 407 Very Useful
- 408 Moderately Useful
- 409 Not Useful

DSP

HARDWARE

Check out our complete line of DSP boards based on powerful floating-point processors like the AT&T DSP32c (25 MFlops) and the Analog Devices ADSP-21020 (75 MFlops). Several analog interface modules are available. DSP boards start at just \$995.

SOFTWARE

We have everything you need to do DSP software development, including C compilers, assemblers, source-level debuggers, algorithm development tools, and many example programs. Data can be transferred between the DSP board and host at up to 3 Mbytes/sec with the host interface library (source code included).

SOLUTIONS

Call our friendly, knowledgeable staff to discuss your applications and we'll show you how easy it is to take advantage of DSP technology.

800-848-0436


BITWARE
RESEARCH SYSTEMS

400 East Pratt Street • 8th Floor • Baltimore • MD • 21202
More Info: 800-848-0436 • FAX: 410-783-7375
 
#123

8031/32/51/52 68HC11

Best Price/Performance In-Circuit Emulators



ONLY:

\$695 8031 \$995 68HC11

INSTEAD OF THOUSANDS

1-800-972-3733

FREE EVALUATION VERSION

14 DAY NO-HASSLE,
MONEY BACK GUARANTEE

EZ-ICE™, the only true next generation in-circuit emulators from **AMS** are the most complete and highest performance PC based in-circuit emulators. **with** the maximum DOS performance in a full windows-like graphical **user** interface.

Performance • Quality' - Ease

Advanced Features:

- 64K of Emulation memory
- 84,000 Breakpoints
- Trace buffer
- 12 MHz and higher clock
- Source level debugging ("C" and assembly language)
- 803 1/32/51/52/535/552 support
- HC11A/E9/811E2 Support
- CMOS support
- 7 User test probes
- Symbolic debugging
- Modem windows-like user interface

ams

Advanced Microcomputer Systems, Inc.
1321 NW 65th Place, FT. Lauderdale, FL 33309
(305) 975-9515 FAX: (305) 975-9698

#124

Add Text Overlay to Any Video Display

All the latest VCRs have on-screen programming in an effort to simplify the notorious task. Now you can have your HCS II or any other computer send you messages while you're watching your favorite TV show.

SPECIAL SECTION

Bill Houghton



Suppose, for the moment, you've built and installed the HCS II home control system described primarily in issues 25 and 26 (February/March and April/May '92) of the *Computer Applications Journal*. In issue 27 (June/July '92), Ed Nisley described an add-on LCD output device as a way to obtain information about the status of the system and its various nodes. It's a nice addition to the network, but useful only when you're near to the display module. What do you do if you're across the room watching TV settled into your favorite armchair? You could get up and venture across the room. Or, if you build the interface described in this article, you could hit a button on your HCS II IR remote and

see network information displayed on your TV set overlaid onto the program you are watching.

This article describes an On-Screen Display (OSD) terminal for HCS II (we'll call it "TV-Link" to match the other HCS II modules) that allows color text characters to be displayed on top of a background color video signal. The terminal is built around the Philips/Signetics 87C054 OSD microcontroller.

FEATURES OF 87C054

The 87C054 is an 80C51-based microcontroller designed to provide an advanced OSD for TV and video applications. It can produce characters in eight foreground and eight background colors. In addition, the background color can be removed, showing through the original video. It also has nine pulse-width modulator outputs for controlling analog functions. Similar to a standard 80C51, it has 28 digital I/O pins, two external interrupts, and two timer/counters. RAM and ROM spaces on the 87C054 are larger than the 80C51: 192 bytes of RAM and 16K bytes of EPROM. (The OSD has *additional* RAM and EPROM areas that are not part of the normal 80C51 memory map.)

One unique feature of the 87C054 is what Signetics describes as a "soft-

 


Photo 1--The W-Link can be used by your computer to overlay messages on any video signal.

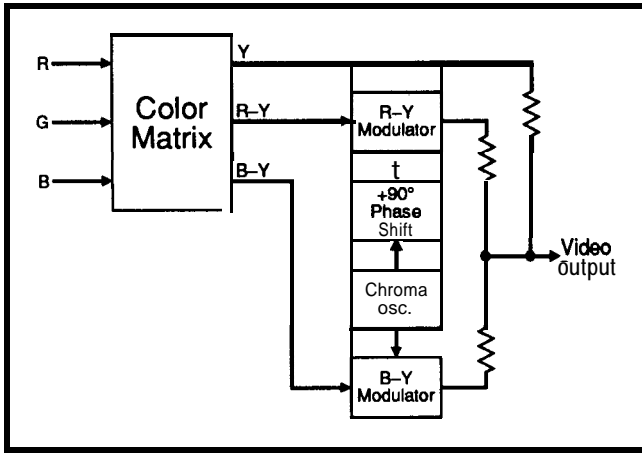


Figure 1-Converting km RGB to NTSC involves modulating and adding difference signals.

ware ADC." This ADC consists of an internal 4-bit DAC that feeds one input of a comparator. The other comparator input can be connected to one of four I/O pins. The output of the comparator is tied to a status bit in a register that is testable by software. A TV set often uses this logic for measuring the AGC voltage during tuning. A real-time clock and other low-precision analog measurements can also use it as a zero-crossing detector.

The OSD of the 87C054 consists of a 128-character RAM array (OSDRAM), a 64-character font EPROM, a video clock oscillator, and the OSD logic. The OSD logic accepts horizontal sync (HSYNC) and vertical sync (VSYNC) signals and provides three digital video outputs for character information. In the datasheet for this part, these outputs are called VID0, VID1, and VID2, but they can also (and perhaps better) be thought of as RED, GREEN, and BLUE. A multiplexer control output is also present to indicate when to display character data or original video information.

The video clock oscillator provides timing for the character dots. In most applications, this oscillator is simply an LC tank circuit connected to the VCLK pins. The frequency controls the character width. One nice feature is that the video clock is killed at the leading edge of HSYNC and restarted at the trailing edge of HSYNC, which causes the video clock to start in the same phase on every line, ensuring the dots align vertically from one scan line to the next.

to the OSD, no further CPU intervention is required to "refresh" the screen.

Many OSD architectures have been developed over the years for use in the consumer television market. Almost all of them have required fixed character row formats, limiting the designer's flexibility in designing video menus and screens.

The 87C054 was designed to avoid such constraints, and there are no architectural limits on the number of characters in a row of text or the number of rows of text to a screen. [There are physical limits imposed by the dot clock frequency and the scan rate, of course.]

The HSTART and VSTART parameters in the OSORG (on-screen origin) register define the initial position of the start of the OSD. Once the initial vertical and horizontal positions have been found, the 87C054 will "fetch" characters from the OSDRAM and place them sequentially on the screen. In order to have multiple rows

The character font stores the binary pattern for the individual characters. Characters are 14 dots wide and 18 scan lines high.

The OSDRAM stores the characters to be displayed on the screen along with certain attribute data pertaining to those characters. Once a character has been written

of text, a special character has been defined and is referred to as NEWLZNE. The NEWLINE character is much like a carriage return/line feed sequence on a computer in that it terminates the current row of characters and starts a new row of text. One advantage of this architecture is that it eliminates the need to pad display memory with space characters. The fetching and painting of rows of text will continue until either a new vertical sync pulse is detected or until an END attribute is fetched along with a NEWLZNE character.

NOW FOR THE DETAILS...

Now that you understand the concepts of an OSD operation and the capabilities of the 87C054, focus your attention on the details required to overlay characters onto live video.

The 87C054 OSD has a multiplexer output for switching video sources. Simply switching between the input video signal and the OSD character data would be nice. Unfortunately, you can't because the input video (from our home entertainment center) is in NTSC format and the character data is in RGB format. (Keep in mind that the goal is to input live video, add on-screen text, and present the result as a video signal at the output of our circuit.)

One solution is to decode the input video into separate red, green, blue, HSYNC, and VSYNC signals. Then you could perform the multiplexing between video information and character data in RGB format. The resultant signals could then be encoded back into baseband video. If

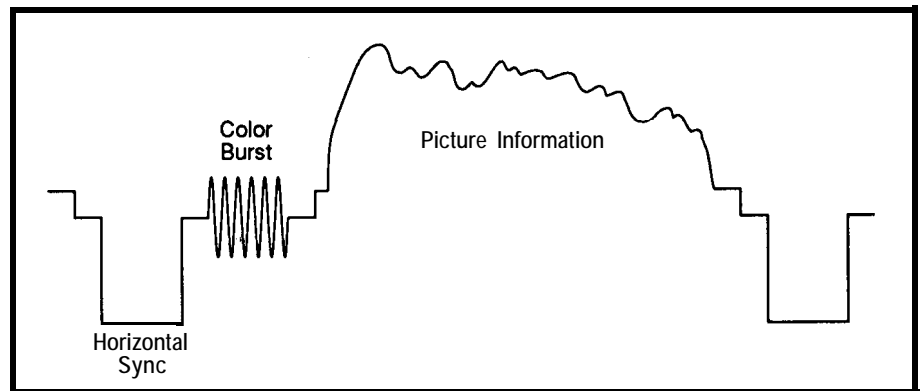


Figure 2-A typical line of NTSC video consists of an initial horizontal sync pulse, followed by a short color burst signal, then the actual picture information.

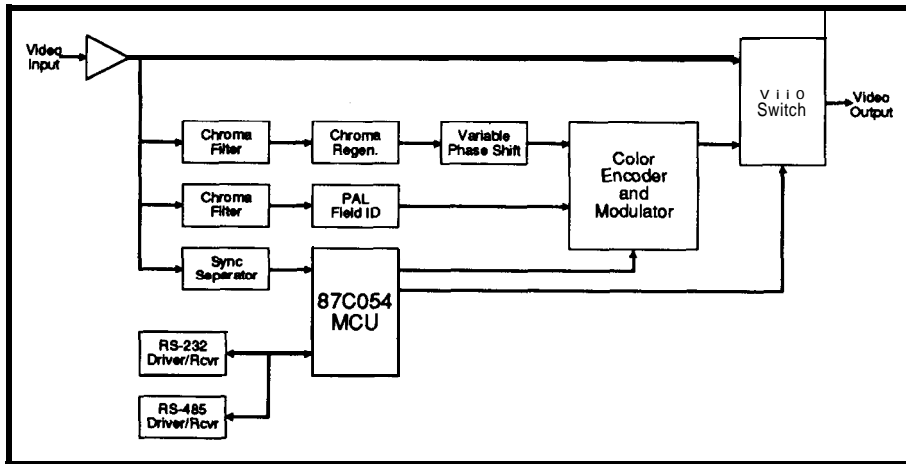


Figure 3—At the core of the TV-Link is the Signetics 87C054 microcontroller. The unit supports both RS-232 and RS-485 communications with a host computer.

there were other reasons for the conversion into RGB, such a conversion would be the way to go. However, the process of converting to RGB and then converting back to video introduces some distortion that could be visible on the screen.

Another solution is to find a way to encode the RGB data from the OSD microcontroller into video. Then you can simply switch between the two

sources. Sound simple? The situation gets a little more complex when you consider the issues of making the characters appear with the proper color in NTSC. Reviewing how color is encoded in NTSC is in order.

COLOR TELEVISION

When you first look at video, you often wonder why in the world it was done the way it was. A long time ago,

before Americans had ever heard the names of Japanese TV makers, RCA research labs were developing color television. One of the requirements imposed on designers by the FCC was that the broadcast signal needed to be compatible with existing black-and-white TV sets and had to be contained within the same bandwidth as a B/W signal. Such requirements meant that some component of the signal had to contain overall brightness information, which is the main reason why they could not simply transmit separate R, G, and B channels within the video bandwidth allowed. To make a very long story short, the engineers involved decided that the scene brightness (which they called "Y" or luminance) could be described by the relationship

$$Y = 0.59G + 0.3R + 0.11B$$

Someone observed that if they took two copies of the luminance signal and subtracted one copy from one of the colors (say, RED) and did the same with a different color (say, BLUR), the result would be two signals that contained all of the information needed to represent color. These resultant signals, R-Y and B-Y, are the color difference signals.

Now that you have two signals, how can they be transmitted on one RF carrier? The answer they came up with was to modulate one of the signals (B-Y) with an RF carrier. The other signal (R-Y) was to be modulated with the same RF carrier, but the carrier would be shifted by 90°. When the outputs of the two modulators are added together, the result is the vector sum of the two signals, containing both an amplitude and a direction (phase angle). See Figure 1.

We now have a single signal that contains all of the color information. The TV receiver needs just one more piece of information to demodulate this signal. It needs a reference for the carrier used for the modulation, that is, the receiver needs to know where 0° of the color carrier is (in video, this color carrier is referred to as the chroma subcarrier). In order to give this reference to the receiver, a small

AVOCET SYSTEMS, INC.

<p>Intel 8051 8048 8085 8096</p> <p>Hitachi 64180 H8</p> <p>Western 65816</p> <p>Rockwell 6500 6502</p> <p>RCA 1802</p>	<p>C and Pascal Compilers</p> <p>Simulators</p> <p>Assemblers</p> <p>In-Circuit Emulators</p> <p>EPROM Programmers</p>	<p>Motorola 680X0 68300 68HC11 6800 6801 6802 6803 6804 6805 6809</p> <p>Zilog Z8 Z60 Z180</p> <p>TI 32010 32020</p>
--	---	---

Source For Quality Embedded Systems

100 Main Street, P.O. Box 490, Rockport, ME 04856

For orders outside U.S., call (207) 236-9055

For technical information call (207) 236-6713 FAX: (207) 236-6713

Call today:
1-800-448-8500


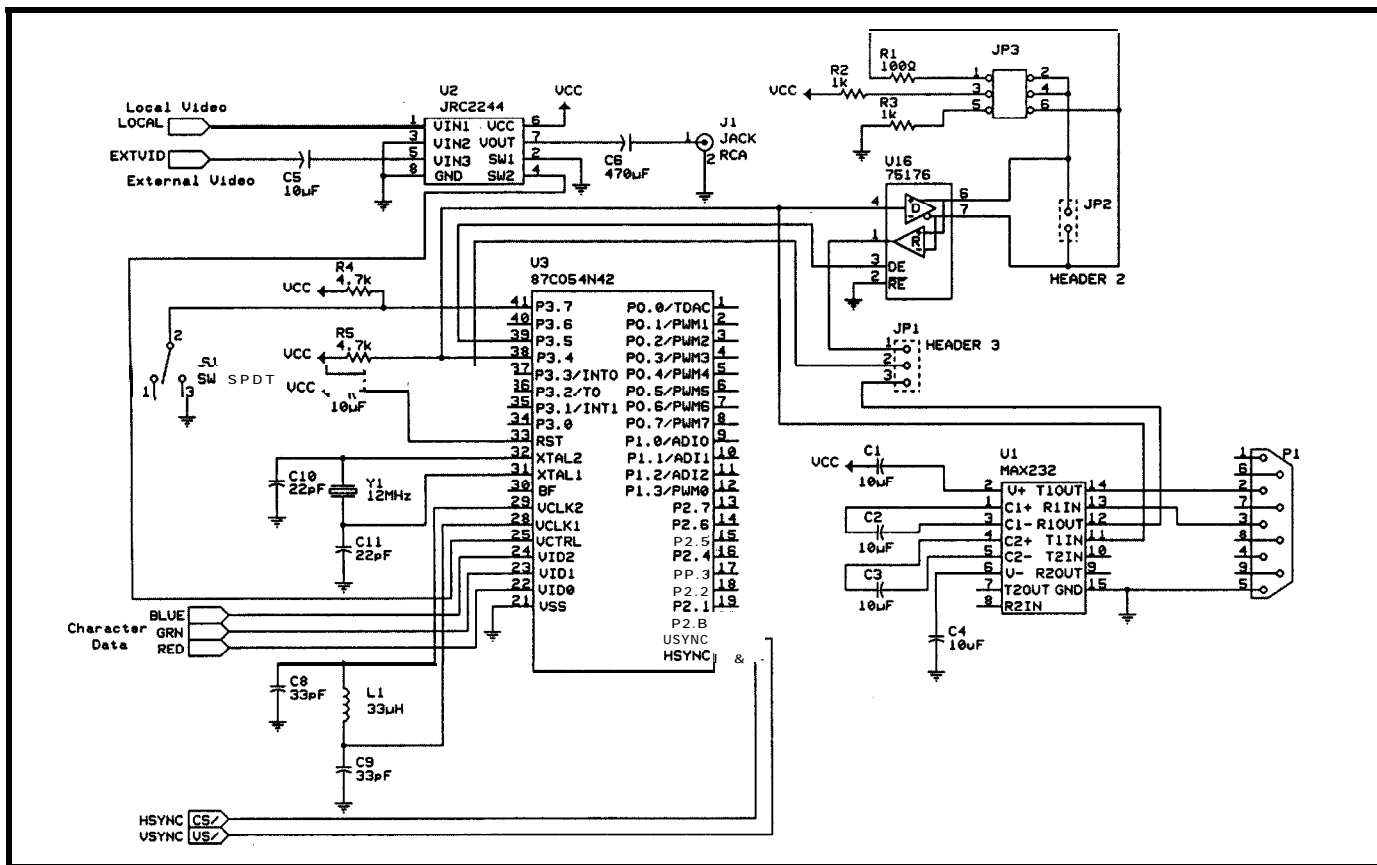


Figure 4a—The JRC2244 switches between the incoming video signal and the on-screen characters under control of the 87C054 MCU.

number, or “burst,” of cycles of the color subcarrier (hence, the term color burst) are transmitted on the back porch of the horizontal sync pulse. In most NTSC systems, this chroma subcarrier has a frequency of approximately 3.58 MHz. A typical line of color NTSC video is shown in Figure 2.

In order to convert the character data from the OSD into NTSC, you will need to sum the data into R-Y and B-Y components. Then you will need to modulate these components with a chroma subcarrier at 0° for B-Y and +90° for R-Y.

One more item to consider. If you have an output video signal composed of a video source with characters overlaid onto it, the chroma subcarrier reference [i.e., color burst] present on the output video signal is the color burst provided in the original input video. In order for the receiver/monitor to interpret the color of the OSD characters correctly, the chroma subcarrier used to modulate the OSD's R-Y and B-Y components must have exactly the same frequency and

 

MultiTask!™ Execs and GOFAST™ Math Speed Time-to-Market

Zap your application with peak performance using tested code and expert support. Control real-time scheduling with MultiTask! source code executives, or ROM-able, re-entrant GOFAST floating point:

- *Replace 80x87 MATH COPROCESSORS;
- *Drop-in IEEE SOURCE LIBRARIES;
- *Link-and-Go with C compilers: Intel®, Microsoft®, Borland®, WATCOM®, Zortech, Metaware®, and more..

Solutions for 80386/486 PROTECTED-MODE, 80x86 & V-Series, Z80/180/64180, 8085, 68xxx, 68HC16, 68HC11, 6801, 6809, 805 1, 80 196, i960, R3000, SPARC® and more.

Call for free information diskettes today. PHONE 503-641-8446; FAX 503-644-2413; USA TOLL FREE 800-356-7097.

14215 NW Science Park Drive
Portland, OR 97229
U S SOFTWARE®

© 1992 US Software Corporation. GOFAST and MultiTask! are trademarks of US Software Corporation. All other trademarks belong to their respective owners.

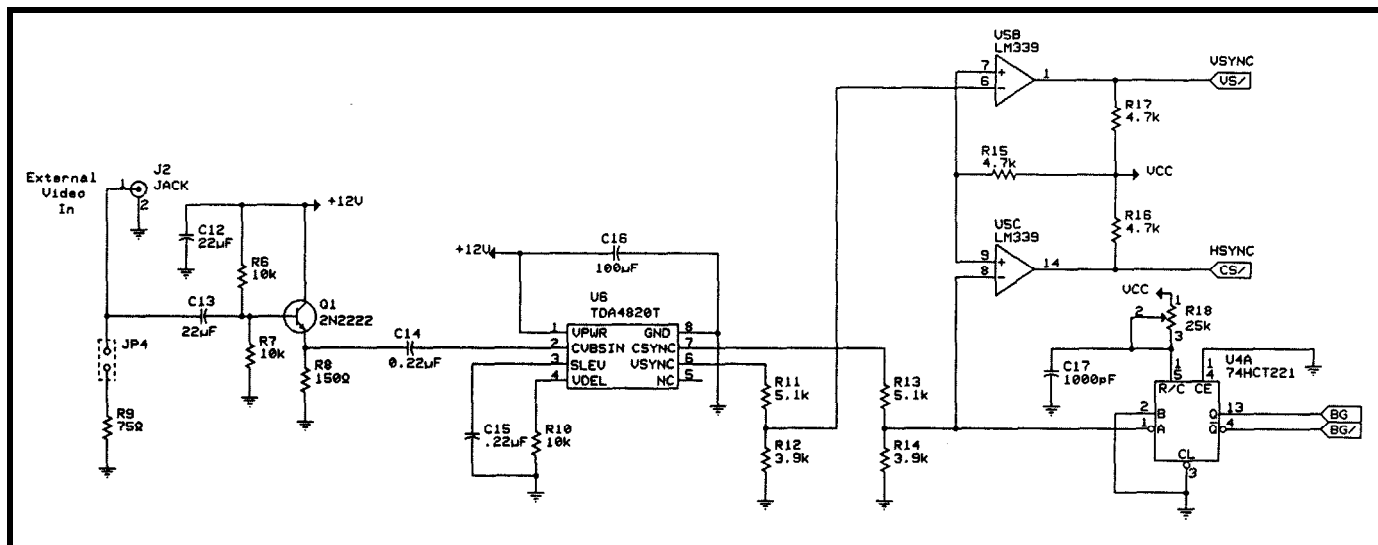


Figure 4b—The TDA4820T sync separator provides the processor with horizontal and vertical sync signals

phase as the color burst on the original video input signal.

Once you get the OSD information in the form just described, you can switch between this “OSD video” and the original input video to produce the final output.

THE TV-LINK HARDWARE SOLUTION

Figure 3 shows a block diagram of the TV-Link, while Figure 4 shows the schematic.

Referring to the schematic, the original input video connects to J2 and is AC coupled into buffer amplifier, Q1. This amplifier provides load isolation between the video signal source and the circuits on the TV-Link board. JP4 is a jumper allowing for a 75-ohm termination resistor to be connected to J2. The output of the Q1 buffer amplifier feeds the sync separator, the video switch, and the chroma subcarrier regenerator circuits.

SYNC SEPARATION

The sync separator consists of U6, a TDA4820T Philips sync separator. The video signal is coupled into the TDA4820T through capacitor C14, where it is amplified with a gain of 15. The black level clamping voltage is stored in capacitor C14. From the stored black level voltage and the peak sync voltage, the 50% value of the peak sync voltage is generated and stored in capacitor C15. A slicing level control circuit ensures a constant 50%

peak sync value regardless of the picture content amplitude provided the sync pulse amplitude is between 50 mV and 500 mV. A comparator in the composite sync slicing stage compares the amplified video signal with the DC voltage derived from the 50% peak sync voltage, producing the composite sync output. Vertical slicing circuits compare the composite sync signal with a DC level equal to 40% of the peak sync signal, producing the vertical sync output. The reduced vertical slicing level ensures more energy for the vertical pulse integration. The slope is double integrated to eliminate the effects of interference caused by noise or line reflections. The value of resistor R10 sets the vertical integration delay time.

The outputs of the sync separator are positive-going signals with peak amplitudes exceeding 10 V. Resistor pairs R11/R12 and R13/R14 serve as voltage dividers for the VSYNC and CSYNC outputs, respectively. An LM339 comparator, U5, serves as an inverter for the sync signals because the modulator circuits require active low sync signals.

There is a great tendency with video circuits to make the coupling capacitors very large to pass the low-frequency sync components (60/50 Hz, typically) into low-impedance nodes. The TDA4820T has a moderately high input impedance on pin 2. Because the black level is stored in C14, the value of C14 should be kept close to 0.22 µF.

THE 87C054 MCU WITH OSD

The 87C054 microcontroller, U3, accepts composite sync and vertical sync signals from the sync separator and provides RGB digital outputs for character data. The multiplexer control output, VCTRL, connects to the video switch, U2, a JRC2244.

Inductor L1 and capacitors C8 and C9 form a video clock oscillator that determines the width of a character font dot. The values of these components are not critical but are typically chosen such that a video dot width is equal to the spacing between scan lines. This oscillator is killed at the leading edge of the HSYNC signal and allowed to startup at the trailing edge. Such synchronization causes the oscillator to start at exactly the same point from one scan line to the next, causing character dots to appear in exactly the same spot on each line.

In addition to the OSD functions, the 87C054 also performs network interfacing and protocol tasks. This microcontroller has plenty of performance bandwidth because the OSD logic is self-refreshing and independent of the MCU core.

VIDEO SIGNAL SWITCHING

The JRC2244 video switch, U2, contains three video inputs, two of which are used in this application. One of these inputs, VIN1, is capacitively coupled to the OSD video signal. This signal is the 87C054’s RGB data after encoding into baseband video.

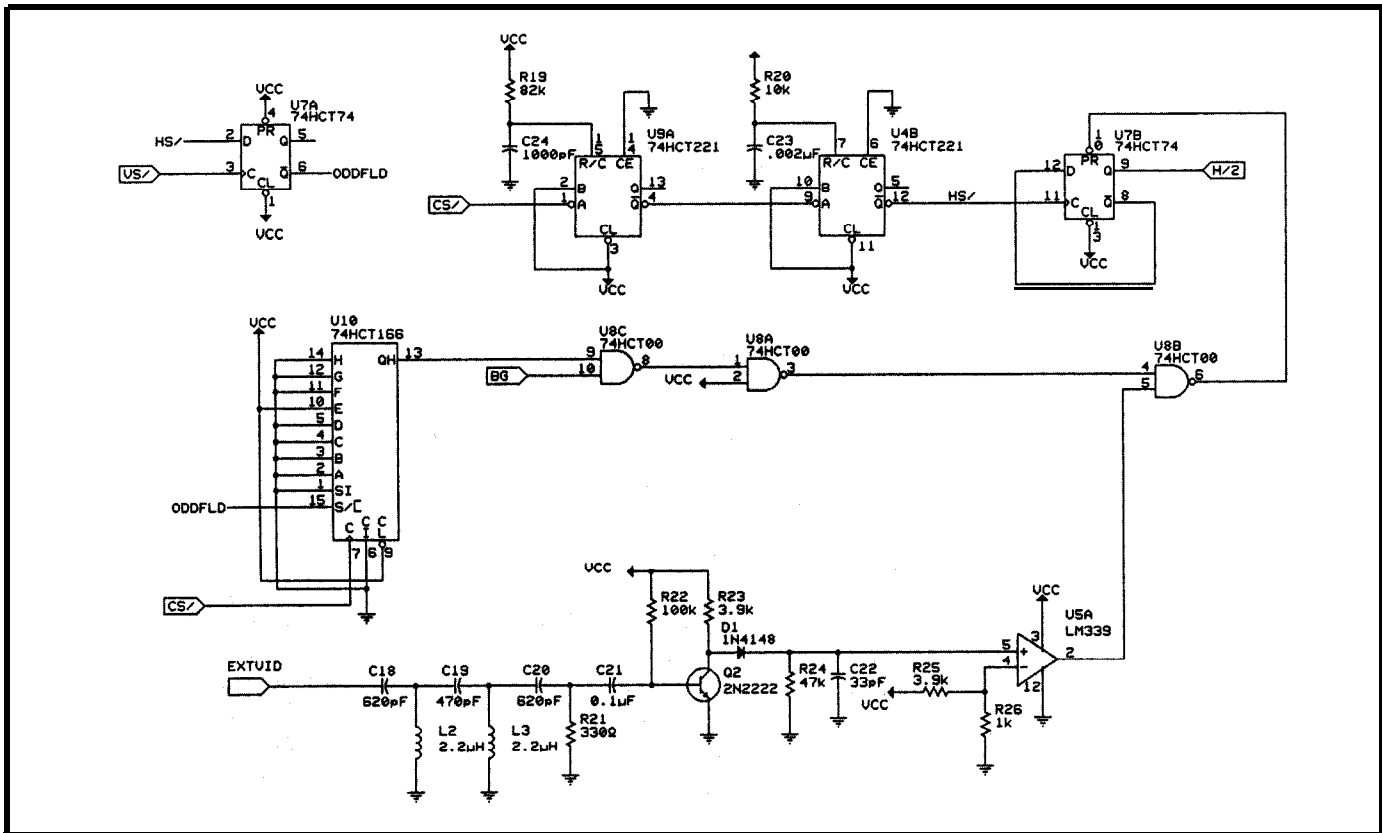


Figure 4c—In order to properly overlay colors onto a PAL signal, you must know whether you're on an odd or an even field, so extra circuitry must be included on the board to support PAL

\$325.




32 Bit RISC and Video Display Module for Embedded Graphic Display Applications

The Pixel Press is a 3.1 x 5.1 inch module used to control video image generation and replace personal computers (PCs) in embedded applications. When compared to a 386 PC the Pixel Press not only provides superior resolution and response but it does so at a fraction of the cost, size and power requirements (5V at 800ma). Further, the Pixel Press does not include the watchdog timer and voltage supervisor required in embedded processors but not found in PCs.

Included in each Pixel Press is a 32 Bit RISC Processor (86C010 from VLSI Technology), 512K byte frame buffer, 256K byte processor DRAM, EPROM, voltage supervisor and watch dog timer. A parallel interface is used for high speed command and data transfer while a RS-232 (TTL Level) port is used for debug or remote input. The parallel port operates in both a master and slave mode and the serial debug port can be configured for connection to a PC compatible keyboard. In slave mode BUSY and /ACK signals are generated to mimic an IBM or Centronics printer. Slave mode also supports direct connection to a micro-processor bus. Master mode allows the RISC to read and write up to 64 external IO ports.

The Pixel Press Module mechanically mounts to either a user printed circuit board (PCB) or chassis. PCB mounting is accomplished by soldering the Pixel Press 0.025 square posts directly into the user PCB. Chassis mounting makes use of four 4x4 threaded mounting holes.

Our other Fine Products

 


Our 24 BIT PARALLEL IO card with double buffered TTL IO features programmable direction control & "Ground between Signal" design for high speed reliable operation. Includes fused power and interrupt support with Schematics. \$95.

The DPROM 2 EPROM EMULATOR with battery backup. RS-232 Port and 57.6K download of HEX and S records. Emulates 2732 27010. Units can be ganged for 27020, 27-1024/2048/4096. 64K Byte-\$150.

The EASYON SMART EXTENDER is so unique we were granted US Patent No. 5,047,708. Allows aboard to be plugged into a PC/XT/AT/PS2 computer with the POWER ON. A Tremendous time saver for R&D and production test. PC/XT-\$195. AT-\$225. PS2-\$325.

 An EASYBUS back plane is a AT style passive back plane that includes 3 bus switches. Program control of the switches allows a processor to power down portions of the bus for repair, maintenance or power reduction \$895.



Call for a complete data sheet, pricing or engineering support.

Applied Data System, Inc.

409A East Preston St. Baltimore MD. 21202

1-800-541-2003 1-410-576-0335 Fax 1-410-576-0338

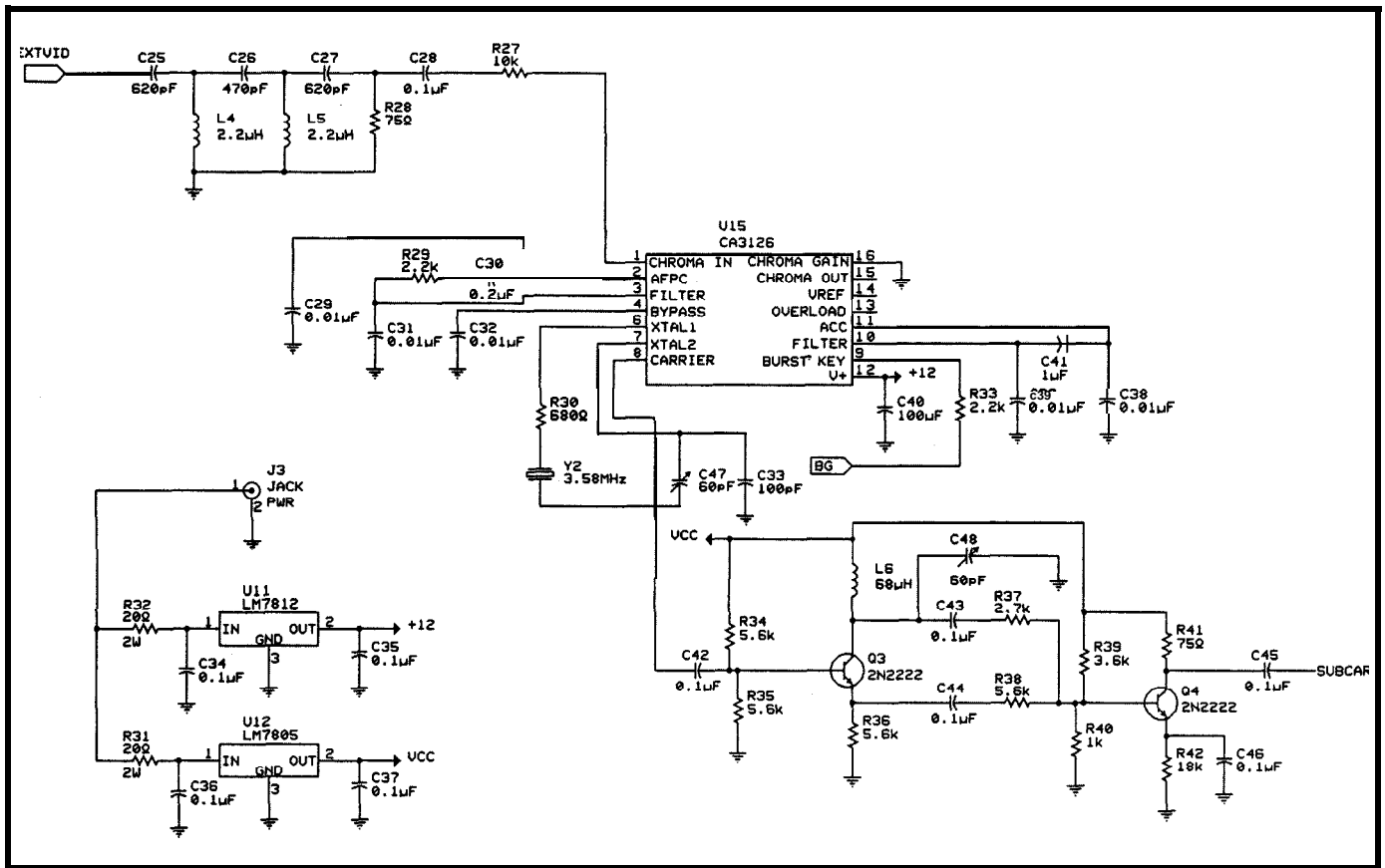


Figure 4d—The CA3126 TV chroma processor is designed specifically for regenerating chroma subcarriers

The other input, VIN3, is capacitively coupled to the original video input signal. The JRC2244 provides internal bias sources to provide DC restoration to its video inputs. The JRC2244 accepts a switching control signal from the 87C054 and switches its output between the original video input and the OSD video signal. The video switch also has an internal 75-ohm line driver in its output stage.

The JRC2244 has a moderate input impedance of about 15k ohms, allowing 10- μ F coupling capacitors to be used. The output coupling capacitor is large because this signal can be used to drive 75-ohm loads.

RGB ENCODING

The LM1886, U13, and the LM1889, U14, encode the RGB data from the 87C054 into baseband video. The LM1886 has three DACs, one for each color. Each of these DACs has 3-bit inputs, but because the 87C054 data is digital, the inputs to the LM1886 DACs are tied together yielding an output for each DAC that is

either full-scale or zero. The outputs of the three DACs are internally summed to produce the luminance, R-Y, and B-Y amplitudes. The LM1889 accepts the regenerated chroma subcarrier, modulates the R-Y and B-Y signals, and produces baseband video on pin 13. Transistor Q5 is used as a buffer amplifier with voltage dividers R49 and R50 producing proper levels for the video switch. Note that the LM1889 accepts an external subcarrier signal at the junction of R46 and C52, but this subcarrier undergoes a phase shift caused by the resistor and capacitor networks associated with pins 1 and 18 of the LM1889. This phase shift will need to be considered when the subcarrier is regenerated.

CHROMA SUBCARRIER REGENERATION

The circuits that reproduce a chroma subcarrier in the same frequency and phase as the color burst consist of a high-pass filter, a sample-and-hold phase-locked loop (PLL), and a phase shift network and amplifier.

The passive high-pass filter consists of inductors L4 and L5, resistor R28, and capacitors C25, C26, and C27. The filter starts passing signals at about 3.2 MHz, allowing the chroma subcarrier to pass through to the CA3126, U15.

The CA3126 is a TV Chroma Processor IC designed specifically for regenerating chroma subcarriers. This IC contains a VCO and a PLL with sample-and-hold circuits in the error correction loop. As a result, the VCO-generated carrier is compared with the chroma signal from the high-pass filter during the time that color burst is present, indicated by the burst gate pulse (which I will describe later).

The regenerated carrier output is present on pin 8 of the CA3126. Even though this carrier is phase locked to the color burst, it is not at exactly the same phase as the color burst. The nature of a PLL is such that the output will be locked but will always have some constant fixed phase delay relative to the input. Also, recall that the input circuits of the LM1889 added

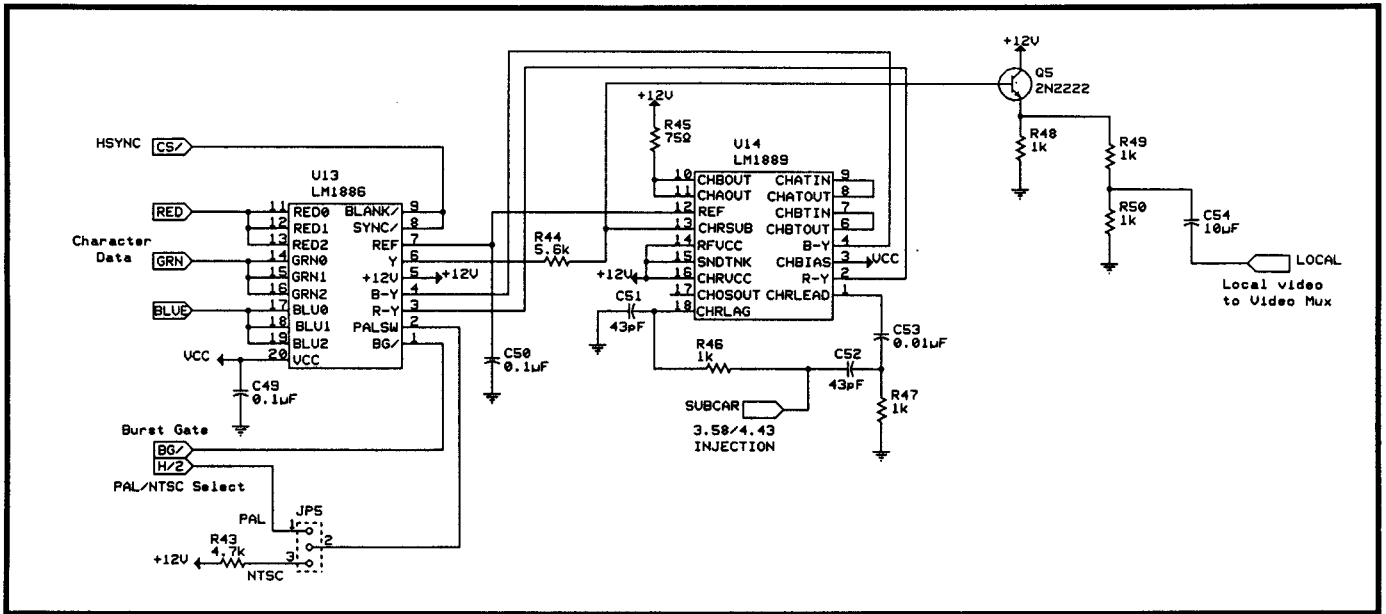


Figure 4e—Encoding the RGB data into baseband video is accomplished with an LM1886, which contains three DACs, and an LM1889, which accepts the regenerated chroma subcarrier, modulates the R-Y and B-Y signals, and produces baseband video.

an additional constant phase shift to the injected carrier.

The phase shift network and amplifier consisting of the Q3 and Q4 stages compensate for these fixed phase delays. This circuit provides an output whose phase is adjustable by means of variable capacitor C48, and has a tuning range of approximately 0° to 160° of phase shift. For a given input signal amplitude, the output signal amplitude is constant, regardless of the phase shift introduced. The output of this circuit is the signal injected into the LM1889 circuits.

CONNECTING TO THE HCS II

Now that you have a working terminal circuit for overlaying text onto live video, you still need to connect it to the HCS II network. In order to do this, you will need a serial interface compatible with the network, some software that handles network message formats, and software that interprets network messages and creates responses or actions (or both) to those HCS II network messages.


This particular design includes both an RS-232 and an RS-485 interface. U1, a MAX232, provides the RS-232-to-TTL conversion for both the transmitter and receiver. U16, a 75176, provides the RS-485-to-TTL conversion. JP1 connects the receiver pin of

the 87C054 to either the RS-232 or RS-485 interfaces. The transmitter pin of the 87C054 connects to both the RS-232 and RS-485 interfaces. One pin of the 87C054, P3.5, controls the driver enable of the 75176, allowing for

selective talking on the HCS II network. JP3 provides for termination of the network.

"But, wait a minute! The 87C054 doesn't have a UART," you say. True. There is no built-in UART on the

8051 68HC11 COP8 68HC05

 

iceMASTER™ Improved User Interface Features

Rental And 10-Day Trials Available

- **iceMASTER delivers productivity:** easy to learn, easy to use and fast!
- **Hyperlinked On-line help** guides you through the emulation process.
- **iceMASTER is FAST!** The 115.2K baud serial link keeps typical download times to under 3 seconds using a standard COMM port!
- **Broad support of derivative devices.**
- **Flexible user interface:** you can completely configure the windows for size, content, location and color.
- **iceMASTER is convenient!** It connects easily to your PC, requires no disassembly, nor does it take up any expansion slots. It works on any PC (DOS or OS/2), Micro Channel or EISA. Even Laptops!
- **Supports source level debug** (C and PL/M) and source level trace. 4K trace buffer with advanced searching and filtering capabilities.
- **Now virtual memory and mouse support.**



Call today for **FREE DEMO DISK!**
Call today to ask about **FREE 8051 Macro Assembler!**
(800) METAICE (800) 638-2423



MetaLink Corporation P.O. Box 1329 Chandler, Az 85244-1329 Phone: (602) 926-0797 FAX: (602) 926-1198 TELEX: 4998050MTLNK

A = string	Set HCS II network address to string
Fx	Execute special function 0 Initialize screen 1 Display on 2 Display off 3 Display color bars 4 Wipe on 5 Wipe off
Hxy	Set Px.y high
Lxy	Clear Px.y low
Nn	Network response mode NO = normal network interface, no auto error or acknowledge responses N1 = auto error and acknowledge response
Px	Query port x 0 = Port 0 1 = Port 1 2 = Port 2 3 = Port 3
Px= nn	Write to port x where nn= two-digit hex value 0 = Port 0 1 = Port 1 2 = Port 2 3 = Port 3
R X	Query register x; returns two-digit hex number 0 = OSDT (contents undefined) 1 = OSAT 2 = OSCON 3 = OSORG 4 = OSMOD 5 = Default char. attribute 6 = Default background space attr 7 = Default NEWLINE attribute
Rx = nn	Write to register x; for use from outside of a string of text; writes to these registers from within a string; should use the \Wxnn command 0 = OSDT 1 = OSAT 2 = OSCON 3 = OSORG 4 = OSMOD 5 = Default char. attribute 6 = Default background space attr 7 = Default NEWLINE attribute
S= string	String for OSD display; can include escape sequences for text formatting, color, selection, etc.
Wxnn	Write to register x; for use within a string; functionally equiv. to the Rx = nn command
Special characters for use within a string of text	
\E	End of Display at current position
\B	Background Space
\S	Split Background Space
\N	NEWLINE

Table 1—The set of supported commands resembles that of most of the other HCS II network modules.

87C054 and the part does not have a transmitter pin or receiver pin.

In this application, the serial data transmission and reception has been performed in software. The routine that handles serial transmission and

reception was taken from the Signetics BBS ([800] 45 1-6644). It was originally designed for the 87C75 1 and had to be slightly modified to operate with one of the 87C054's timer/counters. The technique is often called "bit banging"

and has the advantage of saving some hardware if you can afford the necessary time required of the software.

NETWORK PROTOCOL PROCESSING

As I indicated earlier, in addition to the serial interface software, you need code that handles network message formats. The code starts by waiting until either a "#" or an "!" is received, either of which indicates the start of a network message, then the entire message is stored in a buffer.

Once the carriage return has been stored, the beginning character of the message is checked to see whether the message includes a checksum. If the message does not contain a checksum, the packet is assumed to be valid and the contents of the packet are processed. If a checksum is included, then the VERIFY routine is called to perform a checksum calculation on the packet. If the checksum matches, the packet is processed; otherwise, it is ignored and I return to waiting for the next network message.

My original plans for handling network checksums included a checksum generator for sending network responses and a checksum checker for received messages. However, when I flowcharted the needs of both routines, I found that an awful lot of the logic was common to both. I went back and looked at the suggestions that Ed Nisley had provided for handling the checksums and understand now why he made those suggestions. My VERIFY routine's logic is based on Ed's previous work.

The VERIFY routine performs two functions. First, it takes the checksum digits in the packet, converts them to binary numbers, and stores them in temporary variables. Next, the checksum digits are replaced with ASCII zeros and the checksum of the string is calculated. If the checksum matches, the error flag, CHECKER, is cleared; otherwise, it is set. The checksum that was calculated is converted to ASCII and stuffed into the checksum digits position, replacing the ASCII zeros.

To prepare a string for transmission, all that is necessary is to stuff the

message in the buffer with the checksum digits set to ASCII zeros and call the VERIFY routine. To check a message for correct checksum, simply call the VERIFY routine and check the CHKERR flag on return.

Once the checksum verification (if required) has been performed, you still need to process the packet to see if it belongs to this terminal, and if it does, then you need to determine what action the network controller is asking you to take.

The PROCESS routine first scans the packet, converting characters into upper case until the end of the packet has been reached. Next, the first character is examined to determine if the packet has checksums or not and a pointer is set to the NODEID position of the packet. The NODEID in the packet is compared with the NODEID variable. If there is no match, the packet is ignored and you wait for the next network message. If it does belong to this terminal, you can process the body of the network message.

NETWORK COMMANDS AND SYNTAX

The real essence of a network message is to carry a command from the network controller to the terminal or carry a response from the terminal back to the network controller. Table 1 shows the syntax of the commands available for operating the TV-Link terminal. These commands allow the HCS II Supervisory Controller to manipulate ports on the 87C054, format text for display, implement special built-in display functions such as color bars, and to read and write OSD registers directly, giving full control of the OSD to the HCS II.

CONCLUSIONS

Developing this application was interesting and enjoyable. It also presented some challenges.

The 87C054 proved well suited to this application in large part because of the 80C51 core and that the OSD is independent of the CPU. Once characters have been written to the OSD, you can forget the OSD until you want to change the display, and the CPU is free to pursue other tasks.

The on-screen display and the microcontroller operations are primarily digital functions. The question of how to combine this technology with an analog video signal can be perplexing to most system designers whose professional experiences have been mostly digital circuits. One of the most perplexing issues during this project was how to recreate the chroma subcarrier. I knew that every color TV set had to perform this function, but finding out solutions took some searching before I discovered the CA3126. I'm hopeful you can profit from my experiences on this project. □

My thanks to Herb Knies and George Ellis of Signetics for their help. Thanks also to Greg Goodhue from Signetics, who wrote the software-based UART code for the 87C751 that I modified for this project.

Bill Houghton is an Applications Engineer at Signetics specializing in 80C51-based microcontrollers.

SOFTWARE

Software for this article is available from the Circuit Cellar BBS and on Software On Disk for this issue. Please see the end of "ConnecTime" in this issue for downloading and ordering information.

SOURCES

Requests for literature on Signetics/Philips microcontrollers including the "80C51-Based 8-Bit Microcontroller Data Handbook" may be directed to Sharon Baker at (408) 991-3518.

Contact Bill Houghton at (408) 991-3560 with technical questions specific to the 87C054 and for information on the availability of a PC board and components for this project.


IRS

410 Very Useful

411 Moderately Useful

412 Not Useful

 FAST COMPLETE ACCURATE DRAM TEST DIPs - SIMMs - SIPs



RAMSTAR 1ns. RESOLUTION

ACCESS SPEED VERIFICATION

80 ns. thru 180 ns. (Std.)	\$249.0
45 ns. thru 110 ns. (Fast)	\$349.0
4MEG Option	Add \$ 89.0

AUTO-LOOP

Continuous Test 6.25 MBits/sec.

ADAPTERS:

SIMM/SIP ADAPTER	\$189.0
Tests 64K, 256K, 1 M & 4M Devices 8 or 9 Bit versions.	

NEW

NTX ADAPTER	\$149.0
Tests 64 Pin Dual-Edge LaserWriter Type SIMM's.	

4 X ADAPTER	\$ 89.0
Tests 64K & 256K By 4 Bit Devices	

AC ADAPTER	\$ 18.0
Regulated +5V @ 1 Amp.	

FREE RAMFACTS DRAM NEWSLETTER

1-800-RAMSTAR

COMPUTERDOCTORS
9204-B Baltimore Boulevard
College Park, Maryland 20740

MADE IN U.S.A.


U.S. PATENT No. 4,965,799

#130

The Virtues of the Hue, Lightness, Saturation Color Model

SPECIAL SECTION

James R. Furlong

 

Have you ever wondered why graphics that use the default EGA/VGA color palette look as lousy as they do? Did you think your boss was kidding when he told you to mix equal levels of red and green to create yellow on your computer? My Crayolas never did that. Have you ever wanted to portray the shock heating of a piece of orbital debris impacting a satellite bumper shield at 6.5 kilometers per **zas** continuous tones of red, but gave up after trial-and-error guessing of RGB combinations made you surmise you were color blind? If you answered yes to any of the above, let me assure you that a) you are not alone and b) a well-established but little-publicized color model named HLS (for Hue, Lightness, and Saturation) is the cure for your palette woes.

Designed by people who thought about what color means to people before how color is described for a machine, the HLS model takes the guesswork out of making colors like shocking pink or pastel green. Simple analytic functions and a handful of lines of computer code create a palette of continuous tones of red, or periwinkle, or they can bridge dark blue with bright orange because the model's coordinates are dimensionless.

The following description is of the transformation equations between the **HLS** and RGB color models and the BIOS interrupts necessary to load IBM VGA hardware with RGB values, so you can think in terms of HLS but speak to your computer in RGB. I also introduce an extension to the I-ILS model that allows more color possibi-

ties and unlocks the 262,144 colors of which the VGA is capable.

MODEL COORDINATES

Figure 1 illustrates the conceptual framework for the HLS model [1]. The figure is three-dimensional because the model has three coordinates. They are defined as follows:

Hue-Hue is what many of us would commonly refer to as color. Red, green, and purple all are hues, but in the context of the HLS system they are colors absent of a definition for lightness (dark red or bright red), and saturation (pure red or pink).

Hue is perceived as the azimuth coordinate on the model. This designation isn't arbitrary, but rather it is a consequence of a special additive nature of the RGB system itself. In Figure 1, notice that if blue is arbitrarily taken as the starting point, you can smoothly scroll through the **cyans**, greens, yellows, reds, magentas, and finally wind up back at the beginning, namely blue, without any loss of continuity. You will have the sense that you passed through all the basic colors in the visible spectrum.

Saturation-Saturation defines the pureness of a hue for a given level of lightness. Conceptually, saturation is the radial coordinate in the model. The larger the radial coordinate, the purer the color. Colors of low saturation tend to be soft, or pastel, and fully saturated colors can be harsh, depending upon their lightness.

A lack of saturation defines the grayness of a hue. Note that grayness covers all levels of gray, from total black to pure white. Any hue at zero saturation will be pure gray. Whether the gray is black, white, or somewhere in between will depend on the lightness. A good example of an unsaturated color is pink, which is somewhere between pure red and white.

Lightness-Lightness is how bright or dark a color is, as the name implies. It is the vertical axis of the model. Due to the model's double cone structure, the maximum saturation level depends on lightness. This level varies from 1 at the equator to 0 at the poles. A lightness of 0 or 1 will have a maximum saturation of 0 because

If you thought RGB (red, green, blue) was the only (or best) way to represent color, think again. The Hue, Lightness, Saturation (HLS) model can actually be better than RGB at representing colors in some applications.

 


Figure 1-The HLS model can be conceptualized in three dimensions as a pair of cones. Hue proceeds around the cones, Lightness runs in the vertical direction, and Saturation extends radial from the center and depends to some degree on the Lightness. (© Tektronix Inc.)

those values correspond to black or white, while a hue can be fully saturated at the equator. The intuitiveness and elegance of the HLS model become apparent when it is compared to RGB. Take pastel green, for example. Under RGB you would first set the lightness of green with GREEN intensity, but to soften the green you would have to add equal

levels of BLUE and RED. That doesn't really make sense, does it? Under HLS you would first set HUE to green, then make the green as bright or dark as you want with LIGHTNESS, and as pastel as you want with SATURATION. Furthermore, pastel green happens to be one of the easier colors to make under RGB because equal levels of

BLUE and RED are an exact complement of GREEN. If you shift the color from pastel green to say pastel cyan (cyan is equidistant from BLUE and GREEN), then the ratio between BLUE and RED would no longer be unity, and you would need an ambiguous combination of BLUE and RED to soften the cyan.

TRANSFORMATION EQUATIONS

The process of creating the HLS transformation equations begins by recognizing the relationship between RGB and the hue coordinate. Figure 2 lays out HUE in one dimension. Although HUE is the azimuth coordinate and should be referred to by angle, I have normalized its value to 1, maintaining consistency with the other coordinates. You can make the starting point any value you want because the hue coordinate is circular. In my system, HUE = 0 is defined as blue.

With a little imagination, you can see that if trapezoidal-like functions for BLUE, GREEN, and RED are used (which only differ from each other by their starting hue point) the entire hue coordinate can be traversed to mimic the color transitions shown in Figure 1. For example, starting from HUE = 0 and tracing through the functions in Figure 2, BLUE is the only function with a positive value. Advancing to HUE = 1/6, BLUE remains constant while GREEN begins to increase, eventually equaling BLUE. The equal levels of BLUE and GREEN create the familiar cyan hue.

If you continue to trace through the functions, for 1/6 < HUE < 1/3, GREEN remains constant while BLUE is brought to 0, resulting in the green hue at HUE = 1/3. A subsequent tracing through the functions will show that the growth and attenuation experienced by GREEN repeats for the other two colors, first for RED at HUE = 1/3 and then for BLUE at HUE = 2/3. At HUE = 1, you have come full circle and are back at blue.

Defining the trapezoidal-like functions for RED, GREEN, and BLUE requires nothing more than superposing linear functions with different amplitude offsets. For example, the

function **BLUE** over the interval $0 < \text{HUE} < 1/6$ is defined by

$$\text{BLUE} = f_1 + f_2$$

where,

$$f_1 = \frac{1}{\Delta x} x + 2 \quad \text{and} \quad f_2 = \frac{1}{\Delta x} x - 1$$

where x represents **HUE**, and Δx is a constant equaling $1/6$. These two functions will maintain **BLUE** at a constant value of 1 indefinitely. **BLUE** needs to be attenuated for $x > 1/6$, which is done by adding another linear function, such as

$$f = -\frac{x}{\Delta x} + 1$$

for $x > 1/6$. However, limiting f_2 to negative values with a **MIN** function and letting **BLUE** decrease according to f_1 is just as easy. Similarly, a **MAX** function can be used to prevent **BLUE** from becoming negative for $x > 1/3$. The analytic form for the function **BLUE** over the entire range of the hue coordinate as well as the functions for **GREEN** and **RED** are as follows:

$$\text{Blue} = \text{MAX}\left(\frac{x_2 - x}{\Delta x}, 0\right) + \text{MIN}\left(\frac{x - x_1}{\Delta x}, 0\right) + \text{MAX}\left(\frac{x - x_4}{\Delta x}, 0\right) + \text{MIN}\left(\frac{x_5 - x}{\Delta x}, 0\right)$$

$$\text{Green} = \frac{x}{\Delta x} + \text{MIN}\left(\frac{x_1 - x}{\Delta x}, 0\right) + \text{MIN}\left(\frac{x_3 - x}{\Delta x}, 0\right) + \text{MAX}\left(\frac{x - x_4}{\Delta x}, 0\right)$$

$$\text{Red} = \text{MAX}\left(\frac{x - x_2}{\Delta x}, 0\right) + \text{MIN}\left(\frac{x_3 - x}{\Delta x}, 0\right) + \text{MIN}\left(\frac{x_5 - x}{\Delta x}, 0\right)$$

Listing 1 shows the C code for the functions **BLUE**, **GREEN**, and **RED**, named `mag_blue`, `mag_green`, and `mag_red`, respectively. The values returned are always between 0 and 1.

Listing 2 contains the C code for the set pa 1, which transforms HLS values to RGB and then calls the video BIOS to load VGA registers with the RGB values. set pa 1 receives as its argument values for hue, lightness, saturation, and the register whose color you are going to define.

For VGA 640 x 480 resolution, only 16 colors may be displayed

 


Figure 2—By laying out hue in one dimension, it's possible to begin to see the relationship between hue and RGB. Each of the RGB colors forms a trapezoid that partially overlaps the other colors.

simultaneously, which means only register values 0-15 are legal. set pa 1 is declared in t, so it may return a value about the success of the function call. I did not show you the coding that checks if the arguments passed to setpa 1 are within range and if the current screen mode is 16-color VGA.

The first operation set pa 1 performs is determining the complement of hue, referred to as **eh** in the

coding. Knowing **eh** is essential for establishing the saturation.

Refer to Figure 3, which shows a horizontal slice through Figure 1 at the equator. This figure shows a vector that indicates a fully saturated hue drawn, in this case, at the "orange" azimuth. Adding a vector 180° away from the hue vector reduces the radial magnitude of the hue because the saturation is the magnitude of the

Listing 1—When determining the proper red, green, and blue components, a normalization process must be done to ensure the final values are between 0 and 1.

```

/*=====
return normalized blue component
=====*/
float mag_blue(float x)
{
float result;

result = (max1(x2 - x, 0.) + min1(x - x1, 0.) \
+ max1(x - x4, 0.) + min1(x5 - x, 0.)) \
/ delx;
return(result);
}

/*=====
return normalized green component
=====*/
float mag_green(float x)
{
float result;

result = (x + min1(x1 - x, 0.) + min1(x3 - x, 0.) \
+ max1(x - x4, 0.)) / delx;
return(result);
}

/*=====
return normalized red component
=====*/
float mag_red(float x)
{
float result;

```

(continued)

radial coordinate. euh is just such a vector. It is determined simply by adding 1/2 to the hue if the hue is less than or equal to 1/2, or subtracting 1/2 from the hue if the hue is greater than 1/2.

Next, set pa 1 determines the maximum saturation level, sat 0. Due to the double cone structure of the model, sat 0 is a function of lightness. At a lightness of 0 or 1, sat0 must be 0, and at a lightness of 1/2, it must be 1. In a fashion similar to the making of the functions for RED, GREEN, and BLUE, you make use of two linear functions and a MIN function to create the desired function

```
sat0 = 2*lite
      + min1((-4*lite)+2,0)
```

The hue value is systematically passed to mag_blue, mag_green, and mag_red to calculate blue, green, and red values for the hue, and the euh value is also passed to calculate blul, grenl, and redl values for the hue complement, euh. Functions max 1

Listing 1-continued

```

result = (max1(x - x2, 0.) + min1(x3 - x, 0.) \
          + min1(x5 - x, 0.)) / delx;
return(result);
}

/*=====
return maximum of two floats
=====*/
float max1(float arg1, float arg2)
{
float result;

result = arg1;
if (arg2 > arg1)
result = arg2;
return(result);
}

/*=====
return minimum of two floats
=====*/
float min1(float arg1, float arg2)
{
float result;


result = arg1;
if (arg2 < arg1)
result = arg2;
return(result);
}

```

MAGNUM OPUS CUSTOM ELECTRONIC ENGINEERING

SINGLE BOARD COMPUTERS EPROM PROGRAMMERS

ASSEMBLY
HIGH LEVEL
LANGUAGES

 

- Circuits
- Systems
- Products
- Services
- Assembly
- Repair
- Test

- Analog
- Digital

• Microprocessor

• Engineering

• Manufacturing

• Standard • Custom • Semi-Custom

284 Kennedy St • Iselin, NJ 08830
(908) 283-4925

PLIX™ HARDWARE X-10™ TRANSCEIVER CHIP

Micomint introduces its new Power Line Interface for X-10. Plix is an 18-pin ASIC chip that automatically handles all the specialized X-10 timing and bit-shuffling between a computer and a TW523 power line module.

- ✱ Complete interface between parallel port and TW523 or PL513 modules
- ✱ Performs all X-10 transmit and receive functions
- ✱ Detects AC power loss
- ✱ Simple interface and timing -- operates even in interpreter BASIC
- ✱ Low power -- only 1.8 mA @ 5 V

PLIX chip and
data sheet \$20
100 qty. OEM \$12


PLIX EVALUATION BOARD

To speed your evaluation, we have produced a low-cost Plix interface that plugs into a parallel printer port. The Plix-EKit includes • Plix chip and data sheet, PCB with all components, application note, and PC-compatible software on diskette.

Call 1-800-635-3355
or Write for a Plix data sheet

SPECIAL INTRODUCTORY PRICE
\$29.00

 Add \$20 for TW523 X-10 transceiver module
(sold with Plix-EKit only)



MICROMINT, INC.

4 PARK ST., VERNON, CT 06066
(203) 871-6170 FAX: (203) 872-2204

X-10 is a trademark of X-10 (USA), Inc.

Listing 2—The setpal routine transforms HLS values to RGB and calls the video BIOS to load VGA registers with the RGB values.

```
#include <dos.h>
#define VIDEO_IO 0x10

float delx = 1./6., \
        x1 = 1./6., \
        x2 = 1.13., \
        x3 = .5, \
        x4 = 2.13., \
        x5 = 5.16.;

union REGS regs;

int setpal(float hue, float sat, float lite, int reg)
/*=====
convert. HSL coordinates to RGB
call s set_reg to load VGA hardware with palette data
=====*/
{
void set_reg(int reg, int red, int green, int blue):
float mag_blue(float), mag_green(float), mag_red(float);
float max1(float arg1, float arg2);
float min1(float arg1, float arg2);

float ITENO = 63; /* Max VGA intensity */
float red, green, blue;
float red1, green1, blue1, euh, sat0;

if (hue <= .5) /* hue compliment (euh) */
    euh = hue + .5;
else
    euh = hue - .5;

sat0 = 2. * lite + min1((-4. * lite) + 2., 0.);
sat0 = max1(sat0, 0.); /* max sat = f(lite) */
sat0 = min1(sat0, 1.);

blue = mag_blue(hue);
blue = max1(blue, 0.);
blue = min1(blue, 1.);

blue1 = mag_blue(euh);
blue1 = max1(blue1, 0.);
blue1 = min1(blue1, 1.);

blue = ITENO * lite * (blue + (1. - sat*sat0) * blue1);

green = mag_green(hue);
green = max1(green, 0.);
green = min1(green, 1.);

green1 = mag_green(euh);
green1 = max1(green1, 0.);
green1 = min1(green1, 1.);

green = ITENO * lite * (green + (1. - sat*sat0) * green1);

red = mag_red(hue);
red = max1(red, 0.);
red = min1(red, 1.);

red1 = mag_red(euh);
red1 = max1(red1, 0.);
red1 = min1(red1, 1.);

red = ITENO * lite * (red + (1. - sat*sat0) * red1);

set_reg(reg, (int)red, (int)green, (int)blue);
}
}
```



REAL-TIME MULTITASKING KERNEL

8086/88, 80x86/88 80386
Z80, 64 180, 8080/85 68000/10/20

- Fast, reliable operation
- Compact and ROMable
- PC peripheral support
- DOS file access
- C language support
- Preemptive scheduler
- Time slicing available
- Configuration Builder
- Complete documentation
- Intertask messages
- Message exchanges
- Dynamic operations
 - task create/delete
 - task priorities
 - memory allocation
- Event Manager
- Semaphore Manager
- List Manager
- Insight™ Debugging Tool

THE BEST

Join over 1000 developers such as
IBM®, Xerox, Hewlett Packard,
Hayes, Hughes Aircraft and NASA.

CHOOSE AMX

The best low-cost, high-performance
real-time multitasking system
available today.

No **Royalties**
Source Code included

Demo Disk and
Manual only \$85 US Call for prices for
AMX 86 \$3000 US other processors.
(Shipping/handling extra)

IBM is a registered trademark of IBM Corp.
Z80 is a trademark of Zilog, Inc.
AMX, AMX 86, InSight are trademarks of
KADAK Products Ltd.

KADAK Products Ltd.

206-1847 West Broadway
Vancouver, B.C., Canada
V6J 1Y5

Telephone: (604) 734-2796
Fax: (604) 734-8114

#134

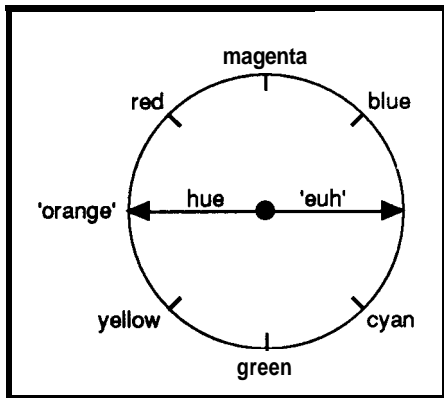


Figure 3—Taking a horizontal slice through the center of Figure 1 shows the "euh," or tie complement of the hue, which is necessary to determine saturation.

and min 1 are used to keep returned values within range.

The RGB components of euh are modified by $(1 - \text{sat} * \text{sat}0)$ to establish the correct radial magnitude of the RGB components of hue. If $(1 - \text{sat} * \text{sat}0)$ is 1, hue and euh will cancel each other, the hue radius will be 0, and the resulting color will be a gray tone.

Finally, each component is multiplied by an intensity value, mapping the RGB values into video hardware space. The VGA is an 18-bit color device. It uses 6-bit values for RED, GREEN, and BLUE. Hence, the range for any component is 0-63. The float variable I_TEN0 is used to hold the value 63. The net intensity is simply

I_TEN0 times the lightness, or in setpal, the variable lite.

Defining the color for a VGA register is most easily done by making the video interrupt BIOS INT 10 call [2]. Listing 3 shows the C code for the subroutine set_reg, which uses the Microsoft C in t86 function to make such a call. All values used by the BIOS calls must be integers, so each color is cast with the i n t type when set_reg is called and then recast as unsigned chars before being loaded into the reg s union structure.

Inside set_reg, two BIOS calls are made. The first call sets the palette register with an attribute. In this case, I have made the attribute equal to the register value. The second call loads the register with the RGB values. To use the color, a program need only make the appropriate graphics library call to use the color defined by the attribute. In Microsoft C, the call would be _setcolor(attribute).

EXTENDED HLS

If you haven't already noticed, the HLS model I just described lacks the ability to define really bright or really dark colors. Before the colors can get bright or dark, they are unsaturated to the point of being either pure white or pure black. This step is because of the double cone structure of the model.

Listing 3—The function set_reg is used to define a color for a VGA register.

```
void set_reg(int reg, int red, int green, int blue)
/*=====
 BIOS call to set color in VGA 640x480/16 color mode
 1) selects register and attribute
 2) sets color
=====*/
{
    regs.h.ah = 0x10;          /* set palette register */
    regs.h.al = 0x00;
    regs.h.bl = (unsigned char) reg;
    regs.h.bh = (unsigned char) reg;

    int86(VIDEO_I0, &regs, &regs);


    regs.h.ah = 0x10;          /* set color register */
    regs.h.al = 0x10;
    regs.h.bl = (unsigned char) reg;
    regs.h.ch = (unsigned char) green;
    regs.h.cl = (unsigned char) blue;
    regs.h.dh = (unsigned char) red;

    int86(VIDEO_I0, &regs, &regs);
}
```

VMAX[®]
TOTAL PACKAGE PERFORMANCE
QUALITY PRODUCTS
RESPONSIVE SERVICE
RELIABLE DELIVERY


SOLID STATE DISK - \$124*

 ½ Card 2 Disk Emulator
 EPROM, Flash and/or SRAM
 1 Meg Total, Bootable




TURBO XT WITH FLASH DISK - \$266*

 2 Serial, 1 Parallel Port
 Up to 2 Flash Drives, 1 Meg Total
 Software Included, 2 Meg DRAM



386DX Complete CPU - \$1099*

 40Mhz, IDE, FDC, SVGA
 1Par, 2Ser (232/422/485), Cache
 Solid State Disk-2 drives to 1.5 Meg



All Tempustech VMAX[®] products are PC Bus Compatible. Made in U.S.A., 30 Day Money Back Guarantee *Qty. 10, Ok, Call for Quantity Pricing

TEMPUSTECH, INC.

TEL: (800) 634-0701

FAX: (813) 643-4981

Fax for 295 Airport Road
 fast response! Naples, FL 33942

#136

In the extended **HLS** model, each cone is converted into a cylinder. Now when **LIGHTNESS** goes from 0 to 1, the colors don't get washed out. Black and white occur only when saturation is 0. In effect, an increase in the number of colors possible given by the ratio of the volume of a cylinder to that of a cone has been realized. This ratio of 3 means an additional 174,762 colors for the VGA without any loss of concept. In fact, the only change to the code in Listing 2 needed is to define **S** at 0 as 1, or better yet, leave it out altogether.

SOME EXAMPLES

Having color defined in an **easy-to-understand** and dimensionless coordinate system means that not only can a single color be defined easily, usually on the first try, but that a complicated color spectrum from shocking pink to pastel green can be defined with simple analytic functions. Listing 4 shows several examples that illustrate the compactness of code needed to define an array of colors and the versatility of the **HLS** model.

Example 1 traverses all the colors of the rainbow in pastel shades. To achieve the pastel effect, the intensity and saturation variables are set to 1/2. The for loop divides the hue into equal intervals between 0 and 1.

Example 2 creates a gray scale. **SATURATION** is set to 0 outside the for loop. **LIGHTNESS** is graded between 0 (black) and 1 (bright white) within the for loop. Any value of hue can be used since **SATURATION** is 0.

Example 3 strives to define a palette that will elucidate the physics of a scientific calculation. In this case, the physics is the plastic strain in a simulation of an aluminum pellet striking an aluminum satellite bumper shield at 6.5 kilometers per second. **Zeus** hydrodynamic computer code [3] performed the simulation.

Whipple [4] first proposed using satellite bumper shields for protecting spacecraft. Orbital velocities of micrometeorites or relics of yesterday's space missions vary from a few to tens of kilometers per second. At those velocities, even gram-sized particles can pack the wallop of a 30-

Listing 4—Several **examples** serve to show the compactness of code needed to define an array of colors and the versatility of the **HLS** model.

```
#include <graph.h>

main()
{
#define MAXREG 15

int setpal(float hue, float sat, float lite, int reg);
void draw_graphic();
void key_wait();
int reg_error = 0;
float hue, sat, lite;

    _setvideomode(_VRES16COLOR); /* VGA 16 color */

/*=====
   Example 1: blue to blue with pastels
   =====*/

    lite = .5;
    sat = .5;
    for (reg = 1; reg <= MAXREG; reg++){
        hue = (float)(reg - 1) / (float)(MAXREG - 1);
        if (error = setpal(hue, sat, lite, reg))
            goto error-handler;
    }
    draw_graphic();
    key_wait();
    _clearscreen(_GCLEARSCREEN);

/*=====
   Example 2: grayscale
   =====*/

    hue = 0.;
    sat = 0.;
    for (reg = 1; reg <= MAXREG; reg++){
        lite = (float)(reg - 1) / (float)(MAXREG - 1);
        if (error = setpal(hue, sat, lite, reg))
            goto error-handler;
    }
    draw_graphic();
    key_wait();
    _clearscreen(_GCLEARSCREEN);

/*=====
   Example 3: blue to orange w/ increas sat and lite
   =====*/

    hue = -.0428;
    sat = .6 - .0285;
    lite = .3 - .0214;
    for (reg = 1; reg <= MAXREG; reg++){
        hue += .0428;
        sat += .0285;
        lite += .0214;
        if (error = setpal(hue, sat, lite, reg))
            goto error-handler;
    }
    draw_graphic();
    key_wait();
    _clearscreen(_GCLEARSCREEN);

error-handler:
    _setvideomode(DEFAULT);
    if (error) printf("setpal error # %d", error);
}
```


mm canon. An inexpensive, thin-walled sacrificial plate, or bumper, is used to intercept the particle. The shock wave stress caused by the collision is high enough to vaporize the particle so the debris carried downstream cannot harm the vehicle.

The palette definition begins with *HUE* set to blue (a subjectively cool color) and ends at orange (a subjectively hot color). *SATURATION* and *LIGHTNESS* vary linearly at different rates as *HUE* goes from blue to orange. This feature emphasizes the change in intensity. When you apply *HLS* to the problem, a tapestry of science and art allows a magnificent visualization of the event.

Other analytic functions produce different effects. Part of the fun with the *HLS* model is just experimenting with different functions. Creative functions lead eventually to a library of function definitions that might aptly be called color effects. With a little practice, you will find that going from periwinkle to thistle is both easy and fun. □

James R. Furlong is a research scientist with a defense-related organization in Arlington, VA. He develops constitutive models for materials undergoing shock used in large-scale hydrodynamic computer codes. He is also head of software development for Eclectic Systems in Springfield, VA.

REFERENCES

1. *Tektronix 4107/4109 Programmer's Manual*, Appendix E, 1982.
2. *IBM Personal System/2 Display Adapter Technical Reference*, International Business Machines Corporation, 1987.
3. *ZeuS: Technical Description and User's Manual*, Computational Mechanics Consultants Inc., Baltimore, MD, 1990.
4. F. Whipple, *Meteoric Phenomena and Meteorite: The Physics and Medicine of the Upper Atmosphere*, University of New Mexico Press, Albuquerque, NM, 1952.

SOURCE

Readers interested in experimenting with the *HLS* model may contact Eclectic Systems for a free copy of the utility "MYPAL." *MYPAL* is an interactive program used to define palettes in *HLS* space. *HLS* coordinates are saved in ASCII files. Programs that read these files can use the source code given in this article to set their own palettes. *MYPAL* is available in DOS and Windows formats. A nominal fee to cover shipping and handling will be requested.

Eclectic Systems
8 106 St. David Court
Springfield, VA 22 153

IRS

413 Very Useful
414 Moderately Useful
415 Not Useful

68HC705K1

REAL TIME In-Circuit Emulation

An add-on board, with re-created 68HC705K1 interrupt logic and 64 bit PEPROM in hardware, converts the 68HC05P8 EVS into a complete 68HC05 K family real time ICE, not a simulator. Comes with user friendly PC driver software, 16 pin emulator cable and plug. (Demo disk: \$5.00)
Part number: EVSK1-ICE Price: \$68.05

68HC11 A,D,E,F1

- PC based user friendly real time 68HC11 ICE.
- New 64K memory module supports different probes.
- Active probe reduces propagation delay to target system.
- Full speed up to 20 MHz, single chip and expanded modes.
- On-board 64K emulation RAM maps to 4K blocks.
- 64K real time hardware breakpoints.
- Breaks on address, address range and memory RD/WR.
- Full symbolic debugging. Supports all A,D,E, and F1 parts.
- 40 pin logic analyzer connector.
- 64K memory module \$295.00
- Probe (with PC driver) \$450.00
- 44 PLCC to 40 DIP adapter \$55.00
- 52 PLCC to 48 DIP adapter \$55.00

Wytec

Suite 238
360 W. Schick Road
Bloomington, IL 60108


FRANCE distributor:
L.S.I.T. CO. Tel: 33 6185 57 67

(708) 894-1440

Z8

WICE Z8 emulator \$995
86C08 adapter w/analog comparators \$55

 8051, 8096, 68HC11, 68332 SINGLE BOARD COMPUTERS



We feature a series of single board computers for process control applications. Each is available as a bare printed circuit board, or fully assembled and tested. Optional development software is also available. Please contact us to discuss your requirements and receive a literature package covering technical specs and pricing.

ALLEN SYSTEMS

2346 Brandon Road • Columbus, OH 43221
(614) 488-7122

Driving Multiple VGA Monitors

Monitor extenders costing hundreds of dollars are available that allow you to drive multiple monitors with a single display adapter. Michael uses just a touch of ingenuity to bring down the price considerably.

SPECIAL SECTION

Michael Swartzendruber

a

t times, driving more than one monitor from a single PC video port is practical

or necessary. Software demonstrations or other kinds of group demonstrations are examples of one type of occasion. Side-by-side comparisons of different brands of monitors are another. Also, certain artistic displays work best when more than one monitor displays an image.

Multiple-monitor drivers that drive from two to sixteen monitors simultaneously are currently available. These devices start at about \$300 and go up in price depending on the number of monitors the device can drive. However, the simple circuit I describe here is an alternative that addresses these problems at a much lower cost. I built the "core" of this circuit with three low-cost transistor chip arrays and a handful of resistors.

Moreover, you can duplicate the core ad infinitum to drive as many monitors as demanded by the task at hand.

THE CIRCUIT

Figure 1 shows my multiple-monitor driver. This simple device implements any number of parallel emitter-follower amplifiers, which serve three essential purposes. The first is to provide a properly terminated load to the video card in the computer. Second, these amplifiers serve as isolation amplifiers between the PC video card and the multiple monitors being driven from the video source. The third purpose of these amplifiers is to provide drive current to the inputs of the monitors connected to the circuit.

Notice that the base of the driver circuits' transistors connect to ground through a 75-ohm resistor. As I mentioned before, this resistance is provides the proper amount of load resistance to the PC video card. The base of each monitor's driver-amplifier connects to this point. The multiple bases connected to this resistor do not alter the 75-ohm termination resistance appreciably, allowing multiple emitter-followers to be driven from the video card. In turn, this feature is what allows the PC video card to drive multiple monitors.

The amplifiers serve as isolation amplifiers between the video card and the monitors by the isolatable charac-

 


Photo 1—Driving multiple monitors from a single VGA display adapter doesn't have to be expensive

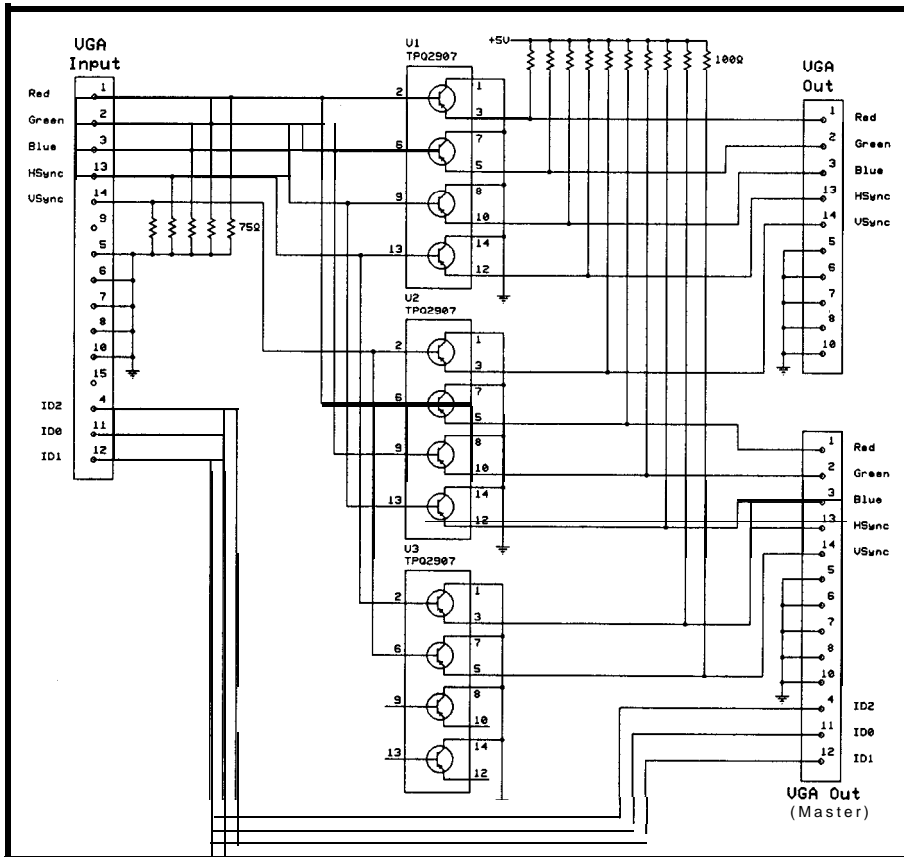


Figure 1--The TPQ2907 quad transistor peck is the key to the multiple monitor driver circuit.

teristics of an emitter-follower amplifier. As mentioned above, the PC video card only "sees" 75 ohms of load resistance no matter how many bases connect in parallel at this point. The emitter of each transistor follows the voltage level of its base, which makes the emitter circuit the signal source to the monitor connected to it. At this point, the signals are directly derived from the video card.

The emitter-follower circuit provides load current that drives the monitor inputs. This drive current is provided by the collector emitter circuit and does not require any significant level of load current from the base circuit. Therefore, you can use this circuit to connect multiple monitors without affecting the load current the video card must supply.

The combination of all of these simple factors allows this circuit to operate. If you need more monitors, simply connect more transistors' base leads to the 75-ohm resistors. Then just build the same "core" over again for each monitor.

1802	6800	8041	COP400
3870	6801	8048	COP800
4004	6805	8051	SUPER8
6301	6809	8085	Z8
6502	68HC11	8096	Z80
64180	78C10	89700	MORE...

Cross-I 6 Meta-Assembler: US\$99 / CN\$119

XDASM Cross-Disassembler: US\$249/CN\$299

- Both MS-DOS products include support for ALL of the above processor families.
- EPROM emulators and Forth compilers too!
- Request our catalog.
- Credit cards are billed in Canadian dollars (CN\$).
- Canadian residents please add 7% G.S.T.


Universal Cross-Assemblers

P.O. Box 6158
Saint John, NB, Canada
E2L 4R6

Voice / Fax: (506) 847-0681



ROMDISK™

 

High Performance Multimegabyte Disk Emulators

NEW MODELS / LOWER PRICES

- Floppy Drive and multimegabyte emulators for ISA bus computers
- 180K to 14 MB capacities
- EPROM, Flash or SRAM technologies
- Autobooting, Single or Dual disk emulation under PC or MS DOS
- List prices from \$195

CURTIS, INC.

418 W. Country Road D. St. Paul, MN 55112

612/631-9512 FAX 612/631-9508

PC DOS is a trademark of IBM; MS DOS is a trademark of Microsoft

I designed this particular version of the circuit to work with the standard VGA D-type 15-pin connector. You can easily change the circuit to have it work with any other color video monitor standard as long as the Red, Green, Blue, H-Sync, and V-Sync signals can be identified. These signals would be input into the core circuit in exactly the same manner. The outputs of the circuit could then be connected to the appropriate pins of the connector for that color monitor standard.

Note the signals are identified as *ID0*, *ID1*, and *ID2*. The VGA monitor provides these signals to the video board for input. They identify a monitor's type to the VGA board, and the video board uses this information during its power-up automatic mode-setting operation.

In order for this operation to finish correctly and without conflicts, only one monitor should provide these signals. Therefore, if you use multiple cores, only one port should pass these signals to the VGA board. The one port that has these signals connected

through it will be named the *master monitor port* because the monitor connected to it will be used to set the power-up mode of the video card.

Connect the lowest-performing monitor to the master monitor port to ensure all monitors connected to the other ports are capable of operating. If you use the highest-performing monitor as the master, some monitors may be incapable of performing at the master's mode. Another way to operate this circuit with monitors that support different resolution levels or capabilities is to leave *ID0*, *ID1*, and *ID2* on all ports disconnected and issue manual video mode-setting commands to the video board.

CIRCUIT USE

This circuit is very easily installed and used. Connect the PC video port to the input port of the circuit assembly, then the monitors to its video output ports. The only restriction is connecting the lowest-performing monitor to the master monitor port, although even this recommendation is

not absolute and depends on your application or your ability to issue video mode-setting commands.

CONCLUSION

This easily built and usable circuit is a great help on those occasions where driving multiple monitors is necessary. A very low cost makes it the most sensible option when compared with similar devices, most of which are offered for sale at about 500 times the cost to build this device. This card has many more applications than the small number I've suggested. Just having a device like this one on hand reveals a whole new world of computing possibilities. □

Michael Swartzendruber is currently employed at System Integrators Inc., where he works with LAN design and Macintosh programming.

IRS

- 416 Very Useful
- 417 Moderately Useful
- 418 Not Useful

8051 EMBEDDED CONTROLLERS WITH ALL THE EXTRAS!


We offer a full line of low cost 80C32 embedded controllers and software tools. They are ideal for developing products, test fixtures and prototypes.

Features include:

- Low power CMOS design
- RS-232 and RS-485 ports
- Up to 60K of code space
- Up to 60K of data space
- 5 to 15 volt operation
- Small form factor (3.5" * 6.5")
- System diskette includes application notes and an assembler.
- Start at \$100

Available Options:

 - Real Time Clock
- Watch Dog Timer
- Multifunction Board adds LCD, Keypad, UART, A/D and 24 I/O lines.
- BASIC-52 or Monitor/Debugger in EPROM
- C Compiler, \$100



Iota Systems, Inc.

POB 8987 • Incline Village, NV 89452
PH: 702-831-6302 • FAX: 702 831-4629

#141

PC BOARDS

- 24 hr. d.s./72 hr. m.l.
 - Prototype to Production
- FR-4, Plated-Thru Teflon, Polyimide
UL Recognized



I.M.P.A.C.®




Call us for an instant quote
24 -hr.modem for easy transfer of
Drill & CAD files.

Free Tooling On First Order!
(up to \$200)

Superior Quality at Competitive Prices!

CAPITAL ELECTRO-CIRCUITS

 7845-J Airpark Road
Gaithersburg, MD 20879
(301) 977-0303
Fax: (301) 990-6715



#142

DEPARTMENTS

64 Firmware Furnace

74 From the Bench

80 Silicon Update

88 Practical Algorithms

95 ConnecTime

FIRMWARE FURNACE

Ed Nisley

Extending Your Control: The HCS II MCIR-LINK

Since the introduction of the HCS II home control system, one of the most requested new features has been the ability to send IR codes to consumer electronic equipment. The new MCIR-Link makes those requests reality.



If you wish hard enough, it will come true" is an aphorism often attributed to the Walt Disney School of Engineering. But at least in the wonderful, malleable world of firmware, wishes sometimes do come true!

Back in issue #25 of the *Computer Applications Journal*, Steve, Ken, and I introduced the Home Control System II (HCS II). The system is based on a Supervisory Controller, which handles all the grisly scheduling and oversees the whole system, and networkable "Link" modules, which expand the system I/O by adding digital I/O ports, LCD display, X-10 power-line control, and more. I've been steadily covering all those network modules in the last few issues.

Back in issue #26's "Firmware Furnace," entitled "Infrared Home Control Gateway," Steve and I presented the IR-Link module as a command and control gateway into HCS II. It received and transmitted infrared signals in the 9-bit Motorola MC145030 format and included enough features to implement IR badges, people tracking, and so forth and so on. Refer to that issue for a complete IR-Link schematic and discussion of the hardware and firmware.

HD addr	dump MCIR data from RAM to HEX w/base addr
HR	receive MCIR data from HEX to RAM
SM n	send MCIR signal n (1-999 RAM, 1001-1999 EPROM)
Tn	train new MCIR code, store in RAM as n (1-999)
TD n	set duty cycle correction factor 0-255
TX	clear MCIR data from RAM

Figure 1—The MCIR-Link firmware adds these commands to the IR-Link's repertoire. Unlike the other Link modules, the new H commands transfer Intel hex data directly between the host computer and the MCIR-Link's RAM.

However, sending commands to the HCS control program with an IR remote wasn't enough for you. What you really wanted was to send IR commands from the HCS to your TV/VCR/CD/amp widgets. The IR-Link seemed to have all the essential hardware, so it ought to be a simple matter of software. Right?

The MCIR-Link module is our response to your requests. In addition to all the IR-Link functions, it can record and play back the IR signals sent by most hand-held remote control units. The initial training must be done manually (you need a finger to push the remote's buttons!), but transmission is entirely automatic and can be handled by the Supervisory Controller's XPRESS program. The MCIR-Link board's 32K-byte RAM has enough room for several hundred remote control signals, so you can control nearly anything.

Figure 1 presents the new MCIR-Link commands; the complete IR-Link set is given in "Infrared Home Control Gateway" in issue #26. You simply teach the MCIR-Link new IR signals using the T command and send them with the SM command. The H commands allow you to dump and restore the IR data, so you can save your work on disk and program it into EPROM.

As with all the other "-Links," you will need a PC with a terminal emulator program to drive the MCIR-Link in the interactive mode. Also like previous modules, this board and firmware can be used in applications that have nothing to do with HCS II. The Links use a straightforward ASCII command set over standard RS-232 or RS-485 wiring; therefore, you can drive this board manually with a terminal emulator, a simple PC program, or your own home control system.

That's about as complex as the user interface gets, so I won't say much more about it. Instead, I'll explore the MCIR-Link firmware and describe some of the gotchas that make IR control such a

challenge. Along the way, you'll discover techniques for your own projects and, perhaps, find new respect for your TV set's lowly remote control receiver.

REMOTES UNCONTROLLED

The first step in any project should be figuring out what you need to do. What you need to do here is add to your home control system the capability to recognize the IR signals of the devices you wish to incorporate, which you do by training the MCIR-Link with the remotes. To begin, a quick review of the basics of IR

frequency. The first chunk may have a long, lead-in burst to wake up the receiver. In some cases, this burst pulls the link out of a power-down deep sleep mode, but usually it is just a way to distinguish an incoming signal from the background clutter.

Each manufacturer uses a different scheme to stuff bits into the IR signal. In fact, two remotes from the same manufacturer may use different encodings, although this inconsistency is less of a problem now that complex A/V systems are the norm rather than the exception. In principle, this variability reduces the chance that an IR signal will trigger the wrong remote, but in practice, it's a source of confusion for those of us trying to make sense of everything.

Some [mostly older] remotes use unmodulated pulses, simply turning their IR LED on to send a pulse and off when it is done. These units tend to be more sensitive to interference from stray IR because there is no way to

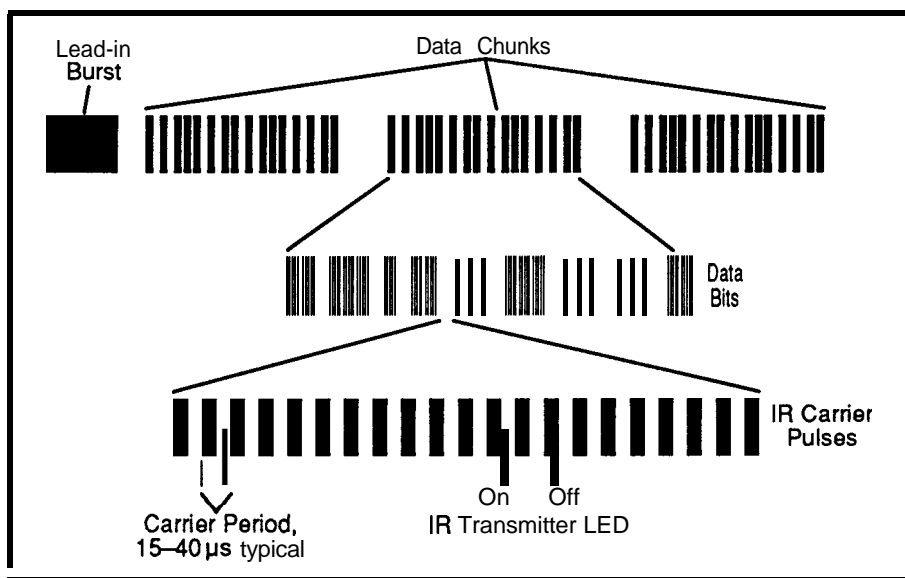


Figure 2—Although remote controls use many different techniques to encode their information into the infrared signals, this sketch illustrates some of the common features.

controls is in order, although you should be reasonably familiar with them from articles about the original Master Controller, the IR-Link, and similar projects.

Most infrared remote control units use modulated IR signals, as shown in Figure 2. An IR signal is made up of large chunks (for lack of a better term) containing bits, which are bursts of IR pulses at a (usually) constant carrier

distinguish a glitch from a real bit. However, even these units do not have a universal bit encoding method.

Photo 1 presents a rogue's gallery of IR signals taken from a shopping-bag-full portion of Steve's remote control collection. Notice the different horizontal sweep speeds required to capture the signals, the number of bursts in each chunk, the timing variations, and the characteristic some

 


Photo 1-Common *hand-held IR remote control units* use a *vast array of coding schemes and timings*. The scope was set for *20 ms per division* on the top trace in all six photos. The bottom trace was set for *10 ms per division* in the top four photos, *5 ms per division* in the bottom left photo, and *2 ms per division* in the bottom right photo. Also note the differences in repeat rate among the remotes.

remotes have of not repeating the same chunk over and over.

How to capture, store, and replay this wonderful variety of signals?

GROUND RULES

The IR-Link board "sees" infrared signals through a Sharp **IS1U60** receiver that expects bursts made up of **IR** pulses repeating at a **38-kHz** rate. While it can handle other carrier frequencies (roughly 25-60 **kHz** for very strong signals), its internal **bandpass** filter reduces the sensitivity, so the maximum distance drops off dramatically as the frequency varies from **38 kHz**. The output is a **low-going** pulse starting 50-100 μs after the **IR** burst begins and ending 100-300 μs after the signal shuts off. The specification sheet is silent about actual timing limits, but it's reasonable to assume the turn-on and turn-off delays depend on the signal strength, carrier frequency, background light level, and, most likely, the phase of the moon.

Steve designed the IR-Link's output circuitry to produce the data format used by the MC145030 remote control encoder-decoder chip. The Manchester bit cell timings are controlled by firmware interrupt routines, and a **38-kHz** oscillator modulates the outgoing signal. Bypassing the modulation is impossible, although a **trimpot** adjusts the modulation frequency around **38 kHz**.

In effect, the hardware converts between real-world modulated **IR** bursts and firmware-timed binary pulses. As long as the remote control signal looks roughly like those shown in Photo 1, the firmware should be able to both record and reproduce it.

Some restrictions exist, though. Unmodulated **IR** signals, such as those used by many General Instrument (Jerrold) **CATV** decoder boxes, cannot be received by the **IS1U60** or transmitted by the IR-Link hardware. Signals modulated with carriers far from **38 kHz** may not pass through the **IS1U60**

without timing distortion and may also fall outside the IR-Link transmitter adjustment range.

Each **IR** burst must include several **38-kHz** modulation cycles, which means that it must be longer than a few hundred microseconds. No upper limit exists, but based on the remotes I've examined, a few tens of milliseconds is reasonable. The **IS1U60** data doesn't include precise timings, but it does respond to signals in that range.

Because a single cycle of **38-kHz** modulation requires about 26 μs and the **IS1U60** response time specifications are extremely vague, recording the burst times to the exact microsecond is pointless. As you will see later, this flexibility allows a data compression method capable of reducing the stored data by roughly a factor of two.

GOING ON RECORD

Recording a **IR** signal using the MCIR-Link is simple, at least in principle. You start a timer on the

leading edge of the first pulse and record the time of each successive edge. The two pairs of times for each pulse (the ON and OFF durations) should be sufficient to reproduce the pulse. Unfortunately, the 8031 does not include a timer that can be controlled by an external signal in that manner, so it's done with firmware.

Because I was already using Timer 0 to send and receive the IR-Link's MC145030 pulses, adapting it to the MCIR-Link functions made sense. Timer Mode 1 selects a 16-bit up-counter clocked at 1.0851 μ s (for an 11.0592-MHz crystal) and the TR0 bit enables and disables the clock signal to start and stop the timer.

Starting is no problem; just wait for an input pulse from the IS1U60. This step is somewhat complicated because you do not want to hang the system if you decide not to send a signal, so I used a short loop that bails out if a character shows up at the serial port. But as the saying goes, "The trouble with doing nothing is it's hard to know when you're done for the day." When recording IR signals, the trouble is there's no good way to tell when the signal is finished!

After examining all the signals available from the sack of remotes, I decided the only reasonable method was to allow a prolonged period of "silence" to mark the end of a signal.

Unfortunately, several remotes insert delays up to 200 ms between some IR chunks. Given that Timer 0 is clocked at a fixed 1.0851- μ s rate, I had to record 19 bits of timer information to get 569 ms of elapsed duration. That's three bytes per edge, and I had to keep track of the timer overflow while waiting!

Obviously, there must be some upper limit on the number of pulses in each signal. I picked 1000 pulses, which seemed enough by far for any reasonable signal, and allocated a 3K-byte buffer in the MCIR-Link's static RAM. Equally obvious, you should press the remote control's key just enough to generate a complete signal; filling the MCIR-Link's memory with repeated bursts is not a good idea.

Listing 1 shows the heart of the "recording" routine. The RR_cLev variable counts the number of bytes in the serial port receiver ring buffer; if it remains zero, there are no incoming characters. When the IS1U60 detects an IR signal, the IRECEIVE input bit goes low and the loop exits into the timer capture section.

Although the 8031 was designed (and is still touted) as a "Boolean processor," there are a few gaping holes in the instruction set. The exclusive-OR bit operator is conspicuous by its absence, leaving no fast, clean way to detect a single bit change! As a result, two separate "wait for next edge" loops also keep track of Timer 0 overflows and check for the end of the signal.

After an edge occurs, the code shuts off Timer 0, stores both timer bytes as well as the current overflow count, restarts the timer, and checks for the end of the buffer. If all goes well, it returns to the top of the loop and waits for the next edge.


I've listed the duration of each instruction in the three loops to show the overhead involved. Ample time is available after each edge to record the data because the IR pulses are a few hundred microseconds long. However, the code will eventually have to account for the time that transpires while the timer is stopped to record each time stamp, as well as the average loop time overhead.

The Snooper™

Ethernet Protocol Analyzer

for LAN Manager and NetWare LANs

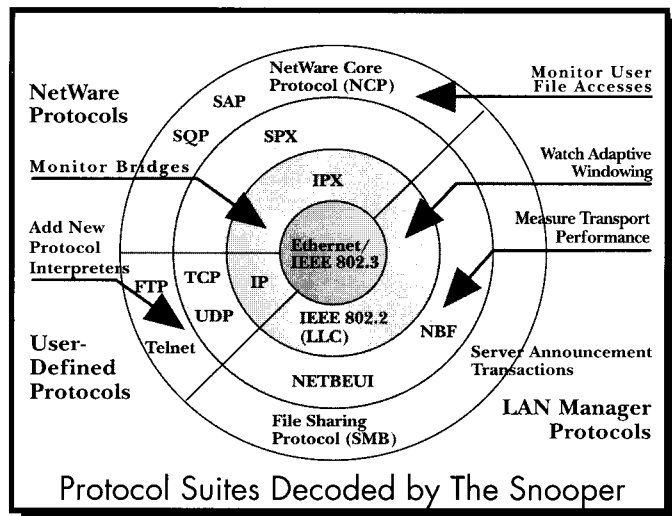Capture and decode live Ethernet traffic with any PC and a garden-variety NIC for only \$350.



Announcing the network manager's dream. Full multilayer decoding of NetWare and LAN Manager protocols, captured live from any PC. Includes ready-to-run DOS-based analyzer, plus full source code (including packet decoding modules in C and assembly). The Snooper easily interfaces to most common NICs through standard packet drivers (supplied in source and binary forms). **CALL TODAY FOR YOUR FREE DEMO DISK!**



GENERAL SOFTWARE™



Tel. (206) 391-4285
Fax. (206) 746-4655
The Protocol Experts

P.O. Box 2571 Redmond, WA 98073

Copyright (C) 1992 General Software, Inc. General Software, the GS Logo, and The Snooper are trademarks of General Software, Inc.

SIGNAL SQUASHING

The only hardware change required for the MCIR-Link function is to substitute a **32K-byte** RAM for the **8K** unit on the IR-Link board. The MCIR-Link code uses the lower **8K** for variables, capture and replay buffers, and so forth, leaving 24K bytes for the remote control IR signals.

Simple division says that if typical signals have 100 pulses at 6 bytes per pulse, then that big RAM has room for about 40 signals. Obviously some data compression is in order!

While deploying an armada of signal processing algorithms against the captured signals would be nice, my plans were straitjacketed by three simple constraints. Whatever method I picked must work reasonably well for all remotes using modulated IR, not take forever to get working, and not displace any IR-Link functions.

I knew that the only practical way to produce accurate arbitrary pulses was to load Timer 0 with a value and wait for it to time-out, because the 8031 has no dedicated pulse generation hardware. Thus, the first data reduction step was to convert the captured times from absolute to relative by subtracting each entry from the previous one (working backwards through the array, naturally!).

The **IS1U60** timing is a little more complex than you might expect because the turn-on and turn-off delays for each pulse are not equal. In other words, although the sum of the ON and OFF times is correct, the pulse appears to be ON longer than it really is. My experiments showed that the correction is about **220µs** for strong signals. The code subtracts that amount from the ON time and adds it to the OFF time as part of the absolute-to-relative time conversion.

As I mentioned, an adjustment is also needed to account for the loop time overheads. However, I managed to match the capture and reproduction loop time overheads, so there was no need for an explicit fudge factor. In effect, the code loses just as much time acquiring the signals as it does playing them back. Think about it.

The next step is to divide all these times by eight, which ensures that the

Listing 1— *This pair of loops waits for the first IR signal, then begins capturing 3-byte time stamps for each edge.*

```

• --- wait for an IR signal or cancel keystroke

    SETB IRECEIVE      : ensure input mode...
    CLR  FOFLAG        : indicate no timeout

?Raw1
    MOV  A,RR_cLev     : 1 monitor serial character count
    LJNZ ?RawDone      : 2 and bail out if any show up
    CPL  HEARTBEAT     : 1 indicate we are alive
    JB   IRECEIVE,?Raw1 : 2 high with no IR signal
    CLR  FlagMCSaveIR  : 1 force memory low to match

*--- hold off interrupts and start timer at zero

    PUSH IE           : 2 save existing interrupt state
    CLR  EA           : 1 shut them off entirely

    CLR  TRO          : 1 reset the timer
    MOV  TLO,#0       : 2
    MOV  TH0,#0       : 2
    CLR  TFO          : 1
    SETB TRO          : 1

*--- repeat for each time entry in array or until signal times out

    MOV  B,#0         : 2 clear wrap counter accumulator

?RawLp
    JB   FlagMCSaveIR.?RawU0 : 2 which bit did we have last time?

?RawD0
    CPL  HEARTBEAT     : 1 indicate we are alive
    JNB  TFO,?RawD1    : 2 check for timeout
    CLR  TFO           : 1
    INC  B             : 1
    JB   B,3,?RawTO    : 2 time out after 8 wraps

?RawD1
    JNB  IRECEIVE,?RawD0 : 2 spin if still down
    SETB FlagMCSaveIR  : 1 remember new bit state
    SJMP ?RawEdge      : 2

?RawTO
    ORL  ErrFlags,#$20 : record for debugging
    SETB FOFLAG        : and force loop exit
    SJMP ?RawEdge      : after normal recording

?RawU0
    CPL  HEARTBEAT     : 1 indicate we are alive
    JNB  TFO,?RawU1    : 2 check for timeout
    CLR  TFO           : 1
    INC  B             : 1
    JB   B,3,?RawTO    : 2 time out after 8 wraps

?RawU1
    JB   IRECEIVE,?RawU0 : 2 spin if still up
    CLR  FlagMCSaveIR  : 1 remember new bit state

*--- edge detected, store current timestamp

?RawEdge
    CLR  TRO          : 1 freeze timer
    MOV  A,B          : 1 pick up wrap counter
    MOV  C,TFO        : 1 incorporate possible wrap
    ADDC A,#0         : 1
    MOV  B,A          : 1 save it for later
    MOV  R4,TLO       : 2

```

(continued)

Listing 1—continued

```

MOV R5,THO          ; 2
CLR TFO             ;1clear timer wrap flag
SETB TR0            ;1and restart it

MOV A,R4            ;store the count in the buffer
MOVX [DPTR],A
INC DPTR
MOV A,R5
MOVX [DPTR],A
INC DPTR
MOV A,B
MOVX [DPTR],A
INC DPTR

*--- decide if we are done yet

JB F0FLAG,?RawEnd  ; force exit on timeout

DecRR              R3,R2
JNZRR              R3,R2,?RawLp
    
```

data will fit in two bytes rather than three. The division, which is implemented as a bit shift, preserves the remainder and adds it to the next time. Thus, each regenerated time may be in error by up to 7 μ s, but there is no cumulative error.

Most of the remote control signals I measured started with a long lead-in pulse and a long delay, then had relatively short bursts in each successive chunk. Chunks might be separated by long pauses, but there were also few cases where long and short delays were mixed together. A simple run-length encoding compression scheme seemed to offer the best trade-off of complexity and efficiency.

The division by eight means that time intervals less than 2.21 ms (255 x 8 x 1.085 μ s) require only one byte. Values longer than that require two bytes, and no values bigger than that

exist (by definition!). Most pulses are shorter than 2.2 ms, so much of the data can be squashed into runs of single-byte times.

I decided to work with pulses rather than individual times. If either time value required two bytes, I assigned four bytes to the pulse. If both could fit into single bytes, the pair took up only two bytes of stored data. In practice, this method works reasonably well, but of course there are some remotes that pair short pulses with long delays.

Figure 3 shows the final data for an actual captured IR signal. The record contains four elements: the record number, the overall pulse count, four bytes for the lead-in pulse, and runs of one- and two-byte pulse times preceded by a one-byte pulse count for each run. The counts may be zero if the data requires more than 255

```


01 00          Block ID Number: 1
1200          Number of pulses: 18
CO 03 F2 01   First pulse ON and OFF times: 03C0 ON, 01 F2 OFF
10           Number of pulses in one-byte format: 16 (32 bytes total)
38 B9 38 B9 37 40 37 40 36 the data...
BA 38 B8 38 3F 37 B9 39 B8
38 3F 37 40 37 B9 38 B9 38
B8 38 B8 39 3F
01           Number of pulses in two-byte format: 1 (four bytes total)
3800 EA ED   Pulse ON and OFF times: 0038 and EDEA (final delay is quite long)
00 00       End markers: two zero bytes
    
```

Figure 3—The firmware stores IR data using run-length compression to encode time values in the least number of bytes. This record was captured from a remote control that uses a long lead-in pulse followed by several shorter pulses.

Real Time Devices

"Accessing the Analog World"

Exciting New Products!

 

AD1200 - \$359

- 12-bit 125 kHz A/D Conversion
- 16 Analog Input Channels
- 3 Timers and 16 DIO Lines
- Supports DMA & Pacer Clock
- AT Bus Version Available!

for AMPRO CPUs

DM200 12-bit 40 kHz 8 channel analog input board; 8254 timer and 16 digital I/O lines \$295

DM406 12-bit 100 kHz 16 channel analog I/O board; 2 D/A outputs; 8254 timer; 16 digital I/O lines; Supports DMA and pacer clock. \$449

DM806 High current digital I/O board; 8254 timer; opto-22 compatible \$195

PC/XT/AT Boards

AD2700 16 channel 12-bit 150 kHz analog input board; Supports DMA, pacer clock and programmable gain; 8254 timer; 16 digital I/O lines; 16-bit AT bus operation. \$525

TC48 Dual Am951 3 Timer/Counters; 24 digital I/O lines; 16-bit AT bus operation with expanded interrupts \$398

DIO24 High current digital I/O board; 24 buffered DIO lines; 8254 timer; Compatible with opto-22 equipment. \$195

AD3110 Super fast 16 channel A/D board! 12-bit 200 kHz A/D rate; Burst mode operation; On board FIFO memory; Programmable gain; Timers; DIO lines; Supports DMA and pacer clock; Optional D/A outputs \$665

AD3710 Low cost version of AD3110 with on board FIFO memory and 200 kHz burst mode operation \$525

DA810 8 channel 12-bit D/A; Voltage or current loop output; 8254 timer; 24 digital I/O lines. \$589

MR16 110 VAC mechanical relay expansion board; Computer control of 16 AC loads. \$215

OP16 Optoisolated 16 channel digital input expansion board. \$225

TS16 16 channel thermocouple expansion board; Supports J & K types. \$298

Unparalleled choices for real world control. Over 50 hardware and software products for single and OEM users.

FREE 80 PAGE CATALOG!

Real Time Devices, Inc.
State College, PA USA



Tel.: 814/234-8087
FAX: 814/234-5218

#144

successive pulses of either type or if the data starts out with more than one long pulse. A pair of zero counts marks the end of each block.

Your mileage will vary, but typical data records weigh in at 70 to 150 bytes, so you may be able to fit 200 IR signals into that RAM, which is probably enough to get you into serious trouble. Think of this collection as the ultimate universal controller with no k&pad!

The original IR Master Controller included a character string with each IR signal, but that unit was intended for stand-alone operation and sported a keypad and LCD panel. The MCIR-Link is designed for computer-driven applications, so I felt that any strings should be stored in the system controller. Each IR signal is identified by a record number between 1 and 999 that takes up only two bytes in the data record.

Although numbers may be cryptic, they suffice for a simple row-column key mapping layout. For example, call upper-left key 11, the key to its right 12, the third key in the fourth row is 43, and so forth. This system breaks down for some recent A/V controllers with shuttle control knobs, but it works like a champ for remotes with vast rectilinear arrays of tiny keys. If you intend to store a zillion keys, write a program on your PC to keep track of 'em, please!

PLAYING DATA

By comparison, playing back the stored data is straightforward. The data records are stored nose-to-tail in RAM, preceded by a two-byte record count and followed by another pair of zeros, so the firmware simply scans through the records to find a matching record number.

Although I could have included an overall record size in each record, I found that scanning through each record and decompressing all the data requires only about 150 μ s per pulse. Again, your mileage will vary, but scanning to the last of 100 records, each with 30 pulses, might take 400 ms. While this may sound excessive,

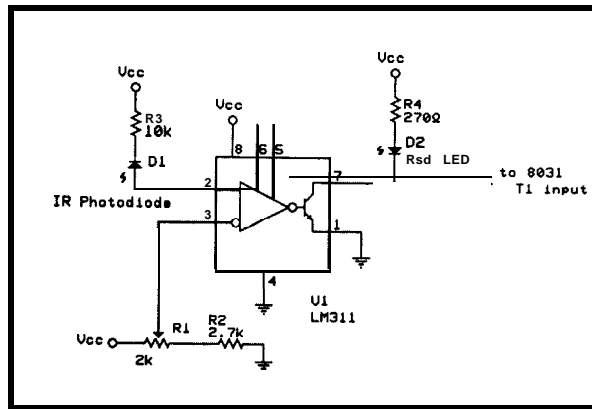


Figure 4—The *IRSAMPLE.C* program uses this circuitry to capture raw IR signals from a remote control without the processing imposed by the normal IS1U60 receiver. Adjust *R1* so the LED is off under ambient light and on for an IR signal.

remember that typical IR signals weigh in around 100400 ms themselves!

The data expands back into the 3000-byte buffer used to capture it in the first place, with each value occupying the low two bytes of each three-byte entry. The values are then multiplied by eight to recover clock cycles, which puts the timer overflow count in the high-order byte. Because the 8031 timers count upward, the time values must be two's comple-

mented: 0123 hex becomes FEDD. Finally, to allow a simple DJNZ loop, the number of timer wraps is incremented.

Once the data is ready, the code simply fetches each time value, loads the two low bytes into the timer, starts it, and counts down the number of timer wraps found in the high byte. As I mentioned before, the recording and playback loops have similar overhead, so the time lost in the former is made up in the latter.

That's all there is to it!

WELL, ALMOST

The good news is that the IS1U60 responds to nearly any modulated IR signal, regardless of carrier frequency, as long as you hold the remote within a few inches of the receiver's lens. Remember that the 38-kHz bandpass filter decreases sensitivity for off-frequency signals, but if you have enough firepower, it doesn't matter how bad the response is.

The bad news is that the IS1U60 also responds when hit with singleton

Listing 2—This section of code from *IRSAMPLE.C* captures the raw IR input signal from the circuit shown in Figure 4 and stores it in External RAM at the address formed by P2 and R0.

```

MOV A, #HIGH(IRBuffer); point to buffer
INC A ; align to next 256 byte boundary
MOV P2, A
MOV R0, # $FF ; start from the top

?IRWait
JB IR_INPUT, ?IRWait ; wait for input bit

?IRTop
MOV C, IR_INPUT ; 1 fetch input
RLC A ; 1 add to byte
MOV C, IR_INPUT ; repeat for full byte
RLC A ; at two cycles per sample
MOV C, IR_INPUT
RLC A
MOV C, IR_INPUT
RLC A
MOV C, IR_INPUT
RLC A
MOV C, IR_INPUT
RLC A
MOVX [R0], A ; 2 save in external RAM
DJNZ R0, ?IRTop ; 2 step to next sample

```

 


Photo 2—The IS1U60 can be fooled by single pulses from unmodulated remotes, so differentiating between good data and trash can be difficult at times.

pulses from unmodulated remotes. Photo 2 shows the response to a low-frequency square wave: a 300-µs pulse each time the IR LED goes ON! I have also seen clusters of two or three pulses for a single unmodulated input pulse. Distinguishing trash from treasure is difficult when they look alike.

I used an oscilloscope and logic analyzer to classify the remotes for this project, but I realize many of you don't have access to that kind of test equipment. To help you decide if MCIR-Link will work with your remotes, I wrote a utility program to capture raw IR data and dump it to the serial port in logic-analyzer format. IRSIGNAL.C runs on a standard IR-Link board [with an 8K RAM in-

stalled), but it requires an IR photodiode to "see" the raw IR signal. Figure 4 shows the circuitry required for this addition. T1 is normally used for the carrier frequency calibration, so make sure you remove IR-Link jumper JP6 as part of the modification to prevent confusion.

Listing 2 is the core of IRSAMPL.E's code to capture 8 bits of data and store each byte into external RAM. Two cycles are needed to capture each bit, two to write a complete byte into RAM, and two more to tick the counter or address register. I think this loop is the fastest one to capture external data that you can pull off; suggestions and improvements are welcome! Note that the bytes are stored "backwards" to allow RO to


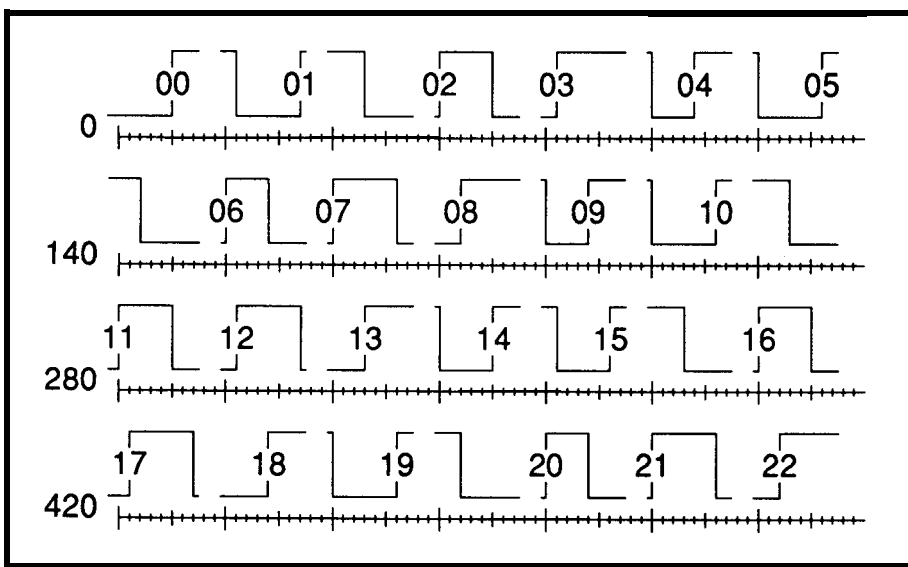


Figure 5—IRSAMPLE.C captures and dumps the first 5.5 ms of raw IR in a logic analyzer format. The gap in the simulated waveform indicates where the firmware stores the data in external RAM. Each vertical tick represents one sample of 2.17 µs.

PC/XT/AT/386 Users!

DIRECT CONNECT™

 A time-cutting approach to plug-in data acquisition



Save valuable project time with ADAC's DIRECT CONNECT™ data acquisition modules. FREE DIRECTVIEW™ Board Tutorial and Data Acquisition software means a shorter learning curve and quicker results. CALL FOR A FREE COW

Thermocouple 8 Channel A/D Board \$650

- Direct Connection to Thermocouple wires and shields
- 0.1°C resolution
- Software selection of JK,TR,S,&B

Strain Gage 8 Channel A/D Board \$795

- Direct Connection to 3 & 4 wire Strain Gages
- 1 µstrain resolution
- Quarter, Half & Full bridge completion
- On-board excitation voltage

RTD 8 Channel A/D Board \$795

- Direct Connection to 4-wire RTDs
- 0.02° C res., 100 ohm platinum
- 1 mA current source per channel

High Resolution 8/16 Channel A/D Board \$895

- 16 bit A/D resolution
- 15 kHz throughput (50 kHz option)
- DMA
- 8 lines digital I/O
- 3 channel counter/timer

Multifunction 8/16 Channel A/D Board \$595

- 12 bit A/D resolution
- 25 kHz throughput
- DMA, Prog. Gain
- 8 lines digital I/O
- 3 channel counter/timer

Many other models available, Call:

I - 800- 648- 6589



70 Tower Office Park, Woburn, MA 01801
FAX (617) 938-6553 TEL (617) 935-6668

8145

serve as both address and counter with a DJ N Z instruction.

Figure 5 shows the first few lines of a 38-kHz signal dump. Each group of ten vertical tics represents one byte of samples, with the two blank sample periods indicating the dead time required to store the eight data bits in RAM. The first IR burst is long enough that all 255 bytes are filled with carrier, but that is precisely the level of detail I RSAMPLE is intended to present.

You can calculate the modulation frequency by finding the elapsed time for 10 or 20 cycles, dividing to get the period of one cycle, then taking the reciprocal to get the frequency. I RSAMPLE enumerates the rising edges to simplify this process: the elapsed time for pulses 10 through 22 is $544 - 252 = 292$ cycles = $3.17 \mu\text{s}$. Dividing by $22 - 10 = 12$ gives $26.4 \mu\text{s}$ per cycle or 37.9 kHz .

Many remotes need a few cycles to "get up to speed," so you might want to skip the pulses in the first line or two when you calculate the fre-

quency. You should also avoid using edges immediately after the timing gaps, such as edge 2 in Figure 5, because the firmware was busy storing the previous byte and could not sample the input bit. That transition may have actually occurred any time in the previous two sample times, so precise timing isn't possible.

Unmodulated IR signals will appear to be straight lines, low while the LED is ON and high for the OFF times. Remember that the MCIR-Link hardware and firmware can't handle those signals.

ON THE AIR

The MCIR-Link EPROM hex file (MCIRB.HEX) is available on the Circuit Cellar BBS for your noncommercial use. The source code is not available, but it may be licensed from Circuit Cellar Inc. (not INK). Contact them for details.

You may also download the complete I RSAMPLE.C source code and I RSAMPLE.HEX for your IR-Link board to check your remotes for

MCIR-Link compatibility. You will need the current version of Dunfield's Micro-C compiler to recompile the code.

Pure Unobtainium has most of the odd parts you need to build the IR-Link and MCIR-Link projects, including the IR photodiode and LM3 11 for the I RSAMPLE.C program. ☒

Ed Nisley is a Registered Professional Engineer and a member of the Computer Applications Journal's engineering staff. He specializes in finding innovative solutions to demanding and unusual technical problems.

SOURCE

Pure Unobtainium
89 Burbank Road
Tolland, CT 06084-2416
Fax/Voice (203) 870-9304

IRS

419 Very Useful
420 Moderately Useful
421 Not Useful

MICROWAVE SENSORS

For non-contact detection of:

- Motion
- Velocity
- Direction
- Point level
- Presence

Our microwave sensors see up to 150 feet through foam, buildup, glass, and non-metallic substances, and are unaffected by environmental conditions. These proven, low cost solutions are available off-the-shelf, or custom made for OEM use.


Call For Your Free
Selection Guide
I - 800-289-261 1

AM Sensors, Inc.
26 Keewaydin Drive
Salem, NH 03079-2839
Phone: 603-898-1 543
Fax: 603-898-1 638



The Circuit Cellar Project File, Volume 1

GET
YOURS
TODAY!

 

The Circuit Cellar Project File, Volume 1 has over 200 pages of new and expanded hands-on projects and tutorials. The Computer Applications Journal's editors have chosen a dozen of the top projects from the Circuit Cellar Design Contest, independent submissions, and topresponse articles to make a book with something for every interest!

now only \$17.95! (includes domestic delivery!)

Order your copy today!

*\$17.95 Visa, Mastercard, Check, or Money Order (US Funds Only)
(Add \$2.00 for delivery to Canada or Mexico, \$4.00 for delivery to other non-U.S. addresses)

The Circuit Cellar Project File, Vol. 1

4 Park Street, Vernon, CT 06066 • Tel: (203) 875-2 199 • Fax: (203) 872.2204

#146

X-10 Interfacing with PLIX

The TW523 might be considered by some to be the perfect X-10 computer interface. The complicated timing can be daunting to many, though. Throw a PLIX chip at the circuit and your troubles may be solved.

FROM THE BENCH

Jeff Bachiochi

Let me see the hands of all the engineers out there who still enjoy getting down on the floor and building forts and castles out of blocks or Legos with the "kids." For some of us, doing such an activity with young children is a successful enough smoke screen to save us from the label "eccentric." Call me what you like, but building a fantasy empire out of wood is just as rewarding as designing a product.

I enjoy using the rules of gravity and balance with good old wooden blocks, and building with Legos has its own reward even though working with them is a bit different. Every task has its own set of rules. An understanding of these rules and a bit of imagination is all you need to do well. The same

concept used in castle construction applies to product design. I guess that's why I enjoy being an engineer. If you choose the correct mix of components, your design will withstand the test of time (or gravity). If not, well that's how we got the term "smoke test."

One of the most widely discussed topics here in the *Computer Applications Journal* (and on the Circuit Cellar BBS) is home control. X-10 control is a favorite subject within this topic. Let me show you how the new PLIX (Power Line Control for X-10) chip can ease you into X-10 control without even breaking a sweat, and why you should consider using a chip to handle X-10 communication in your next design. I think you'll find this blend a perfect one.

WHERE WE'VE BEEN

Many of us have been using X-10 modules for appliance control for over ten years. X-10 Powerhouse remains unchallenged as the leader in power-line carrier transmission control systems. CEBus's PLBus may render X-10's code transmission format obsolete, but its large, installed user base will prevent that from happening any time soon. (For more information see the assorted CEBus articles by Ken Davidson in issues #10, #15, and #21 of *Circuit Cellar INK*.)

 


Photo 1—PLIX simplifies the task of X-10 interfacing by *handling all the complicated liming*.

Housecode	Data	Function	Data	Function	Data
A	6	1	6	All Units Off	16
B	7	2	7	All Lights On	24
C	4	3	4	On	20
D	5	4	5	off	26
E	6	5	6	Dim	16
F	9	6	9	Bright	26
G	10	7	10	All Lights Off .	22
H	11	6	11	Extended Code .	30
I	14	9	14	Hail Request .	17
J	15	10	15	Hail Acknowledge .	25
K	12	11	12	Preset Dim Low .	21
L	13	12	13	Preset Dim High .	29
M	0	13	0	Extended Data .	19
N	1	14	1	Status=On . *	27
O	2	15	2	Status=Off . *	23
P	3	16	3	Status Request . *	31

• denotes not supported by any current X-10 module
 * denotes supported only by the RR501 RF gateway module

Table I-X-10 transmissions always contain a housecode and a function code. The function code either selects a particular module or invokes some action.

The X-10 system can handle up to 256 unique module addresses, but the manual controllers marketed by the company can deal with only eight or sixteen of those at a time. If you have more than sixteen modules in your house, putting them under computer control is the next logical step in making them easier to use.

Although some companies developed X-10 products in the past that used a microcontroller, there was no clean way to connect the controller and the power line. This void limited product development to those companies who could afford UL and FCC testing of such interfaces. Several years ago, X-10 finally eliminated this bottleneck with the introduction of the PL513 computer interface module.

The PL513 provides the designer with an optoisolated interface to the power line. A signal coming from the module tells the computer when each power-line zero crossing occurs. Additionally, a signal to the module controls when the 120-kHz carrier is applied to the power line. The user is the one who must send properly formatted data to the PL513 in synchronization with the zero crossings. [See "Power-Line-Based Computer Control" by Ken Davidson, *Circuit Cellar INK 3*, May/June 1988.]

One other void had to be filled before X-10 became more practical. In addition to sending commands, the capability to listen for them was

important as well. X-10's TW523 corrected this omission. This module error checks any data received and sends it to the computer, again during zero crossings. Like transmissions, the user is responsible for decoding the received binary data. (See "The X-10 TW523 Two-Way Power Line Interface" by Ken Davidson, *Circuit Cellar INK #5*, September/October 1988.)

PRE-PLIX GYMNASTICS

Confusion as to what makes up an X-10 transmission still exists, even with these two interfaces. The X-10 format consists of a serial data stream

containing a start code, a housecode, and a function code. Table 1 shows valid housecodes and function codes.

Each bit of data in the bit stream consists of six 1- μ s time periods. Each time period is 2.778 μ s apart, or six per 60-Hz line cycle (Figure 1a). (If the first period is synchronized to the zero crossing of the 60-Hz line, then the remaining five time periods will be in step with each zero crossing of a three-phase power line and, in principle, be detected on systems with three-phase power.) A data bit with a value of "1" is sent as On-On-On-Off-Off-Off (Figure 1b), whereas a bit value of "0" is sent as Off-Off-Off-On-On-On [Figure 1c]. "On" is the presence of a 1- μ s pulse of the 120-kHz carrier and "Off" is its absence. Thus, one bit time equals one 60-Hz cycle.

Notice that each data bit is sent as three copies of the data bit plus three copies of the opposite logic state to allow simple error checking. Noise occurs equally on each half of the power line's cycle, whereas 120-kHz bursts must be present on only half the cycle to be considered legal. This aspect is true for all house and function code data bits. The start code uses a different format. It is always the same two-cycle sequence: On-On-On-On-On-On for the first cycle and On-On-On-Off-Off-Off for the second (Figure 1d).



 


Figure 1-a) X-10 transmissions are synchronized to the AC power line zero crossings. b) A 1 data bit is represented by three 1-ms bursts of 120 kHz signal, followed by silence during the next half cycle. c) A 0 data bit is just the opposite, with the bursts occurring during the second half of the cycle. d) Every transmission begins with a unique start code, which lasts two full AC cycles.

 

CP-1128
Combination Programmer
\$1295.00

- ✓ Supports **AMD's MACH110/210/120/130/230 EPLDs, Altera's 900-, 1800-series and MAX EPLDs, Cypress' CY7C361, Lattice's irp LSI1032 & pLSI1032, National Semiconductor's -5D & -7D devices and MAPL devices.**
- ✓ Qualified and recommended by AMD, Lattice, National Semiconductor, Signetics and others.
- ✓ Utilizes only manufacturer approved programming algorithms.
- ✓ Supports upto 28-pin E/EPROMs and bipolar PROMs including the microwire I²C devices.
- ✓ Supports **Dallas Semiconductor NVRAMs and TI DSP320, Microchip PIC microcontrollers.**
- ✓ Lifetime **FREE software** updates available via BBS and US Mail.
- ✓ Call for a **DEMO disk** and literature pack.
- ✓ Made in the USA

 

EP-1 140
E/EPROM & μ controller
Programmer
\$695.00

- ✓ The EP-1 140 supports **NEC's 27C8001, 8-Mbit EPROM, all 27C240 4-Mbit 16 bit EPROMs, FLASH EPROMs, NVRAMs and all microwire EPROMs**
- ✓ All Intel, AMD, and Signetics **40-pin μ controllers** supported directly.
- ✓ Qualified and recommended by Intel, Signetics, National Semiconductor, and others
- ✓ Lifetime **FREE software** updates available via BBS and US Mail.
- ✓ Risk-free **thirtyday money-back** guarantee.
- ✓ Made in the USA

With lifetime **FREE** software updates, you can't go wrong and BP Microsystems offers a thirtyday money-back guarantee to ensure product satisfaction. Remember, BP Microsystems is...

The Engineer's **Programmer**TM

BP MICROSYSTEMS

10681 Haddington • Houston, TX 77043-3239
(713-461-9430 • FAX (713) 461-7413

© 1991 BP Microsystems, Inc.

#149

Listing 1—Sending and receiving X-10 commands can now be done even using interpreted BASIC.

```

10 PORT1=09FH: REM P1.0-4 AS I/O. P1.5-6 AS OUT, P1.7 as IN
20 V=0: GOSUB 1000: GOSUB 1000: GOSUB 1000: V=31:GOSUB 1000: REM
  SYNC
30 PRINT 'Hit 'W' to write to PLIX. 'R' to read from PLIX'
40 G=GET
50 IF (G<>57H.AND.G<>77H.AND.G<>52H.AND.G<>72H) THEN 40: REM RrWw
60 IF (G<>57H.AND.G<>77H) THEN 180: REM Rr

70 REM Write Routine
80 INPUT 'Write which house code (0-15)?',V
90 IF (V<0.OR.V>15) THEN 80
100 GOSUB 1000
110 INPUT 'Write which function code (0-31)?',V
120 IF (V<0.OR.V>31) THEN 110
130 GOSUB 1000
140 INPUT 'Repeat code how many times (1-30)?',V
150 IF (V<1.OR.V>30) THEN 140
160 GOSUB 1000
170 GOTO 30

180 REM Read Routine
190 GOSUB 2000
200 IF V>15 THEN PRINT "New". ELSE PRINT 'Old'.
210 PRINT . House Code =",V.and.15
220 GOSUB 2000
230 PRINT 'Function Code =",V.and.31
240 GOTO 30

1000 REM Write a Value
1010 IF (PORT1.AND.80H)=80H THEN 1010: REM Wait for RDY to drop
1020 PORT1=((PORT1.OR.60H).AND.OE0H).OR.V: REM Set DIR, CS. DATA
1030 IF (PORT1.AND.80H)<>80H THEN 1030: REM Wait for RDY to rise
1040 PORT1=PORT1.AND.9FH: REM Clear DIR and CS
1050 RETURN

2000 REM Read a Value
2010 IF (PORT1.AND.80H)=80H THEN 2010: REM Wait for RDY to drop
2020 PORT1=PORT1.OR.0BFH: REM Set DIR, Clear CS. Data as inputs
2030 IF (PORT1.AND.80H)<>80H THEN 2030: REM Wait for RDY to rise
2040 V=PORT1.AND.1FH: REM Get the lower five bits
2050 PORT1=PORT1.AND.9FH: REM Drop CS
2060 RETURN

```

A normal transmission will take **11 60-Hz** cycles: two for the start code, four for the housecode, and five for the function code. In addition, every command should be sent twice. To turn on module A3, send housecode A, function code 3 (for unit 3), then housecode A, function code On.

Taking into account the repeated transmissions and the required three cycles of silence between complete transmissions, you end up with $2 \times [(2 \times 11) + 3]$, or 50 cycles, which is close to a full second. I hope you don't have anything else for your processor to do while it's busy watching for zero crossings and turning the 120-kHz carrier on and off. To make matters worse, I haven't even taken receiving

into account, where you must check for received data at every zero crossing (using the **TW523**). I have better things to do with my processing time. There must be a better way.

A BETTER WAY: PLIX

PLM takes the burden of X-10 serial transmission and reception off the processor, performing these functions as background tasks on its own. Simply send the housecode, function code, and the number of times to repeat the command (normally two), and PLIX outputs the proper gating sequences to the PL5 13 or the **TW523**. If you're using the **TW523**, you can ask **PLIX** for the last X-10 transmission it heard. The reply

also indicates if the data is new [was received after the last query]. If your system is battery backed, you may want to use PLIX's "AC power fail" output pm as a system input that indicates power-line status.

A simple bit-programmable, bidirectional, 8-bit port is all that is necessary to carry on a conversation with PLIX. Two output bits control chip select and data direction (RD/WR), one input bit reflects PLIX's status (RDY/BUSY), and five bidirectional lines transfer data.

Only five external components are necessary: two resistors (pull-ups for the PL5 13 or TW523), two capacitors, and a crystal. The 18-pin DIP package requires less than 2 mA at 5 volts to operate. Slightly more is needed when supplying the gating pulse to the optocoupler of the PL5 13 or TW523 during X- 10 transmissions.

USING PLIX

Figure 2 shows the PLIX chip connected to Port 1 of an 8031/8052 processor. Listing 1 shows a sample program that **exercises** the chip. The code is straightforward and easy to understand because the port is bit addressable and accessible directly through BASIC.

If you're not using an 8052, Figure 3 shows a pair of flowcharts that describe the proper algorithms to use to write to and read from PLIX.

Getting in sync with the PLIX chip after reset and terminating a function prior to finishing are both good practices. Simply send the PLIX three or more 0 data bytes followed by a 3 1. [The 0 values are illegal repeat commands and PLIX will hold in the repeat state. If a 31 is received, which is also an illegal repeat value, the previous commands are flushed and chip resets.]

DESIGNING WITH PLIX

PLIX does not have the speed required to interface directly as an I/O bus peripheral, so it must interface through port bits. As you have seen, interfacing to the 8052's port 1 is easy because each bit is individually programmable for input or output. However, all control does not have to

Position and/or Velocity

Motion Control




1 to 8 Axis Motor/Motion Controllers

- Intelligent, state-of-the-art, DSP Multifunction Programmable Controllers can be configured in minutes using "off the shelf" components
- Model DCX "motherboard" contains intelligence/memory/firmware and 6 or 8 sockets for "plug-in" DCX Control Modules
- 1 to 8 "plug-in" DC Servo, Stepper or Special Purpose Control Modules can be mixed/matched on same DCX board
- Install in ISA-bus (PC/XT/AT) or VME-bus (6U), or use "stand-alone" with RS232 or IEEE-488 (GPIB) communications interface Modules
- 436 Analog I/O (8 or 12-bit); 16-144 Digital I/O (TTL), plug compatible with Opto22
- High level interface libraries in "C," "BASIC," and Turbo Pascal, with examples and source code, and many Utilities (CAD/CAM, G-Code, Servo Tuning, etc.) included



Precision MicroControl
CORPORATION
8122 Engineer Road · San Diego, CA 92111
Tel (619) 565-1500 • FAX (619) 565-1511

Complete PC/XT®

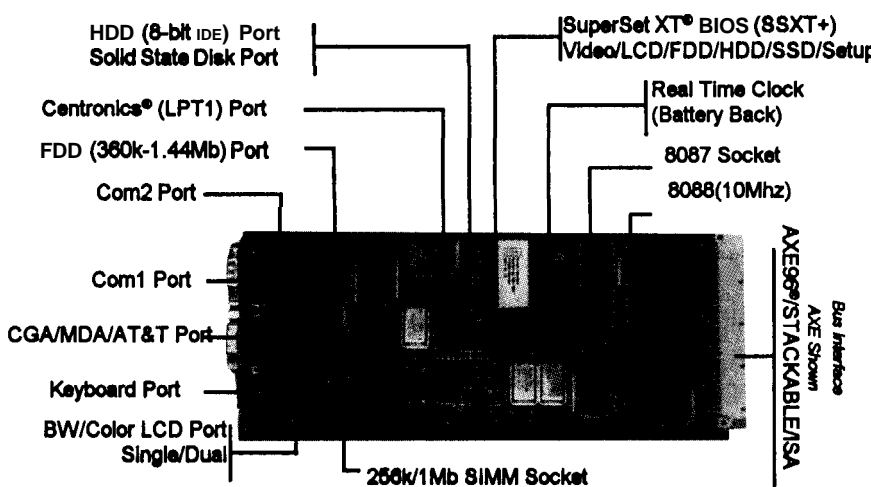

Model 1088-A \$329.00

Other Product

PCB/ASIC/Software Design
10V30 & 25386SX SBCs
Digital/Analog I/O, V.29/32 Module(s)
Solid State Disk Drive(s)
Soon 486DX SBC: Model 33486DX-A

Newman Associates
PO Box 22035
Lansing, Mi. 48909
(517)394-2560

Pricing subject to Change Without Notice
AXE96 Trademark of Newman Associates
All others to rightful owners

#151

IMAGENATION...

VIDEO FRAME GRABBERS

- ◆ Simplicity
- ◆ Functionality
- ◆ Affordability
- ◆ Accuracy

Cortex-I

\$495⁰⁰

- ◆ Real-Time Capture
- ◆ Half Slot XT/AT
- ◆ 512x484x8 Bit
- ◆ RS-170/CCIR
- ◆ External Trigger

Cortex-STD

\$595⁰⁰

- ◆ Dual Video Input
- ◆ Opt. XMS Mapped
- ◆ Low Power Options
- ◆ STD-80 or 32 Bus
- ◆ External Trigger

Vidmux-4

\$99⁰⁰

- ◆ 4 to 1 MUX
- ◆ Half Slot XT/AT

Includes Software...

- ◆ C Library & Source
- ◆ Image Capture Utility
- ◆ Tiff Utilities
- ◆ "Image" Drive Ram Disk Emulation

STARTER PAK...

Cortex-Pak

\$1395⁰⁰

- ◆ NEC/TI-23EX Camera With Lens
- ◆ 9" Video Monitor
- ◆ Frame Grabber
- ◆ Software & Cables

OEM PRICING AVAILABLE

IMAGENATION CORP.

P.O. Box 84568
Vancouver, WA 98684

PH/FX (206) 944-9 13 1

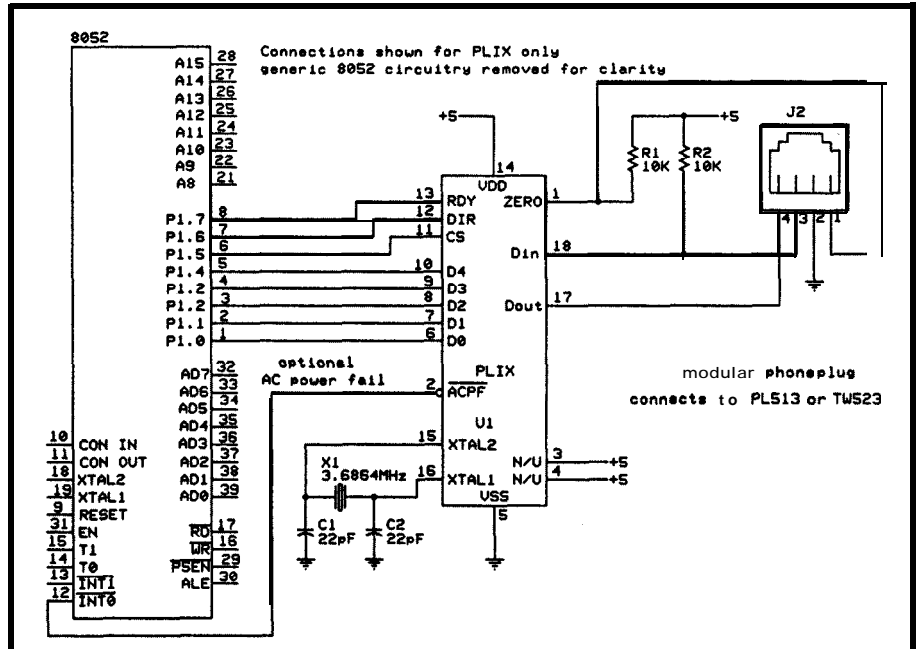


Figure 2-Adding PLIX to a generic 8052 circuit is just a matter of connecting it to the processor's spare I/O port

come from the same port. A minimum of two output bits, one input bit, and five bidirectional bits are needed from any source. If your processor does not have any spare bits, then use a peripheral interface chip, like the 6821,

mapped into the available I/O space. Each of its two 8-bit ports is bit programmable.

However you choose to interface with it, the PLIX chip will allow your processor to keep up with all its

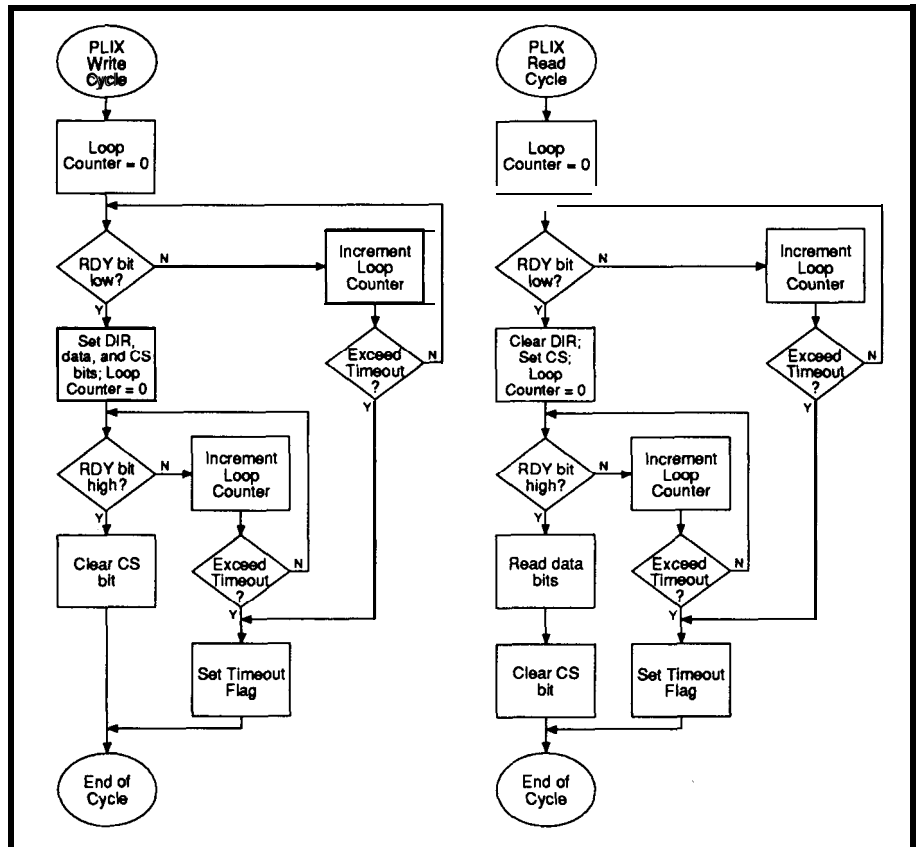


Figure 3-The PLIX read and write cycles use very similar algorithms and rely on handshaking between the processor and the chip.

 


Photo 2—Due to the PLIX chip's low power consumption, the demo board can be run off a 9-V battery.

important functions without having to twiddle its thumbs [or bits] during a time-intensive X-10 serial transmission or reception. If I didn't know better, I'd have guessed it was X-10 who came up with this missing link. Some companies just can't wait for the future; they have to invent it.

PLIX DEMO BOARD

I've put together a little board that will allow you to experiment with this chip (Photo 2). Even though PLIX only needs five external components and can be handwired easily, immediate gratification can be a worthy attribute. A modular phone jack permits direct connection to either the PL513 or the TW523. A short piece of ribbon cable off of the square-pin header simplifies interconnections between PLIX and your port bits. Finally, power is supplied by a 9-volt battery.

If you don't have a controller project in the works and can't directly connect to PLM, but still want to experiment, you are in luck. The PLIX demo board will also interface to your PC's parallel printer port. Because the PC printer port is not a true bidirectional port, the data must be read in through the status port as nybbles, which adds a bit more complexity to the circuit. The low power of the PLIX chip allows battery operation.

The routines written for the PC's parallel port are written in BASIC, but

are adaptable to any language, including straight assembly language. The quick evaluation of PLIX is this demo board's purpose. Once you see the benefits of using PLIX, you will likely want to include it in your future X-10 designs. ☛

Jeff Bachiochi (pronounced "BAH-key-AH-key") is an electrical engineer on the Computer Applications Journal's engineering staff. His background includes product design and manufacturing.

SOURCE

Micromint Inc.
4 Park St.
Vernon, CT 06066
(203) 871-6170

- 1. PLIX Chip and Data Sheet ... \$20
- 2. PLIX-EKit Evaluation Board. Includes PLIX chip, data sheet, PCB with all components, application note, and PC-compatible software on disk. \$29

Add \$20 for TW523 X-10 transceiver module (sold with PLIX-EKit only).
Shipping extra.

I R S

- 422 Very Useful
- 423 Moderately Useful
- 424 Not Useful

DATA ACQUISITION BOARD FOR PCs

Affordable Data Acquisition plug-in board. Easy to use. For industrial applications, home control, electronic hobbyist, educational purposes.

8 A/D INPUTS
32 PROGRAMMABLE I/O
PC PLUG IN BOARD
SOURCE PROGRAM INCLUDED
(BASIC, TURBO PASCAL, TURBO C)

Only \$130.00
MONEY ORDER

OEM PRICING AVAILABLE






OMZAR INDUSTRIEL INC.
6555 Métropolitain est, Suite 502
Montréal, Québec, H1P 3H3, Canada
Tel: (514) 322-6646 Fax: (514) 322-8688

I'm 18.432— and I Like It

SILICON UPDATE

Tom Cantrell

 

S ometime during the '70s, Alice Cooper paid homage to those with raging

hormones by making his classic statement, "I'm 18 and I like it."

Today, many of us yearn for a return to the days of our youth when we were strong and good looking.

Meanwhile Alice, who still wears tights and makeup 20 years later, barely made it out of adolescence before jumping directly into mid-life crisis. Come on Alice, update our generation's anthem-how about "I'm middle-aged and it stinks."

Baby-boomers and the like aren't the only ones having mid-life crises. ICs are having them, too. Chips that once were the darlings of industry have ended up feeble "commodities."

Now a chip, unlike the typical burnt-out Silicon Valley executive, can't turn to Grecian formula, a Nehru jacket, and singles bars for a mid-life "kicker." However, as I will show, old chips and systems can also be rejuvenated.

DANCING AS FAST AS I CAN

The Z80, and its follow-on the Z80 180 (a slightly modified HD64180), certainly qualify as some of the most popular chips of all time. Nevertheless, these parts are starting to show their age.

Now, Zilog has come to the rescue with the new Z8S180. Though fully plug compatible with the existing '180, the 'S180 has a number of new features.

The S stands for the *static* design of the chip. The primary benefit of static [as opposed to *dynamic*] designs

is you can arbitrarily run the clock slowly and, indeed, stop it altogether.

This ability to stop the clock is exploited with the new power-down modes *IDLE* and *STANDBY*, which supplement the *SLEEP*, *IO STOP*, and *SYSTEM STOP* modes of the original '180 (Figure 1). The *STANDBY* mode (10 μ A) cuts power consumption dramatically when compared to the previous lowest power mode, *SYSTEM STOP* (17.5 mA), making the 'S 180 far more suitable for battery-powered applications.

A neat addition, but nobody is going to rave about a new chip that runs slower than ever. However, the new static CMOS design offers another benefit: the 'S180 runs at up to 20 MHz, twice as fast as the regular '180!

Longtime readers know I'm a big believer in clock rate when boosting CPU performance. Let others dabble with the complexities of superscalar, superpipeline, and various other super-duper tricks. I'd rather just crank the clock. So, I grabbed a '180 board and headed for Zilog. Mission (Possible, I hope): double the performance or bust!

NO FREE LUNCH

In my view, the performance of general-purpose computers boils down to bus bandwidth. Yes, architecture, compilers, and system design have an impact, but in today's competitive environment—"religious wars" to the contrary—gaining a significant advantage in these areas is difficult. However, the performance gains of a faster clock come at a price: the need for a corresponding faster memory. Without it, any improvement will be lost to the dreaded wait state.

In fact, boosting the CPU speed without facing up to memory bottlenecks can lead to a somewhat pathological decrease in performance. The reduction happens when the "granularity" of a wait state exceeds the percentage speed-up in the clock.

This scenario is most easily illustrated with RISCs that call for 1-clock bus cycles. In this case, the granularity of adding the first wait state is 100% (i.e., a 1- to a 2-clock bus cycle). Now, what happens if the clock is boosted without faster memory?

Some people just can't get enough horsepower out of their processors, and Tom is certainly one of them. Zilog's newest speed demon runs the faithful Z180 (HD64180) up to 18.432 MHz and beyond.

Power-Down Modes	CPU Core	On-Chip I/O	osc.	CLKOUT	Recovery Source	Recovery Time (Minimum)
SLEEP	stop	Running	Running	Running	RESET, Interrupts	1.5 Clock
I/O STOP	Running	stop	Running	Running	Programming	
SYSTEM STOP	stop	stop	Running	Running	RESET, Interrupts	1.5 Clock
IDLE†	stop	stop	Running	stop	RESET, Interrupts, BUSREQ	8+1.5 clock
STANDBY†	stop	stop	stop	stop	RESET, Interrupts, BUSREQ	2+1.5 Clock
						2+1.5 Clock

Notes: † IDLE and STANDBY modes are **only** offered in **Z8S180**. Note that the minimum recovery time can be achieved if INTERRUPT is used as the Recovery Source.

Figure 1—Due to its static design, the Z8S180's clock oscillator can be stopped completely (STANDBY) for extreme & low power consumption.

Say the RISC runs at 10 MHz and thus has a 100-ns bus cycle. The current memory has 70-ns access time resulting in zero-wait state operation. Now, Joe Naive-User hears that a hot 16-MHz CPU is available and plugs one in, ignoring messy details such as upgrading memory.

While the placebo effect may cause Joe to think his PC seems a little snappier, the reality is the 16-MHz CPU, with its 66.6-ns bus cycle, is going to need a wait state to work with the existing 70-ns memory. The sad reality is that the hot CPU is running 33% slower (133.3 ns vs. 100 ns) than before the "upgrade."

Fortunately, the RISCer's need for speed has driven IC manufacturers to deliver ever faster memories. In this era of 50- to 100-MHz CPU chips, fast memories are de rigueur.

Unsure of which memories I could scrounge at Zilog, I took the precaution of tweaking the '180 board's BASIC EPROM to take advantage of the '180's on-chip wait state generator (a great feature) to inject the maximum number of three wait states. This stretches memory access to six clocks (three is the minimum), making the bus cycle 300 ns at 20 MHz. Past experience told me that the access time required of the memory is about half the bus cycle, or 150 ns, which isn't a problem even for EPROM and certainly not for the SRAM.

Before heading off, I also wrote a simple test program to allow me to exercise the board with different wait state settings.

HUMAN ERROR

Over at Zilog, '180 board and test program in hand, I sat through a nice

presentation describing the 'S180, though I was chomping at the bit to head for the lab.

The helpful folks at Zilog pointed out some of the other key enhancements. One particularly unique feature is the Z8S180's ability to reduce the drive programmably to all of its outputs or just to selected subsets. The effect is to slow the edge rates, thereby reducing radiated ElectroMagnetic Interference (EMI) significantly [Figure 2]. Besides keeping the FCC at bay, this feature is especially helpful in wireless communications applications.

Surprisingly, the 'S180 consumes little more power than the '180 even at full-speed operation. Normally, CMOS power consumption is almost linear with the clock rate. If the clock rate is doubled, the power consumption should increase significantly. However, the 'S180 consumes only 40 mA at 20 MHz compared to 36 mA at 10 MHz for the '180. One simple explanation for this difference is the shrink from a 1 S-micron to a 1.2-micron process. A less obvious reason is that the static design, just as for memories, eliminates the need to refresh internal circuits like the register file.

A programmable divide-by-1 or divide-by-2 clock option is a really nice touch Zilog added. The original '180 requires a 2x clock input, so my board had an 18.432-MHz crystal running the CPU at 9.216 MHz (the weird clock rates are called for by the '180 on-chip baud rate generator). When the 'S180 is reset, the programmable clock divide is set to 2; thus, the 'S180 also comes up running at 9.216 MHz. A single OUT instruction can then toggle the divide bit to 1x and speed things up.

This result means existing '180 designs can be upgraded without changing the crystal! That's good, because I wasn't looking forward to doing the switch; my soldering skills are definitely not improving with age.

As the presentation ended, I thought that this upgrade, a simple change of three chips (the '180, BASIC EPROM, and SRAM), would be about as easy as one can get.

Once in the lab, we dug up an 85-ns EPROM and a 35-ns SRAM. I'd been told that the 20-MHz 'S180 required memories of about 60 ns. Even relaxing that to reflect 18.432-MHz operation, I realized I'd need at least one wait state to deal with the EPROM. No problem. I'd programmed the BASIC EPROM to boot up with the maximum number of wait states and the 'S180 boots at 9.216 MHz anyway, so at least it should come up.

Sure enough, I popped the parts in, hit power, and—success, the board worked! I exercised my test program and everything was solid. The test confirmed the 'S180 was functionally equivalent to the older '180, something that shouldn't be taken for granted when a chip is redesigned.

But now the time was right for the real test, a double-dose of megahertz.

OK, how do I toggle the clock-divide bit!

Oh, simple, just output an 80H to register 3FH.

Inserting an OUT \$3F, \$80 at the front of my program, I was ready for blast-off. I entered "RUN," left my finger poised over the return key, took a deep breath, and thought, "Hang on to your hats. Here we go."

Of course, you know what happened when I hit that key. The

board just locked up, remaining mute and unresponsive while I pounded on the keyboard. Finally, I gave up hope and reached for the board's reset switch. **Hmm...still** came up at 9 MHz.

When facing such a situation, an inexperienced user will often jump to the conclusion "the chip is busted." After all, the 'S180 was marked "ENGR SAMPLE" and these things happen when you're on the "bleeding edge."

However, having done my post-graduate work in the school of hard knocks, I know that 99% of the time "the chip is busted" excuse doesn't pan out. An old-timer will sit down and say "What's the best way to figure out what I did wrong?"

After a little head-scratching (heaven forbid I should get out schematics and scope this early on), I began to wonder about some of the '180's on-chip control bits. Hadn't the CPU gone through some revisions to better adapt the bus timing to Zilog peripheral chips? I seem to remember an "I/O

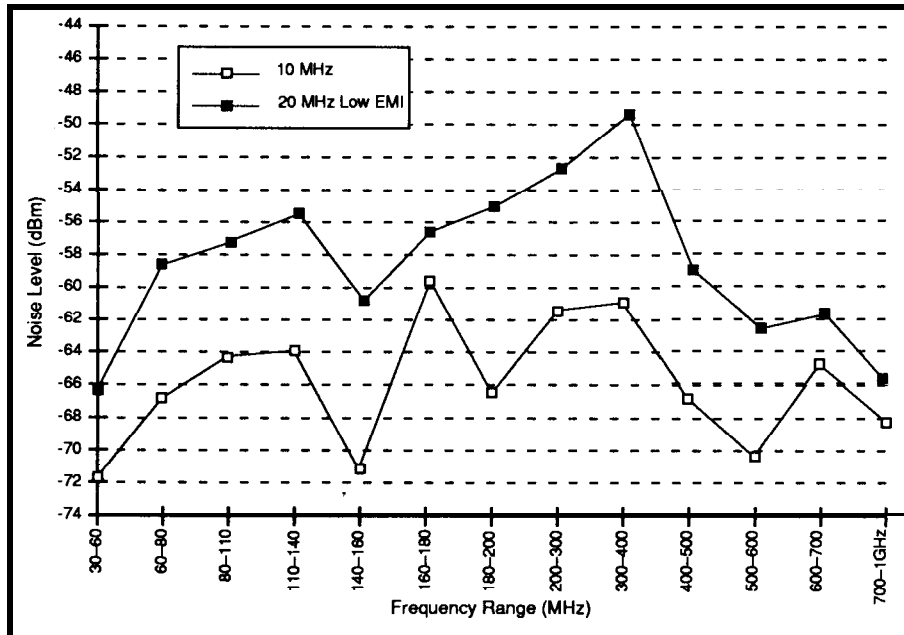


Figure 2—One of the Z8S180's new features is the ability to reduce drive current on some key control lines to reduce radiated EMI. With the feature turned on, a 20-MHz Z8S180 is quieter than the original 10-MHz Z80180 that doesn't have the feature.

compatibility" bit somewhere. I thought I'd better take a quick look at the register definitions. I also thought about the rest of the bits I was setting

in register 3FH. Maybe they did something.

Hey, register 3FH doesn't have any "clock-divide" bit.

The Disk is DEAD!

DON'T SELL YOUR CUSTOMERS A PROBLEM!

Dust, moisture and vibration kill rotating disks every day. Instant **Access™ No Motion™** solid state memories offer extremely high reliability, light speed access and the ultimate in data integrity. **Instant Access™** is available in FLASH EEPROM and NVRAM and is programmable in DOS or WINDOWS. Rely on **Instant Access™** -the demonstrably superior No Motion Memory.

"Instant™ Access" is the Solution!

- 1000 times faster!
- 100 times more reliable!
- Ideal for storing DOS and programs!
- Perfect for booting diskless workstations.
- Hard Disk Drive replacements available

Call 1-800-451-DISK to order your evaluation unit



**PRODUCTIVITY
ENHANCEMENT
PRODUCTS**

26072 Merit Circle, Ste. 110 • Laguna Hills, CA 92653
1(800) 451-DISK • (714) 348-1011 • FAX (714) 348-1310

VISA
AMEX
MCHG

#154

ROMboy

Low Cost, Reliable, High Quality ROM Emulation from the Creators of PROMICE

- Emulation of up to 1 Mbit ROMs (4 Mbit-soon)
- Supports any ROM type (DIP or PLCC)
- Supports high speed ROMs
- Supports any word size up to 2048 bits wide
- Host software for DOS, Unix, Mac, VMS
- Battery backed memory
- Intelligent micro-controller based unit
- SMT CMOS layout for robustness
- Tiny size: 2.5" x 3.8" x 0.9"
- Unbelievably low price!

ROMboy...

from the authority in firmware development tools

Orders: (614) 899-7878
West: (415) 750-0219
FAX: (614) 899-7888



**Grammar
Engine
Inc.**

See us at the Embedded Systems Conference—Booth #705

#155

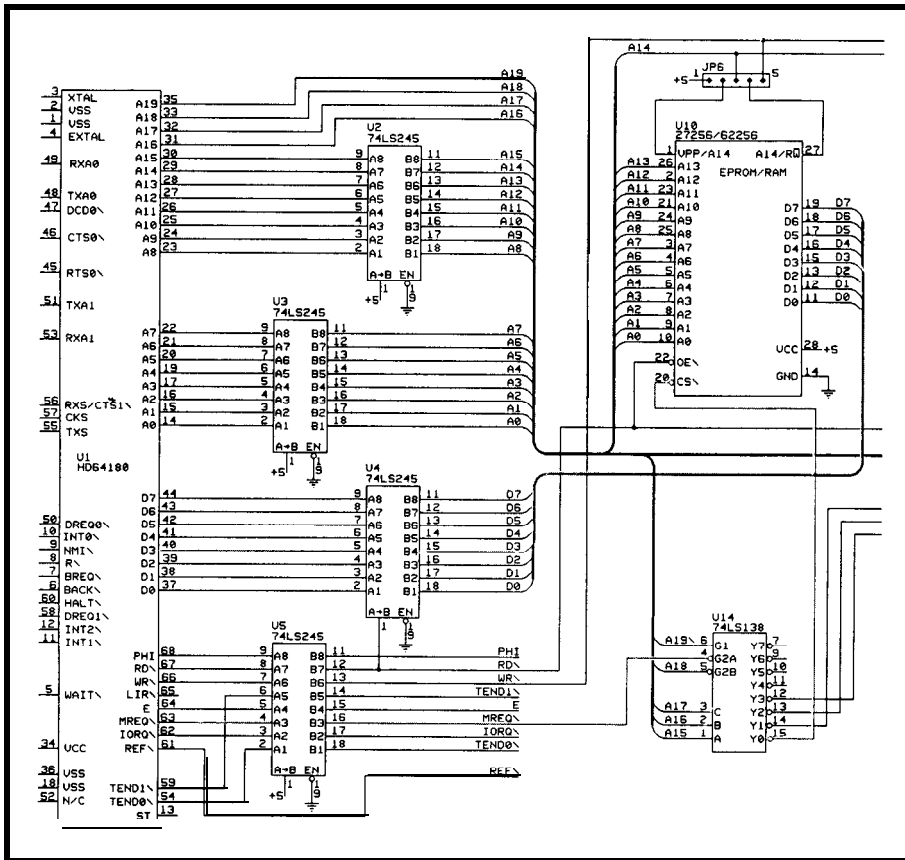


Figure 3-A sample HD64180 (Z80180) circuit shows the critical timing paths in the memory section.

Oops-oh yeah, it's in register 1FH.

The bits I was setting in register 3FH happened to have the interesting property of relocating the '180 on-chip I/O addresses. Thus, after the OUT instruction, the software was trying to talk to I/O ports (including the console port) that weren't there anymore!

Changing the, OUT instruction from 3FH to 1FH, I skipped the dramatics and hit it.

I experienced an apprehensive moment when garbage appeared on the screen, but it was only a reflex because I'd already anticipated the doubling of all the chip's baud rates, timer constants, and so forth. I calmly switched my terminal software from 9600 to 19200 baud and-voih!

Exercising my test program, I discovered the board worked pretty much as expected [i.e., it would work with a single memory wait state). I tried zero wait states knowing that chips are often faster than specified, especially at room temperature, but the EPROM couldn't hack it.

8052 development system



Introducing the BD52, a complete 8052 development system providing all hardware and software needed to develop 8032/8052-based products. A flexible embedded controller with pseudo-EPROM

capabilities allows you to download and test your code for easy software development. Memory and interface extensions enhance the BD52's capabilities. A PC-based windowed interface gives you complete control of software and hardware functions. The powerful development tools include a fully featured assembler, C-compiler and debug monitor. Software and hardware are closely integrated for greater productivity at an extremely competitive price.

Hardware

8052 microcontroller and EPROM loaded with debug monitor
 ability to address 64K of code space and 64K of data space
 pseudo-EPROM capacity: 30K with 32K SRAM (included)
 RS232 serial interface, 11 parallel I/O lines
 120V AC power supply; documentation and schematics
 sockets for extensions: watchdog & power monitor, 4 A/D & 1 D/A
 converters, 512 byte EEPROM for non-volatile data storage, 7-line relay
 driver, 32K SRAM for up to 62K pseudo-EPROM capacity

Development Software

MICRO-C/52 'C' compiler featuring 5 memory models and a standard
 library with extensions to control BD52's hardware features
 ASM52 cross assembler
 PC-hosted control/debug software with easy-to-use windowed interface
 that provides access to all of the BD52's features

Order a BD52 at the introductory price of \$199.95* US from:

*please add \$10.00 for timing

Dunfield Development Systems

P.O. Box 31044, Nepean, Ont. Canada K2B 8S8

Phone: 613-256-5820

Complete pricing and free catalog of hardware and software products available.

#156

T&e It Easy.

Take it easy on your cargo with a custom 'Cabbage Case built to the exact dimensions of your equipment.

Take it easy on your back with our extension handle and tilt wheels options.

Take it easy on your wallet. Let Cabbage Cases show you how easy it is to save money on quality, custom-built road cases that make shipping and traveling with your valuable cargo, safer and easier. Prices quoted over the phone.

Call 8004884495 today.



CABBAGE CASES, Inc.

1166-C Steelwood Rd.
Columbus, OH 43212

800/888-2495

614/486-2495

FAX/486-2788

#157

I left Zilog happy that despite human error (the cause of most "computer problems"), I had succeeded. However, even as I was driving away, that one remaining wait state started to gnaw at me. . . .

CHIPS IN THE FAST LANE

Zippering down the freeway, I pondered the problem. Yes, state-of-the-art memories exist, but where can I get one? Those puppies aren't exactly a stock item at the local "Ye Old Chip Shoppe."

On autopilot, I registered the red lights stacking up ahead and dove for the off-ramp, planning to take one of the secret short cuts that harried Silicon Valley commuters seek out like rats in a maze.

Though I am skeptical of psychic phenomenon, I wonder if it was just coincidence that my roundabout path took me right by WaferScale Integration!

Hey, didn't I just get something in the mail from these folks about fast EPROMs!

I must have made quite a sight, first careening into their parking lot, then dashing into the lobby waving my '180 board and demanding to speak to the marketing manager. However, the receptionist remained calm, called the appropriate authorities [not the police], and it wasn't long before I was back on the road, this time clutching some real gems, 55-ns EPROMs!

Back at my lab, I programmed a 55-ns chip and plugged it in. I successfully got into high-speed mode and started exercising my test program first with three wait states, then two, then one. Then for the big test: zero wait states!

Crashola-darn!

WaferScale has 45-ns EPROMs (and they'll even be offering 35-ns soon). Therefore, I knew the simplest fix would be to continue plugging in ever faster memories until it worked. But now my curiosity was piqued (and I knew I wouldn't sleep until I snuffed that wait state). Zilog said 60 ns should do the trick, and I wondered why it wasn't working. Knowing I

didn't have a lot of time for a full-blown engineering exercise, I nevertheless reached for the schematic and data sheets.

The relevant portion of the board design is shown in Figure 3, while the timing diagrams are shown in Figure 4. Identifying the likely critical path didn't take me long. Highlighted in Figure 3, this path is described in words as follows:

The CPU outputs addresses and ● MREQ (Memory REQuest) at the start of the cycle. The addresses are guaranteed to be valid before ● MREQ, and furthermore ● MREQ passes through a 'LS245. Thus, *MREQ is the last signal to reach the 'LS138. After it arrives, the 'LS138 will drive the EPROM ● CS (Chip Select). After ● CS assertion, the EPROM will output data within the specified 55 ns, but the circle isn't completed until that data passes through another 'LS245 before finally reaching the CPU.

Time for a little calculation. First of all, at 18.432 MHz, the clock cycle is roughly 55 ns, so a zero-wait bus

TIRED OF WAITING FOR THE PROMPT ?

DOS IN ROM!

Speed up with a ROM DRIVE! Boots DOS and programs instantly. Also used to replace mechanical drive completely in controllers or diskless workstations. The only perfect protection from viruses. Easy to install half size card.

VVDISK1 64k.....\$75	\$75
VVDISK2 360k.....\$150	
VVDISK3 1.44m..\$195	

Quantity discounts!





\$95 EPROM PROGRAMMER

--OO ROMS FOR SBC OR VVDISK
--PROGRAM 2764/27010 EPROMS

WORLDS SMALLEST PC !!!
ROBOTS ALARMS RECORDERS DOS

8088 SINGLE BOARD COMPUTER

THREE EASY STEPS: **\$27** 1K QTY
1. Develop on PC
2. Download to SBC **\$95** 5GL QTY
3. Burn into EPROM

-2 PARALLEL	-LCD INTERFACE
-3 SERIAL	-KEYBOARD INPUT
-PC TYPE BUS	-REAL TIME CLK
-BIOS OPTION	-BATTERY OR 5V

FREE SHIPPING IN U.S.
5 YEAR LIMITED WARRANTY



Box 850
Merrimack, NH
(508) 792 9507



MOVE OVER INTEL MICROMINT SOURCES 80C52 CMOS BASIC CHIP

Micromint has a more efficient software-compatible successor to the power-hungry Intel 8052AH-BASIC chip. The 80C52-BASIC chip was designed for industrial use and operates beyond the limits of standard commercial-grade chips. Micromint's 80C52-BASIC chip is guaranteed to operate flawlessly at DC to 12 MHz over the entire industrial temperature range (-40°C to +85°C). Available in 40-pin DIP or PLCC

80C52-BASIC chip	\$25.00
OEM 100-Qty. Price	\$14.50
BASIC-52 Prog. manual	\$15.00

MICROMINT, INC.

4 PARK ST., VERNON, CT 06066
TO ORDER CALL
1-800-635-3355



8051 Family Tools

In Circuit Emulators

The DryICE Plus is a modular emulator designed so you can get maximum flexibility from your emulator purchase. The base unit contains all the hardware necessary to support pods containing many of the most popular members of the 8051 family of embedded control microprocessors. Buy one base unit, and select one or all of the pods you need to do the job at a much reduced cost. You get the same great functionality found in our popular DryICE 8031 emulator plus real-time Execute-to-Breakpoint, Line-by-Line Assembler, and much more. And the price is (almost) unbelievable! (Yes, it works with the Mac, too!)

Base Unit (w/RS-232 IF) -- \$299

Available Pods: \$149 each

8031/32, 80C31/32, 80C154, 80C451, 80C535, 80C552/562, 80C652, 80C51FA, 8751152, 87C51/52.

Call about **87C751/752 support**

16K Trace Buffer option: Avail. 2nd Qtr '92

Standard 8031 DryICE -- Still only **\$199**

Enhanced 8031 DryICE -- **\$269**

8051 Simulation

The 8051SIM software package speeds the development of 8051 family programs by allowing execution and debug without a target system. The 8051 Simulator is a screen oriented, menu command driven program doubling as a great learning tool. **\$99.**

Single Board Computers

8031SBC - A fast and inexpensive way to implement an embedded controller.

8031/32 processor, 8+ parallel I/O, up to 2 RS232 serial ports, +5 volt operation.

The development board option allows simple debugging of 8031151 family programs. **\$99ea**


80C552SBC - 10 bit 8 ch. A/D, 2 PWM, 1 RS232 & 2 RS232/422/485 serial ports, sockets for 64k ROM, 64k RAM, +5 volt operation; optional RT Clock w/ battery, 2k EEPROM. Development board version available. Call for pricing!

Call for your custom product needs.
Free Quote - Quick Response




HiTech Equipment Corp
9400 Activity Road
San Diego, CA 92126
[FAX: (619) 530-1458]

(619) 566-1892

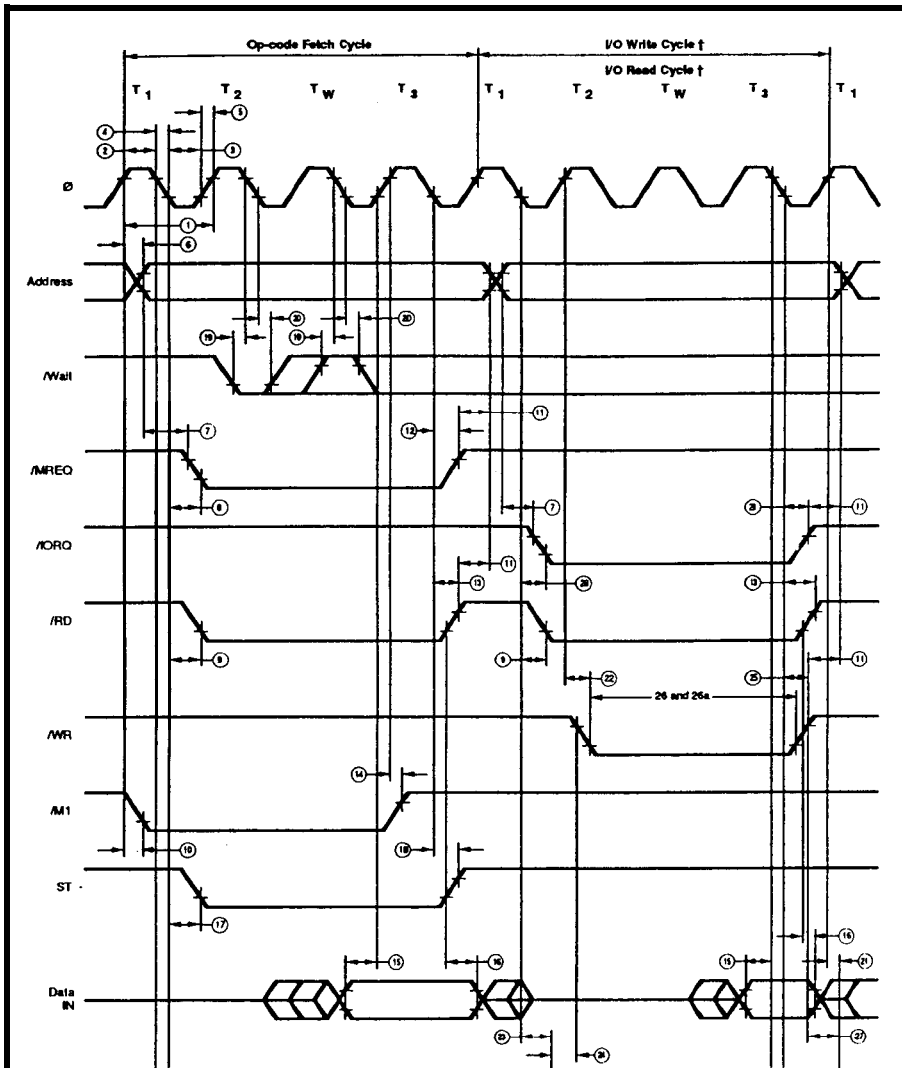

Symbol	Parameter	-35		-45		-55		-70		Units
		Min.	Max.	Min.	Max.	Min.	Max.	Min.	Max.	
t _{acc}	Address to output delay		35		45		55		70	ns
t _{ce}	CE to output delay		35		45		55		70	
t _{oe}	OE to output delay		20		20		25		30	
t _{of}	Output disable to output float		20		20		25		30	
t _{oh}	Address to output hold	0		0		0		0		

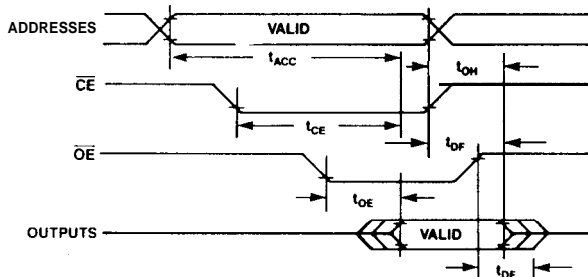

			-16 MHz		-20 MHz		
			Min.	Max.	Min.	Max.	
8	t _{MED1}	Clock fall to /MREQ fall delay Data read setup time					ns
15	t _{DRS}		15	25	10	25	

Figure 4-Using the timing diagrams along with typical discrete-gate delays (not shown), the minimum access time necessary for memory components can be calculated.

cycle is 165 ns (three clocks). Yes, 165 ns sounds like a lot more than 55 ns, but proceed with the calculations and you'll see how the access time gets **nicked and dimed** to death.

First of all, there is a fair amount of slop at either end of the cycle. The ● MREQ output doesn't occur until after the second half of the first clock (**spec #8**), while the data must be given to the CPU prior to the first half of the last clock [third for zero wait states] (**spec #15**). So immediately you can subtract an entire clock, composed of a half clock at each end of the cycle, from the available access time, reducing it to 110 ns.

Now, you have to subtract the worst case ● MREQ output delay (**spec #8**) and input data setup time (**spec #15**). According to the 'S180 data sheet, these are 25 ns and 10 ns, respectively. Subtracting the combined 35 ns from 110 ns leaves us with 75 ns access time.

Because the board with the faster memory isn't working with a 55-ns memory, where did the 20 ns go? If

you haven't looked at a **TTL** data book in a long time, you may be like me and need reminding that the **TTL** in the critical path-two stages of 'LS245 and the 'LS 138-will typically consume an astounding 30' ns! Thus, you're left only about 45 ns access time, which explains why a 55 ns EPROM didn't cut it.

I learned a couple lessons from this experience. The memory access time required is always much less than the bus cycle time [in this example, it's 1/3, or 55-ns access time, for 165-ns cycle time). Also, the discrepancy becomes much worse as the cycle time shrinks, unless you deal with fixed propagation delays (i.e., pokey **TTL**).

What's clear is that the 'LS138 is the main bottleneck, typically taking 21 ns to drive the ● CS output after ● MREQ input. I checked into an 'ALS138 (ALS is a more modem and faster technology than LS) and discovered I could buy the 10 ns I needed for about 50 cents.

Finally, I'm 18.432, with zero wait states, and I like it! ☐

Tom Cantrell has been in Silicon Valley for more than ten years working on chip, board, and systems design and marketing. He can be reached at (510) 657-0264 or by fax at (510) 657-5441.

CONTACT

Zilog Inc.
210 E. Hacienda Ave.
Campbell, CA 95008-6600
(408) 370-8000

The 100-piece price for the 20-MHz Z8S180 (PLCC) is \$17.86.

WaferScale Integration Inc.
47280 Kato Rd.
Fremont, CA 94538-7333
(5 10) 656-5400

The 100-piece price for the 55-ns WS57C256F (32K x 8) EPROM is \$11.70.

IRS

425 Very Useful
426 Moderately Useful
427 Not Useful

8051*

Single Board Computer

\$65

Singles!

Features: *8051 based Siemens 80535 & 4 Parallel Ports, 1 Serial Port, A/D, Timers, Watchdog, 3 Memory Sockets 64K Addressing, 8K RAM installed, RS-232 Conversion. Board size is 100x 100mm (Approx 4" x4"). CALL NOW!

NEW MICROS, INC.
1601 Chalk Hill Road
Dallas, Texas 75212
Tel: (214)-339-2204

#161

68HC11

Single Board Computer

\$65

Singles!

Features: F68HC11 (Max-FORTH embedded in A8) & 3 Parallel Ports, 2 Serial Ports, A/D, Watchdog, 3 Memory Sockets - 64K Addressing, 8K RAM, RS-232 Conversion. Board size is 100x 100mm (Approx 4" x4"). CALL NOW!

NEW MICROS, INC.
1601 Chalk Hill Road
Dallas, Texas 75212
Tel: (214)-339-2204

#162

The Middle Ground

Negotiating a Keyboard Interface

Much of the computer engineer's life is spent making tradeoffs between doing things in hardware and doing them in software. John looks at several options available when designing a keyboard interface.

PRACTICAL ALGORITHMS

John Dybowski

O firmware, the middle ground between hardware and software, has the disposition at times to take on the attributes of both. That this type of code has the capacity to perform tasks normally assigned to hardware may explain why its design often resembles a mechanism more so than the workings usually associated with programming. Firmware tricks can impersonate many hardware functions, but as usual you must take into account the strengths and limitations of the methods you choose.

SOFT HARDWARE

Generally speaking, either using ICs dedicated to serving the desired purpose or emulating these functions in firmware can achieve the peripheral functions required by an embedded system. The choice is usually based on the need to strike a balance among overall system necessities, complexity, and cost. As an example, you can use a UART to fulfill asynchronous serial communications or, alternatively, you can take a firmware-only approach.

Furthermore, depending on system requirements, the firmware-based approach can perform as a dedicated loop that basically shuts down all other operations and bangs the bits using embedded timing loops. You can refine this approach by referencing the timing to a timer interrupt where other system functions can continue to be serviced as well. As usual, any choice you make is relative, and the demands of the system under consideration dictate what's appropriate and effective.

A system that simply uploads collected data to the host computer when in a dedicated dump mode has no penalty regarding the suspension of other system functions. This lack of restriction exists to perform the communications chores entirely in firmware using simple bit-banging.

When performing communications on an intermittent basis with a system that has to remain live, running the communications in firmware while off-loading the timing burden to a timer interrupt may be appropriate because some processing power is available for other functions. Of course, if the system in question must be on-line in a networked environment with heavy communications traffic while performing its routine functions, then keeping it on-line without the use of a hardware UART makes no sense.

When considering functions such as serial communications, the choice of using a hardware or firmware approach is usually clear cut, based on the prevailing needs. Some decisions may not be quite as apparent, and taking the wrong approach can cause significant problems down the road. Although much can be done using a firmware-only approach, there comes a point of diminishing return where a little hardware can save you much heartache.

One function that I've never felt compelled to use a purely hardware approach on is keyboard scanning. Although special cases exist where a strictly hardware approach makes a great deal of sense, I've had good results using firmware-based scanning, particularly because the process load is extremely minuscule.

Before I show you several different arrangements for scanning a keyboard, I'll familiarize you with the common requirements of a keyboard driver.

THE FUNCTIONS OF A KEYBOARD DRIVER

The basic functions of a keyboard driver consist of doing a contact scan [checking the state of all the key contacts], **debouncing** a key closure, implementing the keyboard style, and performing the key code translation.

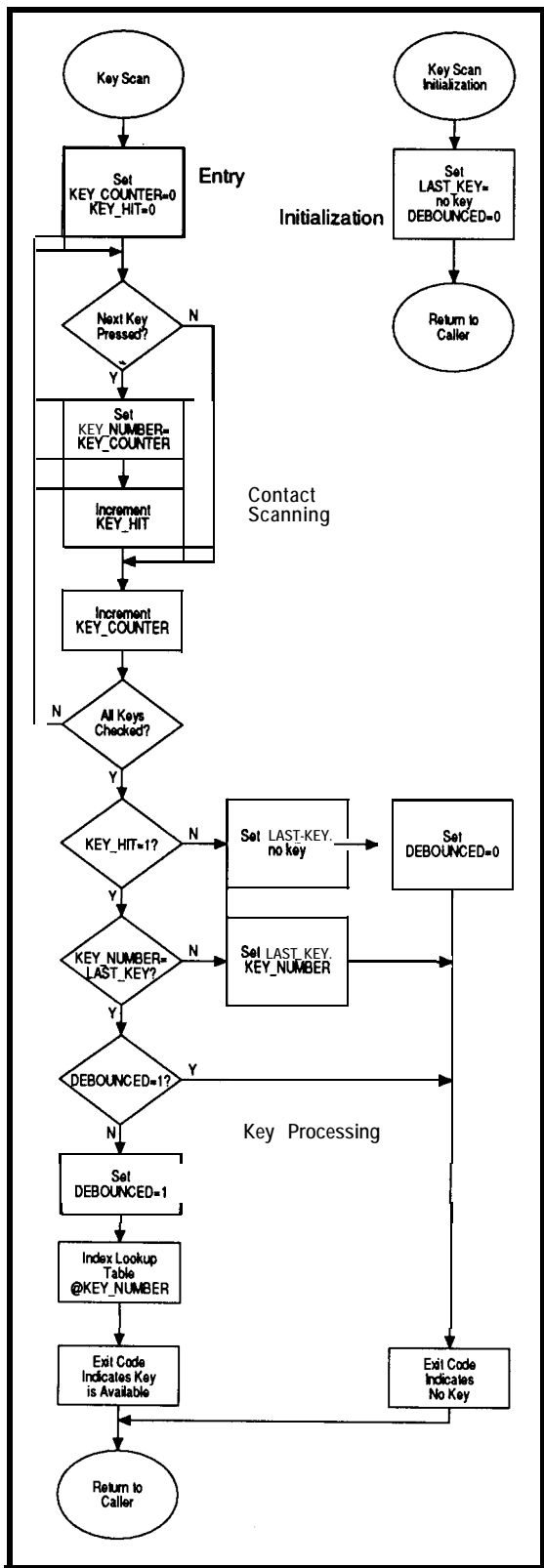


Figure 1—The generic keyboard driver routine can be broken into three sections: entry, contact scanning, and processing.

As far as the contact scan goes, it may consist of doing a row-column matrix scan using a variety of methods or simply reading the key switches if they connect in a parallel fashion.

Debouncing is the rejection of the switch chatter that usually accompanies a key hit. It includes the proper deglitching of the occurrence to prevent indicating a false closure in the event of transient noise pickup at the interface.

The keyboard style describes the type of action that the keyboard presents to the user. A few examples of this function are two-key rollover, n-key rollover, and **multikey** lockout. Some of these styles are the result of keyboard operation streamlining to accommodate the needs of touch typists. My intention is to show how to develop a simple driver suitable for embedded applications that are most often served by simple switch-type or membrane keyboards. For this application **multikey** lockout is most appropriate. **Multikey** lockout refers to the rejection of multiple closures at the keypad and the recognition of a single key hit as the only valid condition for processing.

For solid response and proper **debounce** operation, have the entire keyboard scanned once about every 20 ms either piecemeal or all at one time. My preference is just to go ahead and scan the entire keyboard, which is not a problem because I don't do the actual scan from an interrupt service routine. You could do the scan from an interrupt, but if you weren't careful you might end up hogging the system for perhaps 100 μ s or more at a shot. If interrupt level processing is desirable,

then the piecemeal approach makes more sense, but you will have to maintain state information on where you are in the scanning process, adding to the overhead load.

THE GENERIC KEYBOARD DRIVER

The idea behind the way I implement key scanning consists of invoking a callable routine at 20-ms intervals, which is usually referenced to an interrupt-driven timebase. A minimal amount of state information must be retained so the process can progress in a seemingly unbroken fashion because the operation is discontinuous. Fundamentally, the routine checks all the keys, then determines whether a valid key is available using local and global variables. On completion, an exit code indicates if a key code is being returned to the caller.

Although uncomplicated enough in principal to begin with, you can further simplify the keyboard scan algorithm by breaking it up into three sections. As I'll show, viewing the process thus allows adapting the general concept for use with various hardware schemes.


I describe the three components of the key-scanning procedure as the entry, the contact-scanning, and the processing sections. Additionally, you must provide a separate initialization routine to set up the global variables to their default state on power up before key scanning can begin.

Local working storage is allocated for the elements called **KEY-COUNTER**, **KEY-NUMBER**, and **KEY-HIT**. The entry code simply consists of clearing **KEY-COUNTER** and **KEY-HIT** to zero; **KEY-NUMBER** may be left indeterminate.

The contact-scanning procedure consists of a repetitive loop that checks the state of each key. You will best understand the function of the loop from a quick definition of the local variables: **KEY-COUNTER**, a counter that increments each time a key is checked; **KEY-HIT**, a counter that is incremented each time a key closure is detected; and **KEY-NUMBER**, a register to which the **KEY-COUNTER** is copied when a key closure is detected. The loop terminates when **KEY-COUNTER** reaches its terminal value, indicating all keys have been checked.

At the conclusion of the **contact-scanning** loop, control is passed to the process code where a decision is made as to whether a valid key was been

LCR - Hz - dBm - True RMS

 

Model 94

.1% ACCURACY on DC Voltages

TRUE RMS PLUS

MAX/MIN/AVERAGE MEMORY RECORD
RELATIVE MODE / DATA HOLD

DC/AC VOLTMETERS

DC Range: 400mV, 4V, 40V, 400V, 1000V

AC Range: 400mV, 4V, 40V, 400V, 750V

DC/AC AMP METERS

DC/AC Range: 400uA, 4mA, 40mA, 400mA, 10A

OHM METER

Range: 400, 4K, 40K, 400K, 4M, 40M, 4000M Ohm

FREQUENCY COUNTER-AUTORANGING

Range: 4KHz, 40KHz, 400KHz, 4MHz (Trigger Low), 20MHz (Trigger High)

LOGIC PROBE

AUDIBLE CONTINUITY TESTER

CAPACITANCE TESTER

Range: 4nF, 40nF, 400nF, 4uF, 40uF

DIODE TESTER

Range: -25.7 dam to 59.7dBm

INDUCTANCE TESTER

Range: 40mH, 400mH, 4H, 40H

10 MEGA OHM IMPEDANCE

10A HIGH-ENERGY FUSE PROTECTION
AUTO SLEEP & AUTO POWER OFF

WATER & DUST RESISTANT

MODEL 94 COMES COMPLETE WITH
TEST LEADS, YELLOW HOLSTER,
TILT STAND, BATTERY & FUSE

Stock No. 990111 **\$199⁹⁵**
ONLY

2 YEAR WARRANTY

KELVIN

10 HUB DRIVE, MELVILLE, NY 11747
(800) 6459212
(516) 756-1750 (516) 756-1763/FAX

detected, and if so, if the key has already been debounced. This operation consists of first checking KEY_HIT. Only single key hits are allowed, so the routine terminates if KEY_HIT is anything other than one.

If KEY_HIT is one, then the global variable LAST-KEY is consulted. If KEY-NUMBER is equal to LAST-KEY, the Boolean global DEBOUNCED is checked. If LAST-KEY equals KEY-NUMBER and DEBOUNCED is zero, this key is being seen for the second successive pass, has not yet been recognized, and is therefore valid. DEBOUNCED is set to one and KEY-NUMBER may be used as an index into a lookup table to extract the decoded value for this key, which can be a scan code or an ASCII code depending on the usage. The decoded key is then returned to the calling program with the exit code set to the appropriate state. Figure 1 summarizes these steps.

HARDWARE TECHNIQUES

Having established how you want to do the general keyboard scanning, turn your attention to combining the general principals with some hardware. The classic method of interfacing a keyboard to a microcontroller is based on the matrix scan, where the key contacts are connected as an array consisting of driven rows and scanned columns. With the rows diode-coupled as shown, the circuit is able to dis-

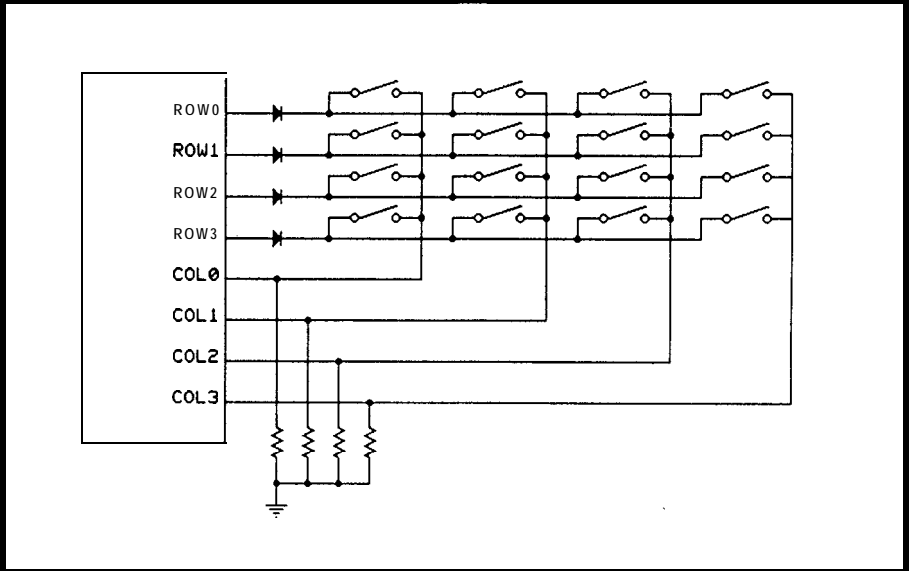
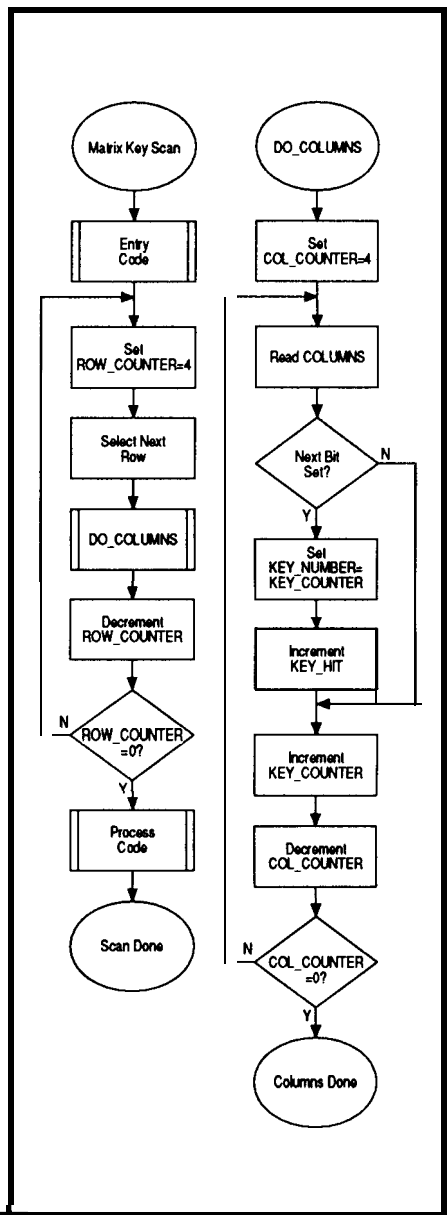


Figure 2-A popular keyboard scanning scheme uses one line for each row and one for each column. Each row is successively energized and the columns are read to detect a keypress.

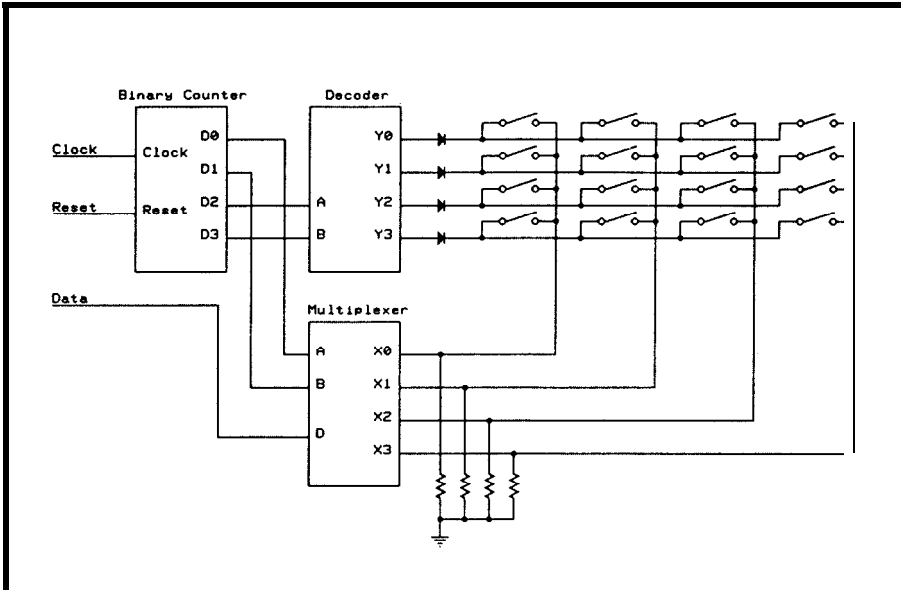




Figure 3—When port lines are scarce, a little more hardware drops the interface down to just three lines. A 4-M counter is used to cycle through the rows and columns automatically.

criminate at least two simultaneous key closures at a time, although the algorithm does not make use of this capability. In any case, this arrangement prevents the jamming of two

outputs together if someone presses the wrong two keys at the same time.

The benefit of this organization is the reduction in the number of port pins required for the interface. For example, if you scan 16 keys, four outputs and four inputs will be consumed. To proceed, turn on a single-drive line and then read the columns. Repeat by driving each row in sequence. Figure 2 shows how this process is done.

Port pins are often in short supply. Similarly, a congested PCB layout may mean you need to conserve lines because the keyboard is on another card or even located remotely to the controller. With a little extra hardware, you can get by using just three port pins: two outputs and one input. As shown in Figure 3, a decoder (in this case using active-high output) and a multiplexer operate under control of a binary counter to perform the functions done previously in firmware. Here, the hardware performs the sequencing. The counter's reset pin initially resets the matrix, which is

  

The Best Laid Plans Begin With ViewTask!™

Chart Your Course To Improved Real-Time Design, Processor Selection, and System Prototyping

Find the shortest route through your next embedded system project with ViewTask! from US Software.

With ViewTask!, you can design an operating task set on your PC—complete with timing parameters and your choice of processor—to run a series of “what if scenarios. Then use your monitor to evaluate worst-case timings and verify task set viability—you can even generate executable tasking code—all for only \$495. Chart a course to success with ViewTask!



800-358-7087 USA
503-641-8446 FAX 503-6442413
14215 NW Science Park Drive
Portland, OR 97229

U S SOFTWARE®

© 1992 US Software is a registered trademark and ViewTask! is a trademark of United States Software Corporation

DIAL-IT-ON




\$149.00

No one to turn your computer on? Dial-It-On turns on your computer via the telephone.

- Security ring sequence lets only you turn on your computer
- 6 Outlets at 10 AMPs each
- 6 Rocker lighted switches
- Surge protection for both the AC and phone line
- Fits nicely between the computer and monitor

P-MODULE

 

\$149.00

Need to interface your electronic equipment to PC? P-Module saves the IO s/of and interfaces your electronic equipment to any IBM PC compatible through the parallel port.

- Addresses 256 16-bit or 512 8-bit read/write registers through the parallel port
- Microsoft and Turbo C software drivers
- Turbo Pascal software driver
- Includes the hardware/software design examples
- No power supply needed
- Enclosed in small and sturdy plastic box

DROM128K EPROM EMULATOR



\$349.00

Eliminate wasting time burning EPROM with DROM128K during the development cycle. Plug DROM128K in place of EPROM and download your code as many times as you need through the parallel port.

- Emulates two 2764 through 27010 (1 meg.)
- Dual ROM emulation for 8-bit or 16-bit operation
- Battery back-up
- Optional external 9 VDC or uses the target's power
- Fast loading 10K/sec.

- *Accepts Intel Hex, Motorola S, and Binary files
- Fast editor allows changes in the download code
- Source code written entirely in C available for user modification
- All cables and accessories Included

For more information or to order contact:
QUALINK PRODUCTS

6194784678 • (FAX) 619-578-5678

7564 Windy Ridge Road • San Diego, CA 92126


 


Figure 4—The simplest keyboard interface is to run each switch to its own port line. Such simplicity doesn't eliminate the need for driver software, however.

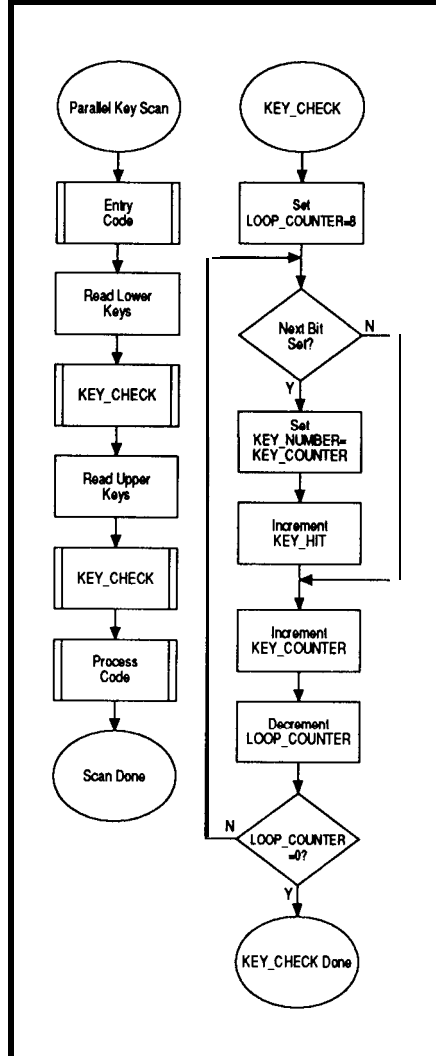

then sequenced by the issuing of successive pulses on the clock line.

As the figure shows, the counter's low-order outputs connect to the multiplexer with the high-order bits tied to the decoder. The selection of row 0 and column 0 occurs at reset. As the counter is clocked, the multiplexer sequences through all the columns until the next row is picked, then it repeats until all the keys have been checked. Notice in this arrangement that the hardware functions of asserting reset and emitting clock pulses closely follow the software counterparts of the algorithm.

If you're really pressed for pins, you can use a little more hardware to eliminate the reset line. A retriggerable one-shot releases the counter reset when the clock pulses begin. At the conclusion of the scan, reset will reassert when the one-shot times out.

Use to your advantage the selection of the key at row 0, column 0 at counter reset in systems that include a self-power-down capability. Here you may realize this circuit in CMOS to

reduce current usage and run it off the RAM backup power. The active key can be used as a power button, providing the stimulus to the power control circuitry to return the system to a powered state. Just make sure you properly isolate the data line so as not to backfeed the unpowered key input port pin.

The nice thing about this three-wire interface is, in principal, it can be extended to service fairly large keyboards. (I've gone as high as a hundred keys.) You may have to use larger decoder and multiplexer chips, but as far as the firmware is concerned, all you do is increase the terminal value for KEY-COUNT in the contact scan loop and provide a larger lookup table.

At the other extreme, you may be faced with interfacing a keyboard that has connections to each contact with a single common. The electrical interface of course is trivial; you just bring all the keys in on individual port pins. You're all hooked up, and at first a key-scanning algorithm may seem unnecessary, but you're still faced

with performing the fundamental keyboard functions. Figure 4 shows that the basic algorithm still holds.

The algorithm I've presented is intentionally rudimentary, keeping with the concept of the soft machine I alluded to earlier. If you require additional functionality, consider adding a layer of code between the application and driver levels rather than tweaking the driver itself. For instance, if you want to remap the keys in response to the changing needs of the application, place these functions in this stub code.

You can place shift functions in the stub code also, but with the driver I've described, these would have the shift key operate in an alternating fashion rather than in the conventional sense, because the driver only returns single key hits. Actually, I find this action desirable usually for the types of embedded instruments that have small front-panel keyboards, which aren't all that easy to use anyway. If you want a traditional shift key arrangement, you can run the shift

key outside the matrix... or I suppose you can tweak the driver.

I'll let you in on a little secret. Over the years, I've developed equipment that's run under control of various processors and controllers, and interfaced to dozens of strange and wonderful keyboards, but I've only had the need to develop one keyboard driver algorithm. When developing soft hardware, always make sure you understand the magnitude of the task and the needs of the system, make the right decisions, and work smart. Being wasteful is foolish; there is no virtue in drudgery. □

John Dybowski has been involved in the design and manufacture of hardware and software for industrial data collection and communications equipment.

IRS

428 Very Useful

429 Moderately Useful


430 Not Useful

Z80, Z180, HD64180, HD647180 In-Circuit Emulators

Affordable state-of-the-art in-circuit emulation for Z80 family processors. Increase your productivity with features like:

- Symbolic and C Source Level Debugging
- Pull-Down Menus and Command Line interface
- Complete Context-Sensitive Help
- Real Time Emulation up to 12 MHz
- Serial Interface works on any PC, even on laptops.

 Z80
Z180
Z84C13
Z84C15
HD64180
HD647180
TMP84C015



Satisfaction guaranteed with a risk free 15 day trial. Rentals also available. **Call or write today for more information/**

Control Resources

19042 San Jose Unit S, P.O. Box 8694
Rowland Heights, CA, 91748
818/912-5722 (Voice) 818/854-1439 (Fax)

The
only
8051/52
BASIC
compiler
that is
100 %
BASIC 52
Compatible
and
has full
floating
point,
integer,
byte & bit
variables.

- Memory mapped variables
- In-line assembly language option
- Compile time switch to select 8051/8031 or 8052/8032 CPUs
- Compatible with any RAM or ROM memory mapping
- Runs up to 50 times faster than the MCS BASIC-52 interpreter.
- Includes Binary Technology's SXA51 cross-assembler & hex file manip. util.
- Extensive documentation
- Tutorial included
- Runs on IBM-PC/XT or compatible
- Compatible with all 8051 variants
- **BXC51 \$ 295.**

508-369-9556

FAX 508-369-9549



Binary Technology, Inc.

P.O. Box 541 • Carlisle, MA 01741



CONNECT TIME

conducted by Ken Davidson

The Circuit Cellar BBS
300/1200/2400 bps, 24 hours/7 days a week
(203) 871-1988—Four incoming lines
Vernon, Connecticut

*We're going to cover a few new topics in this installment of **ConnectTime**. The first thread deals with sensing engine knock in a racing motorcycle. Next, we move into high-speed data collection. Finally, we'll make some noise-white noise, that is.*

Msg#:58203

From: KELLY DRESSER To: ALL USERS

Has anyone out there worked with pressure sensing in internal combustion engines? What I'm looking for is essentially a poor man's Kistler. I don't need absolute accuracy as much as low cost and ease of use. I want to sense the pressure peak and have enough frequency response to detect uncontrolled combustion ["knock"] in a single-cylinder four-stroke 600cc racing motorcycle engine. It's air cooled, which adds even more of a heat problem to an already messy sensing environment. Has anyone used any unconventional or clever techniques to measure [or infer] the pressure profile [with respect to crank angle]?

Msg#:58227

From: MIKE RAPP To: KELLY DRESSER

If you really need to get cylinder pressure data then I think there are no cheap and dirty solutions. In your application, you might be able to avoid the instrumented spark plug by drilling the head and directly mounting a pressure sensor [no need to worry about water jackets]. Your data sampling and storage will be nontrivial (1" rotational resolution at 6000 RPM will need 36,000 samples/sec.).

On the other hand, if what you actually need to do is detect detonation (knock), then there is a much simpler and cheaper approach. All you need to do is to detect the audio frequency sound (pinging) produced by the detonation. It's much more commonly heard in a car than on a bike, but will be produced by any engine that is driven into detonation.

The standard approach is to mount a vibration sensor on or near the head and use the filtered output to indicate detonation. This is already being done in production of certain cars and trucks (particularly with turbo charging). The frequency of interest is somewhere around 6 kHz in the automotive application. Your aluminum air-cooled engine might be different. You can find out by mounting up a sensor and smacking the head area with a hammer. The

predominant frequency produced by the sensor should be usable for detecting detonation. (Hammering on the engine is how the automotive sensors are tested!)

Best source for a sensor might be the parts department at a GM dealer. This technique is even used in laboratory (dyno) testing since the vibration sensor will detect detonation well before even the best operator can hear it.

Msg#:58492

From: KELLY DRESSER To: MIKE RAPP

Thank you, Mike, for your reply. You confirm my general hunches about how I'm going to get the info I want. I'm still hoping for some unorthodox manner in which to skin this cat. Already, with a water-cooled two-stroke I've had much better than beginner's luck at sensing the cylinder pressure by epoxying the sounding disc from a piezo squeaker on a flat spot next to the spark plug. Got an incredibly clean and strong signal. The piezo even survived the temperature, but did display a whopping DC signal that varied with the rise and fall of the head temperature. However, an air-cooled four-stroke is a lot hotter, a lot noisier (mechanically), and there's no place to stick the thingumy.

Mr. Kistler makes good stuff, but it's out of reach in cost. Maybe someone has found another rugged sensor that will work in this application. Your suggestion about using a resonating piezo sensor from an automobile engine is a technique I want to try last, since I really do want a pressure trace (for some combustion phasing fiddles) plus be able to detect knock, and doing both with the same sensor still attracts me.

I've been through all the recent SAE papers, but without anything looking really good, except maybe an under-spark plug washer (piezo again) that Nissan (I think) has used in the past. Any experience by anyone out there with such a sensor?

As far as having a fire hydrant of data pointed at me, I'm not yet worried—some combination of digital and analog techniques can minimize that. In any case, these bikes are running on an inertial dyno that a friend and I constructed (it's just like Dynojet's) and there's a PC already in the vicinity ready to swallow more data.

I'll keep on plugging, looking for an elegant and/or cheap (especially) solution to this problem.

CONNECT TIME

what's the best way to **sample** a 50-MHz signal without paying an **arm** and a **leg**? In the next discussion, we look at several different techniques and their tradeoffs.

Msg#:58226

From: TERRY NORRIS To: ALL USERS

I am in need of help. My problem is I want to do some analog-to-digital conversion at very high speeds. The data will eventually be sent to a PC. Problem is, the signal being sampled can range up to around 50 MHz, and that means much higher sampling rates. A PC would rather format a hard drive than be forced to process data at that rate. The fastest ADC I can find supports a 100-MHz sampling rate (not good enough for a clear display without averaging).

I believe if the signal were shifted into a high-speed analog shift register, I could slowly shift the signal out at a sample rate I could use. I know there are analog shift registers out there for reverbs and the like, but are there high-speed shift registers? Any help would save some headaches.

Msg#:58248

From: GUY RESH To: TERRY NORRIS

Well, depending on your application, there ARE 100-MHz DSO boards for the PC line. Give Gage Applied Sciences Inc. a call (514/337-6893). They've got a few boards ranging from around \$1500 up to \$10,000. Steep, but if you want to play with those frequencies, you're going to need the "proper" tools (am I actually saying this??? :). The reason I say that is I'm in the same ballpark, and want to do the same thing (or so it sounds). If you don't mind a repetitive sampling, there are "cheaper" boards on the market that sample at 20 MS/s with a 50-100-MHz bandwidth. All depends on your requirements.

Rolling your own is going to be challenging to say the least; Analog Devices and TRW are two of the major suppliers of ADC chips that will do what you want-be prepared for >\$75 per chip, though. [Heck, Tek will sell you a single chip for \$1875.00 if you want REAL quality!] G'luck.

Msg#:58369

From: TERRY NORRIS To: GUY RESH

It is interesting that you mention Tektronics, because I found that they used an analog shift register in their 2430A oscilloscope. They used a charge-coupled device (CCD for acronym people) to shift the data in at 100 MHz, then shifted out the data to a (lower priced than \$1870) analog-to-digital converter. I also have data on Analog Devices ADCs, and still wish for more knowledge, but at least I am not out in left field.

Msg#:58298

From: MATTHEW TAYLOR To: TERRY NORRIS

I just left a scientific government agency where one of the guys was working on a 1-GHz data acquisition box for ground-penetrating radar. The converters were from Tektronix and the boards consisted of 50+ amps of ECL logic. To get the required throughput, there were several banks of converters, and each was fired in succession over and over until the 4-ns bank of static RAM was filled up.

Maybe this technique would work for you application: stagger several slower (and cheaper) converters and fire them in order to get up to the speed you need.

Msg#:58422

From: TERRY NORRIS To: MATTHEW TAYLOR

Unless I learn something new, it seems the most effective way to build this circuit is to have a 100-MHz ADC working at full speed to store data in some high-speed RAM. Then have the RAM accessed by a DSP or two. I don't think the CCD that Tektronics uses will be too cost effective (I hear now that if something goes on the 2430 'scope, it is the CCD). All of this will yield what I want [if I

Cross-Assemblers from \$50.00 Simulators from \$100.00 Cross-Disassemblers from \$100.00 Developer Packages from \$200.00 (a \$50.00 Savings)			
Make Programming Easy Our Macro Cross-assemblers are easy to use. With powerful conditional assembly and unlimited include files.			
Get It Debugged -- FAST Don't wait until the hardware is finished. Debug your software with our Simulators.			
Recover Lost Source! Our line of disassemblers can help you re-create the original assembly language source.			
Thousands Of Satisfied Customers Worldwide PseudoCorp has been providing quality solutions for microprocessor problems since 1985.			
Processors			
Intel 8048	RCA 1802, 05	Intel 8051	Motorola 6805
Motorola 6800	Motorola 6801	Motorola 68HC11	WDC 65C02
Hitachi 6301	Motorola 6809	MOS Tech 6502	NSC 800
Rockwell 65C02	Intel 8080, 85	Zilog Z80	
Hitachi HD64180	Mot. 68k, 8,10	Intel 8096, 196kc	
New Zilog Z8 Zilog Super 8 • All products require an IBM PC or compatible.	For Information Or To Order Call: PseudoCorp 716 Thimble Shoals Blvd., Suite E Newport News, VA 23606 (804) 873-1947 FAX: (804) 873-2154		

CONNECT TIME

use repetitive sampling) although I now must use ECL all the way till the DSP accesses the data (I hoped to leave the high frequencies on the other side of the ADC). Well, if anyone knows who I can contact about high-speed RAM, drop me a line, any help received is always greatly appreciated, including that already received.

Msg#:58491

From: JOE PIERSON To: TERRY NORRIS

I too am working on a high-speed data acquisition system (I am using the Analog Devices AD9038 300-MHZ ADC) and have the following comments/suggestions concerning your problems:

1) Fast ECL/CMOS/BiCMOS memories can be obtained from Cypress Semiconductor, IDT, Mosel, and Motorola.

2) You can latch the data coming out of the ADC with a ECL latch and then use an ECL-to-TTL converter so that everything after the converter is TTL/CMOS logic (interleave the slower CMOS memory to achieve the desired sampling rate). You will find that CMOS memory is much cheaper if you require deep memory.

3) If you only need 100 MHZ, consider using the

Analog Devices AD9058. It has two matched 8-bit 50-MHZ ADCs on one chip with TTL outputs. Simply send your analog input into both of the ADCs and clock them out of phase, you will have your 100-MHZ system without any ECL logic. Cypress has CMOS memories that will store data at 50 MHz so you won't have to mess with interleaving. The AD9058 is about \$55 in 100s.

4) If you don't want to bother with repetitive sampling, you might want to check out some of Sony's ADCs. They make some very fast 8-bit ADCs (\$300 will get you a 500-MHz ADC).

5) You mentioned that you want to measure 50-MHZ signals; are these periodic or one-time events? If they are periodic then don't bother using the high-speed ADCs; they won't buy you anything. HP uses 20-MHz ADCs in their 20-GHz scopes. Just remember to put a sample-and-hold in front of the ADC since most of the ADCs in the 20-MHz range have lousy full-power bandwidth.

Msg#:58549

From: TERRY NORRIS To: JOE PIERSON

You have closed the link on a difficult path for me. I

FINALLY

A Universal Tool for the Firmware Developer

More flexible than any Microprocessor ICE
PROMICE doesn't use a microprocessor pod
and handles any word size (8,16,.....2048 bits).


More versatile than intrusive ROM based debuggers
PROMICE doesn't use your target system's I/O resources
yet allows you to debug firmware contained in ROM.

More powerful than simple ROM emulators
PROMICE provides complete, source level
debugging and full memory control.

PROMICE ... The Universal Firmware Development Tool.



 Grammar
Engine
Inc.
921 Eastwind Dr.
Westerville, OH 43081
Tel: (614) 899-7878
Fax: (614) 899-7888




GNU Cross Compilers

Are you looking for a 68xxx or 386/486 ANSI C cross compiler for DOS OR UNIX? Is complete source code to your compiler important to you? How about a complete Standard C library implementation, including floating point emulation?

Hundred Acre Consulting is now offering GNU C support packages in several cross **compiler configurations**. Each Package includes the GNU ANSI C compiler from the Free Software Foundation, a complete Standard C library with hooks for your own file system implementation, several support utilities, and one year of support at no additional charge. Platforms supported include MS/DOS, Sun 3 and Sun 4 with SunOS 4.1, and Interactive or SCO UNIX. Call today for more information!

GNU Support Package: \$495

 

Hundred Acre Consulting
1260 Terminal Way Suite 26, Reno, NV 89502
Phone: +1-702-329-9333 Fax: +1-702-329-9566
Email: info@pooh.com

#171

CONNECTIME

would like to have the address and phone number of Cypress. The more I find the more challenging it gets, but never too much challenge. My signals are "not guaranteed to be periodic," as much as I wish anything in life had a guarantee. I am going to look at what you gave me, and I'll leave a message if anything stops me.

Msg#:58552

From: JOE PIERSON To: TERRY NORRIS

You can get hold of Cypress at (800) 858-1810; try to get their CMOS/BiCMOS data book. Also, evaluate their CY7C443 Synchronous FIFOs. These can store data at 70 MHz (using the fastest non-ECL memory device you can buy). It is also very clean to work with since it latches all data and control lines on the rising edge of the clock input (read the data sheets). In addition, FIFOs in general require the smallest part count of any memory storage system since they do not require the generation of address inputs as SRAMs do (they generate it internally). The disadvantage? You guessed it: they're expensive, about \$50 for 2K bytes. But they are so easy to use that the probability is high your system will work the first time.

Finally, it seems engineers spend a lifetime trying to minimize noise in their circuits. What about when you need to deliberately generate noise? Digital or analog, there's more than one way to do it.

Msg#:59034

From: NELSON CHANE To: ALL USERS


I am trying to simulate a white noise generator for a project I'm working on. I understand this can be accomplished using some shift registers and XORs. The bandwidth I want for the noise is DC to 5 kHz. I've checked a few sources: TI and National Semiconductor had white noise generators, but they've recently obsoleted them. Can anyone help me find a solution to this? Can pin diodes and an amplifier be used? Any ideas?

Msg#:59043

From: RUSS REISS To: NELSON CHANE

Yes, you can use a feedback shift register to generate pseudorandom noise ("pseudo" since it actually repeats at the length of the sequence). There are particular feedback taps that permit maximal-length shift codes/sequences for

 8031 MICROCONTROLLER BOARD WITH 128 kB FLASH EPROM



- Monitor and Flash Manager software are provided in the protected boot block
- Parameters and main blocks are user programmable and erasable on-board.
- 128 kB Flash EPROM has an 8 kB boot block, two 4 kB parameter blocks and one 112 kB main block * Software source code is included. *
- Serial RS232 with MAX232 chip • +5V and +12V supplies
- Two 20 pin headers for port lines and expansion • 11.0592 MHz Clock Speed

Assembled and tested board with documentation.....\$ 80.00

Kits, power supplies and application software are available. Ask for more information and price list.



L.S. ELECTRONIC SYSTEMS DESIGN
2280 Camilla Rd., Mississauga,
Ontario, Canada L5A 2J8
Phone/Fax: (416) 277-4893 BBS: (416) 277-0047

Victor Now includes color reduction Image Processing Library

- ▶ Load and save TIFF/PCX/GIF/TGA/bin
- ▶ Work with large images in expanded or extended mem
- ▶ Powerful grayscale and color image processing: brightness, contrast, sharpen, outline, linearize, overlay, matrix convolution, rotate, resize, etc
- ▶ Color reduction: 24-bit to 256 or fewer colors, display super VGA images on EGA
- ▶ Control ScanJet scanner
- ▶ Print image at any size on laser printer
- ▶ Display on EGA/VGA/super VGA up to 1024 x 768, 256 colors or 800 x 600, 32K colors

Call or fax to order
314-962-7833

VISA/MC/COD

Victor Image Processing Library. \$195

Victor Image Processing Library
with IDEC 512 x 512 frame grabber. \$499

Ca tenary Systems

470 Belleview St Louis MO 63119
voice/fax 314-962-7833

Victor Image Processing Library supports Microsoft and Borland C/C++ compilers.
No royalties. Source code available.

CONNECTIME

various size registers. But if you'd rather do it in analog, you might consider a back-biased diode (e.g., a zener diode capacitively coupled to an amplifier). You won't find that the spectrum is flat from DC to 5 kHz, but you can wave-shape it with filters as required.

Msg#:59074

From: NELSON CHANE To: RUSS REISS

Thanks for the tips. I heard from one manufacturer—NoiseCorn—that they make noise generators for the RF and microwave industry. I can use a noise diode that they produce and capacitively couple to an op-amp as you suggested, but the cost of the diode is \$18.00. I was hoping for a cheaper solution. I am considering the digital approach and will try to program a FPGA for the prototype. The only problem is how to characterize the noise [using Fourier transforms?] and plot the results using, say, MathCad.

Msg#:59144

From: RUSS REISS To: NELSON CHANE

Forget the "noise diode." It's probably spec'ed for good performance into the microwave region, but not for the

low-frequency audio that you need. Try simply biasing a zener through a resistor and feeding that to an audio amp. See what you hear. :-)

For those low frequencies, you could probably connect a simple ADC to your PC and do an FFT in software. Maybe not in real time, but who cares? Just store some data, process it, and see what the spectrum is. You can "flatten" it by passing the signal through an inverse filter—and I'll bet some simple HP or LP stages will do fine once you find the slope of the frequency response of the noise source.

I suspect this wave shaping will be required for your digital shift-register source too. You don't need fancy gate arrays and stuff; all you need is a big shift register and a few XOR gates to create the feedback. See any college text on "signals and noise" or "coding theory" for the design. They come under the title "Maximal Length Sequence Generators" or "Pseudorandom Codes."

Msg#:59320

From: NELSON CHANE To: RUSS REISS

I tried what you suggested: a zener diode reverse biased, using 15-V source and 1M resistor; it generated noise just

REMOTE POWER CARD!

3 VERSIONS:

RESET

WATCHDOG RESETS PC IF IT HANGS ON HARDWARE OR SOFTWARE REASONS

PHONE



TURN ON PC WITH PHONE, SHARE VOICE / MODEM LINE, CONTROL AC APPLIANCES

TIMER

WAKEUP OR SHUTDOWN PC, LATE NITE BACKUP / MODEM, CONTROL AC APPLIANCES

95\$ 27\$ OEM

  ALL MVS CARDS INCLUDE ASM, BASIC, AND C SOURCE FOR PC OR SBC



8 CHAN ADC

DATA ACQUISITION, SERVO CTL, AUDIO 8-BIT RESOLUTION 22KHZ SAMPLE RATE SHARP CUTOFF ANTI-ALIAS FILTER CREATE STEREO BLASTER (VOC) FILES

95\$

2 CHAN DAC

VOICE MAIL, MUSIC, ALARMS, CTL VOLT 8-BIT RESOLUTION 44KHZ SAMPLE RATE PLAYS MONO / STEREO BLASTER FILES FUNCTIONS AS DIGITAL ATTENUATOR TOO

75\$



MVS BOX 850 MERRIMACK, NH (508) 792-9507

5 YEAR LIMITED WARRANTY P I N G I N U S A

BCC52 BASIC-52 Computer/Controller

The BCC52 Computer/Controller is Micromint's hottest selling standalone single-board microcomputer. Its cost-effective architecture needs only a power supply and terminal to become a complete development or end-use system, programmable in BASIC or machine language. The BCC52 uses Micromint's 80C52-BASIC CMOS microprocessor which contains a ROM-resident 8K-byte floating-point BASIC-52 interpreter.

The BCC52 contains sockets for up to 48K bytes of RAM/EPROM, an "intelligent" 2764/128 EPROM programmer, three parallel ports, a serial terminal port with auto baud rate selection, a serial printer port, and is bus-compatible with the full line of BCC-bus expansion boards: BASIC-52's full floating-point BASK: is fast and efficient enough for the most complicated tasks, while its cost-effective design allows it to be considered for many new areas of implementation. It can be used both for development and end-use applications

PROCESSOR

- 80C52-BASIC, 8-bit CMOS microcomputer
 - jumper-selectable conversion to 80C31/80C32 functionality
 - 8K bytes ROM (full BASIC interpreter)
 - 256 bytes RAM
 - three 16-bit counter/timers
 - 32 I/O lines
 - 11 MHz system clock
 - 6 interrupts
- ### MEMORY
- expandable to 62K bytes
 - five on-board sockets
 - up to four 6264 (8Kx8) static RAM
 - either an 8K 2764 or 16K 27128 EPROM

Input/Output

- console I/O RS-232 serial port
- line printer RS-232 serial port
- three 8-bit programmable TTL-compatible parallel I/O ports using a 8255 PPI
- alternate console RS-422/RS-485

To Order Call
1-800-635-3355
Tel: (203) 871-6170
Fax: (203) 872-2204

		SINGLE Qty.	100 Qty.
BCC52	BASIC-52 Controller Board with 8K RAM	\$189.00	\$149.00
BCC52C	Lower-power all-CMOS version of the BCC52	\$199.00	\$159.00
BCC52I	Full industrial temperature range	\$294.00	\$220.00
BCC52CX	CMOS, Expanded BCC52 w/32K RAM	\$259.00	\$189.00

MICROMINT, INC. 4 Park Street, Vernon, CT 06066

See us at the Embedded Systems Conference—Booth #919

#175

CONNECTIME

fine. However, when coupling to an op-amp (LM318) and setting the gain to about 100, I found that the parasitic capacitance of the coupling cap (1 μF) swamped the noise and gave about a 20-MHz oscillation. Tried different caps from 10 pF to 10 μF and no go. How can I AC couple the zener diode to the op amp? Am I using the wrong op-amp? The configuration of the op-amp is: -ve input has a 200k resistor to ground; a 2M feedback resistor from -ve input to output in parallel with a 200-pF cap; the +ve input has a 150k resistor to ground and is also where the coupling cap from the zener circuit is connected.

Msg#:59363


From: RUSS REISS To: NELSON CHANE

Try coupling the noise source into the negative input. Sounds more like breadboard/prototype problems wherein the high positive gain is causing the oscillation. As an inverting stage it might be much more stable. The noise won't care that it's "upside down." :-)

Msg#:59371

From: PELLERVO KASKINEN To: NELSON CHANE

 Here is a circuit that is useful for true white noise generation:




AD1 & 2 are preferably matched avalanche diodes ("zener" diodes with over 5.1-V nominal voltage). The higher nominal voltage you select, the more noise amplitude you get, but also the narrower the bandwidth. Staying around 5.1 V, you may get flat response to over 20 MHz, depending on layout-induced capacitances and the buffer input capacitance after R3 and R4. Of course, you might choose to have two buffers before summing the two signals.

The values of R1 and R2 should be selected so that the diode currents are above the knee, but not too much. Probably somewhere in the 0.2- to 1.0-mA range is fine. The

SCHEMATIC DRAWING FOR WINDOWS

ISIS ILLUSTRATOR combines the high functionality of the ISIS product line with the graphics capabilities of Windows 3 to give you unparalleled control of the appearance of your drawings. When the drawing is complete, you can output to any printer supported by Windows, or the drawing can be read into most Windows DTP and WP programs.

FEATURES

 

- RUN under Windows 3.x
- Full control of drawing appearance including line widths, fill styles, fonts, colors and more
- curved or angular wire corners.
- Fully automatic annotator.
- Comes complete with component libraries.
- edit your components directly on the drawing.
- Handy for 2D drawing too.
- Drives all window printer devices including POSTSCRIPT and color printers.
- Loads ISIS SUPERSKETCH and DESIGNER files directly.

ISIS ILLUSTRATOR ONLY \$349 US !!!

R4 SYSTEMS Inc.
P.O. Box 451
West Hill, Ontario
Canada M1E 4Y9
(416) 399-0943

Free Evaluation Package
Write or Call Today

EPROM PROGRAMMERS

Stand-Alone Gang Programmer

\$750⁰⁰



- Completely stand-alone or PC-driven
- Programs E(P)ROMs
- 1 Megabit of DRAM
- User upgradable to 32 Megabit
- 3/.6" ZIF Sockets, AS-232, Parallel to and Out
- 32K Internal Flash EEPROM for easy firmware upgrades
- Quick Pulse Algorithm (27256 in 5 sec. 1 Megabit in 17 sec.)
- 2 year warranty
- Made in the U.S.A.
- Technical support by phone
- Complete manual and schematic
- Single Socket Programmer also available. \$550.00
- Split and Shuffle 16 & 32 bit
- 100 User Definable Macros 10 User Definable Configurations
- Intelligent Identifier
- Binary, Intel Hex, and Motorola S
- 2716 to 4 Megabit


Internal Programmer for PC

\$139⁹⁵

New Intelligent Averaging Algorithm Programs 64A in 10 sec 256 in 1 min 1Meg (27010, 011) 27C2001, MCM 68764.2532.4 Megabits

- Automatically sets programming voltage
- Load and save buffer to disk
- Binary, Intel Hex, and Motorola S formats
- No personality modules required
- 1 Year warranty
- 10 days money back guarantee
- Adapters available for 8748, 49, 51, 751, 52, 55, TMS 7742, 27210, 57C1024, and memory cards
- Made in U.S.A.

2 ft. Cable 40 pin ZIF

 

EMPDEMO.EXE available BBS (916) 972-8042

NEEDHAM'S ELECTRONICS

4539 Orange Grove Ave - Sacramento, CA 95841
(Monday-Friday 8 am - 5 pm PST)

Call for more information

(916) 924-8037

FAX (916) 972-9960

C.O.D.



#1


CONNECTIME

positive and the negative supplies have to be reasonably higher than the avalanche voltages.

A more expensive system replaces R1 and R2 with constant-current "diodes" such as the 1N5297. Then you would not need more than a couple of volts above the avalanche voltage for the supplies.

Why the two diodes? It turns out that the noise distribution from a single diode is skewed to one polarity. When you generate both polarities and combine them as shown, you get much improved noise quality.

This circuit produces a signal in the millivolt level, so you would need an op-amp to amplify it to your 3-V levels. On the same amplifier, you can do whatever band limiting and maybe amplitude limiting as well you may need. Just add a capacitor over the feedback resistor for the bandwidth. Add two 3.3-V zener diodes, connected in series with opposite directions over that same feedback resistor to make about a 4-V maximum output. Then use a voltage divider or potentiometer for the final amplitude setting.

By the way, what the commercial noise signal generator diodes contain is pretty much along this description-so now you know...

We invite you call the Circuit Cellar BBS and exchange messages and files with other Circuit Cellar readers. It is available 24 hours a day and may be reached at (203) 871-1988. Set your modem for 8 data bits, 1 stop bit, no parity, and 300, 1200, or 2400 bps.

ARTICLE SOFTWARE

Software for the articles in this and past issues of *The Computer Applications Journal* may be downloaded from the Circuit Cellar BBS free of charge. For those unable to download files, the software is also available on one 360K IBM PC-format disk for only \$12.

To order Software on Disk, send check or money order to: The Computer Applications Journal, Software On Disk, P.O. Box 772, Vernon, CT 06066, or use your VISA or Mastercard and call (203) 8752199. Be sure to specify the issue number of each disk you order. Please add \$3 for shipping outside the U.S.

IRS


431 Very Useful

432 Moderately Useful

433 Not Useful

MICROCONTROLLERS

 - C Programmable
- Data Acquisition
- Control / Test
- Excellent Support
- From \$159 Qty 1
- New Keyboard Display Modules



Use our **Little Giant™** and **Tiny Giant™** miniature controllers to computerize your product, plant or test department. Features built-in power supply, digital I/O to 48t lines, serial I/O (RS232 / RS485), A/D converters to 20 bits, solenoid drivers, time of day clock, battery backed memory, watchdog, field wiring connectors, up to 8 X 40 LCD with graphics, and more! Our \$195 interactive **Dynamic C™** makes serious software development easy. You're only *one* phone call away from a total solution.

Z-World Engineering

1724 Picasso Ave., Davis, CA 95616
(916) **757-3737** Fax: (916) 753-5141
Automatic Fax: (916) 753-0618
(Call from **your fax**, request catalog #18)

► Project Parts ◀

IR3C07 laser diode controller	2.95
IS1 U60 38 kHz IR receiver	4.99
LD273 dual IR LED (<i>bright!</i>)	2.10
IRLEDs: 10-TLN1 10, 1-LD273	5.00
Excellent IR filter (<i>opaque!</i>)	6.75
MC1 45030 IR encoder/decoder	6.75
DS1231 power monitor	9.90
DS2400 silicon serial ID (2 pc)	8.40
MT8809 8x8 analog crosspoint	11.50
MAX134 digital multimeter	33.00
MAX252 optoisolated RS-232	64.00
MAX691 power supervisor	11.85
16C55 logic analyzer w/DRAM	19.00
IL300 <i>linear</i> optoisolator	12.70

Lots more...call/write/FAX for catalog!

UPS Ground/2nd day/next day \$6/8/16 to 48 US states,
COD add \$4. Check or MO only, no credit cards or POs.
CT residents add 6% sales tax. Quantity discounts!
Data sheets included!

Pure Unobtainium

► Your unusual part5 source ◀

89 Burbank Road
Tolland, CT 06084-2416
FAX/voice (203) 870-9304

STEVE'S OWN INK



Let Me Tell You About Yourself

Five years ago when we started the *Computer Applications Journal*, I had a specific idea and direction in mind. Much like the projects that I had been presenting for 10 years in *BYTE*, the magazine I envisioned would appeal to a select group of technically motivated individuals who appreciated the fundamental application of a computer without speculating that it involved some mystical influence.

Five years is a long time, however, and without constant reassessment, it's easy to vary from the defined course or indeed follow one too closely. In the beginning, when I had no other information, I merely defined the editorial focus of *CAJ* to be what I'd like to read.

While that approach might work for a limited time, I would be overly egocentric to assume that my interests always satisfy the majority. In fact, I can already sense a narrower focus of my technical interests. Perhaps converting from straight technical responsibility to more managerial duties has dulled the wit somewhat.

Instead of relying solely on Ken's or my personal interests to continue to stimulate the editorial direction of *CAJ*, we instead resort to asking you that question periodically. On a regular basis, we send 4-6-page questionnaires, called "Editorial Surveys," to randomly selected groups of readers. The results of these surveys help us fine-tune our editorial direction as well as identify emerging interests. These surveys have always had an astonishingly high rate of return, and we are continually encouraged by the comments we receive.

Just in case you don't know who you are, let me tell you. The *CAJ* reader is a "doer" with instinctive entrepreneurial talents. Either as an individual consultant or part of a large company project group, the *CAJ* reader views his or her success as providing real solutions to real-world problems.

The latest survey results show that the average *CAJ* reader is both technical and professional. About 74% of *CAJ* readers say they are involved with microcontroller applications in their work, but with two-thirds of the audience evenly divided between "1-50" and "10,000+" employee companies (nice inverted bell curve distribution), I'd conclude that they seek out *CAJ* as a pure technical resource. The fact that 92% save every issue supports this conclusion.

One fact, unchanged in five years, is that readers prioritized interfacing, computer control, and home automation and security as their dominant interests. There is also a broad range of secondary curiosities but these seem to share equal preference. The truly technical community gains as much relevant resource information from an article on geopositioning as it does on analog sensor interfacing. No effete snobs around here.

One remarkable statistic, probably attributable to a professional audience with money, is that the average reader has more than three personal computers. And, while these cover the spectrum as far as processors and brands, 94% have at least one IBM PC compatible. From an editorial point of view, this makes PC software support of published projects seem logical.

I won't bore you with all the other statistics, but I will say that we continue to learn at the same time we reconfirm our prime directive. Most of all, we recognize that, like ourselves, you are a demanding breed. As a successful technical professional called upon to make real-world decisions, resource material quality is of ultimate importance. Your unprecedented support and our continued growth suggest that we've met that test. Our ensuing goal is to try to present more of it.

A handwritten signature in cursive script that reads "Steve".